

- SPECIFICATION OF ADDER MODULES FOR POSITIVE INTEGERS
- HALF-ADDER AND FULL-ADDER MODULES
- CARRY-RIPPLE AND CARRY-LOOKAHEAD ADDER MODULES
- NETWORKS OF ADDER MODULES
- REPRESENTATION OF SIGNED INTEGERS:
 1. sign-and-magnitude
 2. two's-complement
 3. ones'-complement
- ADDITION AND SUBTRACTION IN TWO'S COMPLEMENT
- ARITHMETIC-LOGIC UNITS (ALU)
- COMPARATOR MODULES AND NETWORKS
- MULTIPLICATION OF POSITIVE INTEGERS

- CONVENTIONAL RADIX-2 NUMBER SYSTEM:

$$\underline{x} = (x_{n-1}, \dots, x_0) \Leftrightarrow x, \text{ integer}$$

$$x = \sum_{i=0}^{n-1} x_i \times 2^i$$

- RANGE: 0 to $2^n - 1$

ADDER MODULES FOR POSITIVE INTEGERS

 


Figure 10.1: ADDER MODULE.

$$x + y + c_{in} = 2^n c_{out} + z$$

A HIGH-LEVEL SPECIFICATION OF ADDER MODULE

INPUTS: $\underline{x} = (x_{n-1}, \dots, x_0), x_j \in \{0, 1\}$
 $\underline{y} = (y_{n-1}, \dots, y_0), y_j \in \{0, 1\}$
 $c_{\text{in}} \in \{0, 1\}$

OUTPUTS: $\underline{z} = (z_{n-1}, \dots, z_0), z_j \in \{0, 1\}$
 $c_{\text{out}} \in \{0, 1\}$

FUNCTIONS: $z = (x + y + c_{\text{in}}) \bmod 2^n$

$$c_{\text{out}} = \begin{cases} 1 & \text{if } (x + y + c_{\text{in}}) \geq 2^n \\ 0 & \text{otherwise} \end{cases}$$

EXAMPLE for n=5

x	y	c_{in}	z	c_{out}
12	14	1	$(12 + 14 + 1) \bmod 32 = 27$	0 because $(12 + 14 + 1) < 32$
19	14	1	$(19 + 14 + 1) \bmod 32 = 2$	1 because $(19 + 14 + 1) > 32$

CARRY-RIPPLE ADDER IMPLEMENTATION

 


Figure 10.2: CARRY-RIPPLE ADDER MODULE.

- DELAY OF CARRY-RIPPLE ADDER

$$t_p(net) = (n - 1)t_c + \max(t_z, t_c)$$

$$t_c = \text{Delay}(c_i \rightarrow c_{i+1})$$

$$t_z = \text{Delay}(c_i \rightarrow z_i)$$

HIGH-LEVEL SPECIFICATION OF FULL-ADDER

$$x_i + y_i + c_i = 2c_{i+1} + z_i$$

INPUTS: $x_i, y_i, c_i \in \{0, 1\}$

OUTPUTS: $z_i, c_{i+1} \in \{0, 1\}$

FUNCTION: $z_i = (x_i + y_i + c_i) \bmod 2$

$$c_{i+1} = \begin{cases} 1 & \text{if } (x_i + y_i + c_i) \geq 2 \\ 0 & \text{otherwise} \end{cases}$$

FULL-ADDER IMPLEMENTATION

x_i	y_i	c_i	c_{i+1}	z_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$z_i = x_i y_i' c_i' + x_i' y_i c_i' + x_i' y_i' c_i + x_i y_i c_i$$

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

FULL ADDER TWO-LEVEL IMPLEMENTATION

 


Figure 10.3: IMPLEMENTATIONS OF FULL-ADDER MODULE: a) TWO-LEVEL.

ALTERNATIVE IMPLEMENTATION

- ADDITION mod 2 \rightarrow SUM IS 1 WHEN NUMBER OF 1'S IN INPUTS (including the carry-in) IS ODD:

$$z_i = x_i \oplus y_i \oplus c_i$$

- CARRY-OUT IS 1 WHEN $(x_i + y_i = 2)$ or $(x_i + y_i = 1 \text{ and } c_i = 1)$:

$$c_{i+1} = x_i y_i + (x_i \oplus y_i) c_i$$

- INTERMEDIATE VARIABLES

PROPAGATE $p_i = x_i \oplus y_i$

GENERATE $g_i = x_i \cdot y_i$

- HALF-ADDER

x_i	y_i	g_i	p_i
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

IMPLEMENTATION WITH HALF-ADDERS

- FA EXPRESSIONS IN TERMS OF p_i 's, g_i 's and c_i 's

$$z_i = p_i \oplus c_i$$

$$c_{i+1} = g_i + p_i \cdot c_i$$

 
 


Figure 10.3: IMPLEMENTATIONS OF FULL-ADDER MODULE: b) MULTILEVEL GATE NETWORK WITH XORs, ANDs and OR; c) WITH XORs and NANDs.

 


Figure 10.2: CARRY-RIPPLE ADDER MODULE.

- WORST-CASE DELAY $t_p = t_{XOR} + 2(n - 1)t_{NAND} + \max(2t_{NAND}, t_{XOR})$

CHARACTERISTICS OF FULL-ADDER IN CMOS FAMILY

Input	[standard loads]
C_i	1.3
x_i	1.1
y_i	1.3
Size: 7 [equivalent gates]	

From	To	Propagation delays	
		t_{pLH} [ns]	t_{pHL} [ns]
C_i	z_i	$0.43 + 0.03L$	$0.49 + 0.02L$
x_i	z_i	$0.68 + 0.04L$	$0.74 + 0.02L$
y_i	z_i	$0.68 + 0.04L$	$0.74 + 0.02L$
C_i	C_{i+1}	$0.36 + 0.04L$	$0.40 + 0.02L$
x_i	C_{i+1}	$0.73 + 0.04L$	$0.71 + 0.02L$
y_i	C_{i+1}	$0.37 + 0.04L$	$0.64 + 0.02L$

L : load on the gate output

- FASTER IMPLEMENTATION
- ADDITION AS A TWO-STEP PROCESS:
 1. DETERMINE THE VALUES OF ALL THE CARRIES
 2. SIMULTANEOUSLY COMPUTE ALL THE RESULT BITS

CARRY-LOOKAHEAD ADDER MODULE

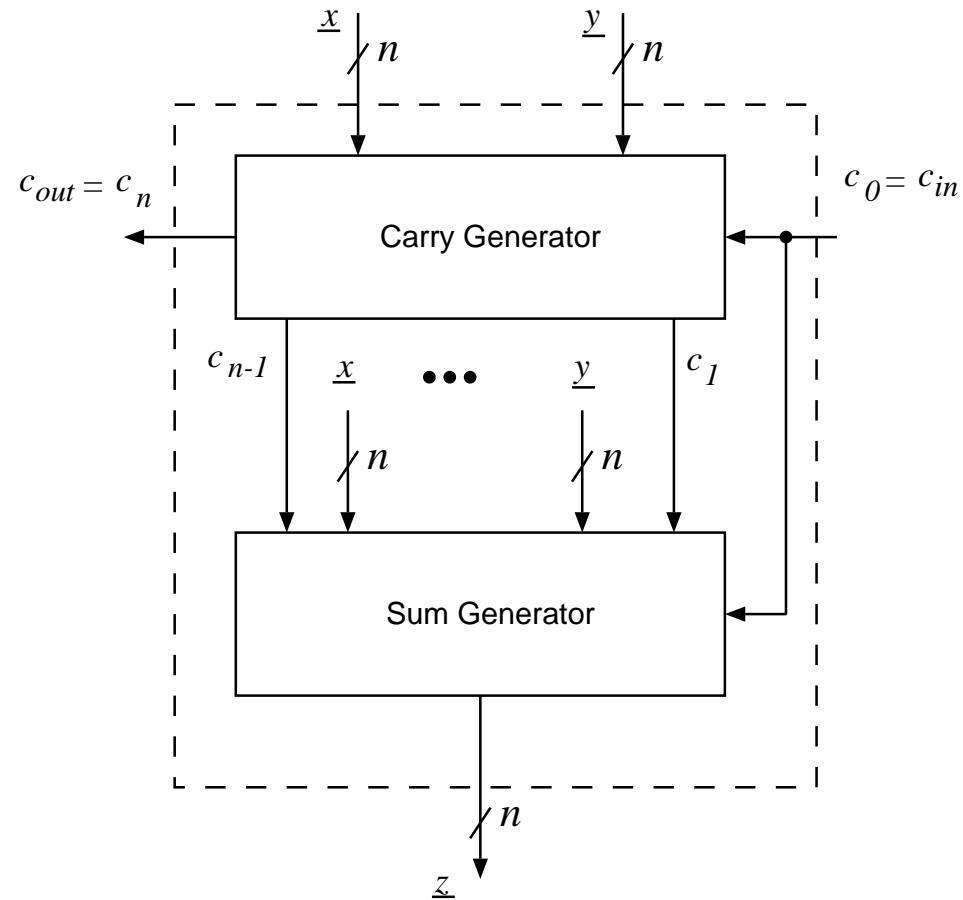


Figure 10.4: CARRY-LOOKAHEAD ADDER MODULE.

- INTERMEDIATE CARRIES:

$$c_{i+1} = g_i + p_i \cdot c_i$$

BY SUBSTITUTION,

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 c_1$$

$$= g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2 c_2$$

$$= g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$

$$c_4 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0$$

 


Figure 10.5: CARRY-LOOKAHEAD ADDER: b) 4-BIT MODULE (CLA-4); (CLG-4).

$$\begin{aligned}
 t_p(x_0 \rightarrow c_4) &= t_{pg} + t_{CLG-4} \\
 t_p(c_0 \rightarrow c_4) &= t_{CLG-4} \\
 t_p(x_0 \rightarrow P, G) &= t_{pg} + t_{CLG-4} \\
 t_p(x_0 \rightarrow z_3) &= t_{pg} + t_{CLG-4} + t_{XOR}
 \end{aligned}$$

$P = 1$: c_{in} PROPAGATED BY THE MODULE

$G = 1$: $c_{out} = 1$ GENERATED BY THE MODULE,
IRRESPECTIVE OF c_{in}

$$P = \begin{cases} 1 & \text{if } x + y = 2^4 - 1 \\ 0 & \text{otherwise} \end{cases}$$

$$G = \begin{cases} 1 & \text{if } x + y \geq 2^4 \\ 0 & \text{otherwise} \end{cases}$$

$$c_{out} = G + P \cdot c_{in}$$

$$P = p_3 p_2 p_1 p_0$$

$$G = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0$$

NETWORKS OF ADDER MODULES

ITERATIVE (CARRY-RIPPLE) ADDER NETWORK

$$\begin{aligned}\underline{x} &= (\underline{x}^{(3)}, \underline{x}^{(2)}, \underline{x}^{(1)}, \underline{x}^{(0)}) \\ \underline{x}^{(3)} &= (x_{15}, x_{14}, x_{13}, x_{12}) \\ \underline{x}^{(2)} &= (x_{11}, x_{10}, x_9, x_8) \\ \underline{x}^{(1)} &= (x_7, x_6, x_5, x_4) \\ \underline{x}^{(0)} &= (x_3, x_2, x_1, x_0)\end{aligned}$$

where

$$x = 2^{12}x^{(3)} + 2^8x^{(2)} + 2^4x^{(1)} + x^{(0)}$$

16-BIT CARRY-RIPPLE ADDER

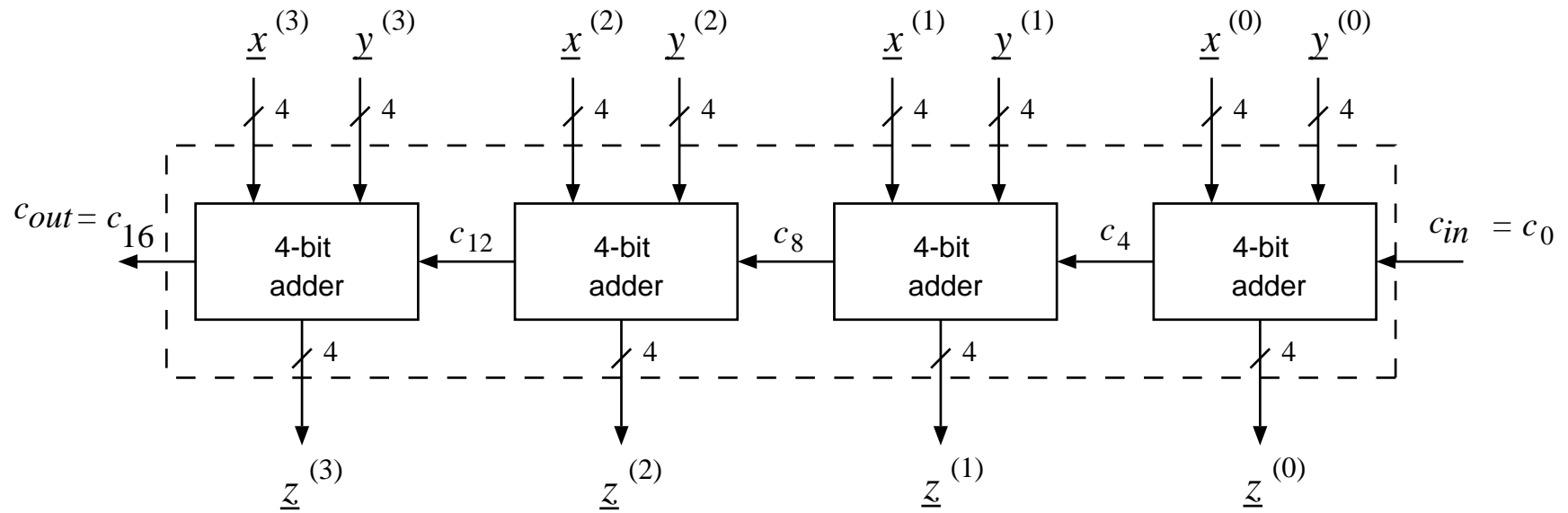


Figure 10.6: 16-BIT CARRY-RIPPLE ADDER NETWORK USING 4-BIT ADDER MODULES.

CARRY-LOOKAHEAD ADDER NETWORK

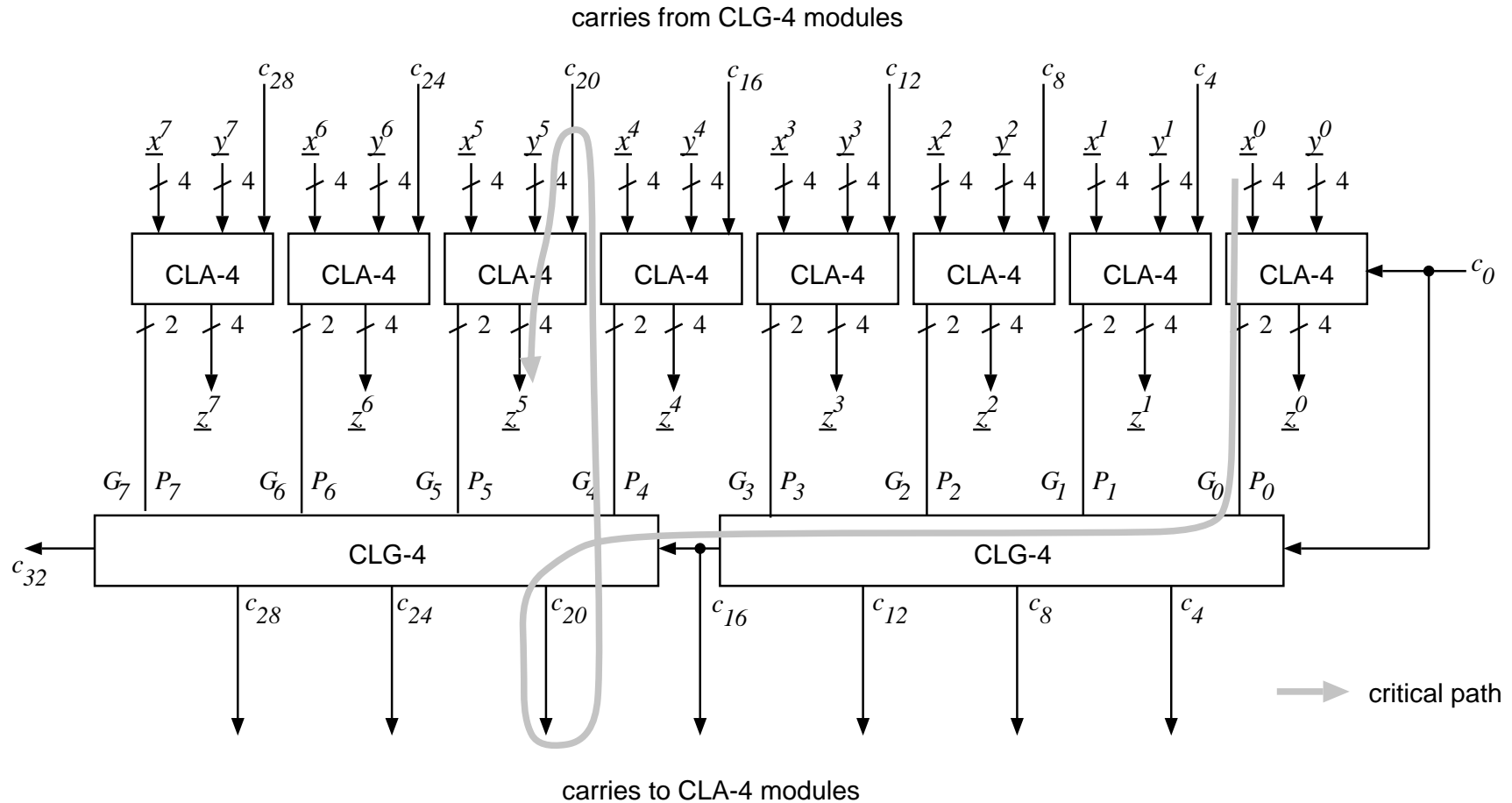


Figure 10.7: 32-BIT CARRY-LOOKAHEAD ADDER USING CLA-4 AND CLG-4 MODULES.

- PROPAGATION DELAY:

$$t_p(\text{net}) = t_{PG} + 2t_{\text{CLG-4}} + t_{\text{ADD}}$$

CLA ADDER (cont.)

$$c_4 = G_0 + P_0c_0$$

$$c_8 = G_1 + P_1G_0 + P_1P_0c_0$$

$$c_{12} = G_2 + P_2G_1 + P_2P_1G_0 + P_2P_1P_0c_0$$

$$c_{16} = G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0 + P_3P_2P_1P_0c_0$$

$$P_0 = p_3 \cdot p_2 \cdot p_1 \cdot p_0$$

$$G_0 = g_3 + g_2p_3 + g_1p_3p_2 + g_0p_3p_2p_1$$

- TWO COMMON REPRESENTATIONS:
 - SIGN-AND-MAGNITUDE (SM)
 - TRUE-AND-COMPLEMENT (TC)

SIGN-AND-MAGNITUDE (SM) SYSTEM

- x REPRESENTED BY PAIR (x_s, x_m)

sign:

$$x_s = \begin{cases} 0 & \text{if } x \geq 0 \\ 1 & \text{if } x \leq 0 \end{cases}$$

magnitude:

x_m

- RANGE OF SIGNED INTEGERS

total number of bits: n

sign: 1

magnitude: $n - 1$

$$-(2^{n-1} - 1) \leq x \leq 2^{n-1} - 1$$

- TWO REPRESENTATIONS OF ZERO:

$x_s = 0, x_m = 0$ (positive zero)

$x_s = 1, x_m = 0$ (negative zero)

TWO'S-COMPLEMENT SYSTEM

- NO SEPARATION BETWEEN THE REPRESENTATION OF SIGN AND REPRESENTATION OF MAGNITUDE
- SIGNED INTEGER x REPRESENTED BY *POSITIVE* INTEGER x_R
- MAP 2: BINARY REPRESENTATION OF x_R

$$x_R = \sum_{i=0}^{n-1} x_i 2^i, \quad 0 \leq x_R \leq 2^n - 1$$

- MAP 1: TWO'S COMPLEMENT

$$x_R = x \bmod 2^n$$

BY DEFINITION OF \bmod , FOR $|x| < 2^n$: equivalent to

$$x_R = \begin{cases} x & \text{if } x \geq 0 \\ 2^n - |x| & \text{if } x < 0 \end{cases}$$

FOR UNAMBIGUOUS SYMMETRICAL REPRESENTATION

$$|x|_{max} \leq 2^{n-1} - 1$$

x	-4	-3	-2	-1	0	1	2	3
x_R	4	5	6	7	0	1	2	3

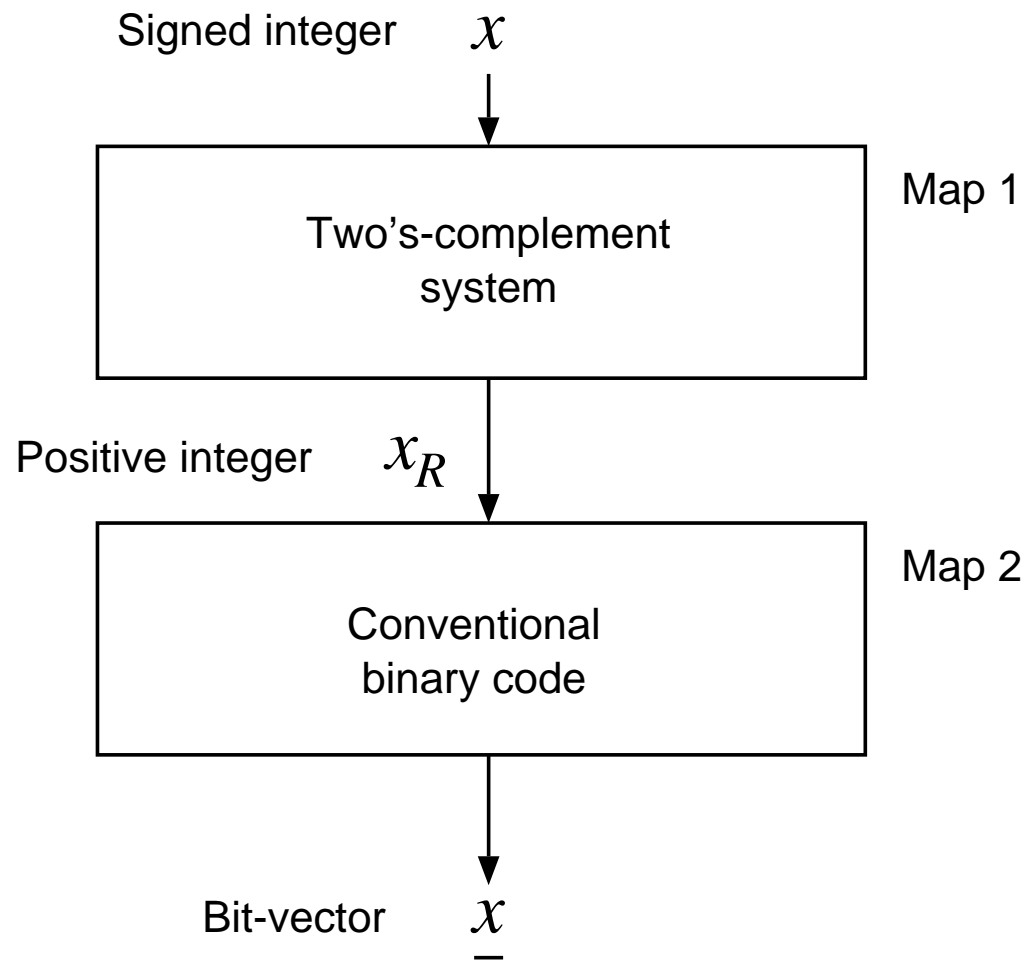


Figure 10.8: SIGNED INTEGER REPRESENTED BY POSITIVE INTEGER.

 


Figure 10.9: TWO'S COMPLEMENT REPRESENTATION FOR $n = 4$.

MAPPING IN TWO'S-COMPLEMENT SYSTEM

x	x_R	\mathcal{X}	
0	0	00...000	True forms (positive) $x_R = x$
1	1	00...001	
2	2	00...010	
-	-	-	
-	-	-	
-	-	-	
$2^{n-1} - 1$	$2^{n-1} - 1$	01...111	
-2^{n-1}	2^{n-1}	10...000	Complement forms (negative) $x_R = 2^n - x $
$-(2^{n-1} - 1)$	$2^{n-1} + 1$	10...001	
-	-	-	
-	-	-	
-	-	-	
-2	$2^n - 2$	11...110	
-1	$2^n - 1$	11...111	

EXAMPLE 10.2: MAPPINGS FOR $-4 \leq x \leq 3$

x	x_R	\mathcal{X}
3	3	011
2	2	010
1	1	001
0	0	000
-1	7	111
-2	6	110
-3	5	101
-4	4	100

CONVERSE MAPPING

$$x = \begin{cases} x_R & \text{if } x_R \leq 2^{n-1} - 1 \quad (x \geq 0) \\ x_R - 2^n & \text{if } x_R \geq 2^{n-1} \quad (x < 0) \end{cases}$$

IN TERMS OF BIT VECTOR $(x_{n-1}, x_{n-2}, \dots, x_1, x_0)$

i) For $x_R < 2^{n-1}$, bit x_{n-1} is 0 and $x \geq 0$.

$$x = x_R = 0 \times 2^{n-1} + \sum_{i=0}^{n-2} x_i 2^i$$

ii) For $x_R \geq 2^{n-1}$ bit x_{n-1} is 1 and $x < 0$.

$$x = x_R - 2^n = (1 \times 2^{n-1} + \sum_{i=0}^{n-2} x_i 2^i) - 2^n = -1 \times 2^{n-1} + \sum_{i=0}^{n-2} x_i 2^i$$

COMBINING BOTH CASES

$$x = -x_{n-1} 2^{n-1} + \sum_{i=0}^{n-2} x_i 2^i$$

$$x = -x_{n-1}2^{n-1} + \sum_{i=0}^{n-2} x_i 2^i$$

8-BIT EXAMPLES:

\underline{x}	x
01000101	0 + 69 = 69
11000101	-128 + 69 = -58

SIGN DETECTION:

$$x \geq 0 \quad \mathbf{if} \quad x_{n-1} = 0$$

$$x < 0 \quad \mathbf{if} \quad x_{n-1} = 1$$

ONES'-COMPLEMENT SYSTEM

$$x_R = x \bmod C$$

ONES'-COMPLEMENT SYSTEM: $C = 2^n - 1$

- the ones'-complement system symmetrical, with the range $-(2^n - 1) \leq x \leq 2^n - 1$;
- two representations for zero, namely $x_R = 0$ and $x_R = 2^n - 1$;
- the sign also detected by the most-significant bit

$$x \geq 0 \quad \mathbf{if} \quad (x_{n-1} = 0) \quad \mathbf{or} \quad (x_R = 2^n - 1)$$

MAPPING IN ONES'-COMPLEMENT SYSTEM

x	x_R	\mathcal{X}	
0	0	00...000	True forms (positive) $x_R = x$
1	1	00...001	
2	2	00...010	
-	-	-	
-	-	-	
-	-	-	
$2^{n-1} - 1$	$2^{n-1} - 1$	01...111	
$-(2^{n-1} - 1)$	2^{n-1}	10...000	Complement forms (negative) $x_R = 2^n - 1 - x $
-	-	-	
-	-	-	
-2	$2^n - 3$	11...101	
-1	$2^n - 2$	11...110	
0	$2^n - 1$	11...111	

ADDITION IN TWO'S COMPLEMENT SYSTEM

- TO GET

$$z = x + y$$

COMPUTE

$$z_R = (x_R + y_R) \bmod 2^n$$

CORRECT IF $-2^{n-1} \leq (x + y) \leq 2^{n-1} - 1$

- PROOF: CONSIDER

$$(x_R + y_R) \bmod 2^n$$

AND SHOW THAT IT CORRESPONDS TO z_R

BY DEFINITION OF THE REPRESENTATION,

$$x_R = x \bmod 2^n \quad \text{and} \quad y_R = y \bmod 2^n$$

THEREFORE,

$$\begin{aligned} (x_R + y_R) \bmod 2^n &= (x \bmod 2^n + y \bmod 2^n) \bmod 2^n \\ &= (x + y) \bmod 2^n = z \bmod 2^n \end{aligned}$$

BY DEFINITION OF REPRESENTATION

$$z \bmod 2^n = z_R$$

2's COMPLEMENT ADDITION: A SUMMARY

1. ADD x_R AND y_R (use adder for positive operands)
2. PERFORM THE *mod* OPERATION
 - DOES NOT DEPEND ON THE RELATIVE MAGNITUDES OF THE OPERANDS AND ON THEIR SIGNS (simpler than in S+M)

EXAMPLES OF ADDITION FOR $C=64$ and $-32 \leq x, y, z \leq 31$

Signed operands		Representation		Two's-complement addition	Signed result
x	y	x_R	y_R	$(x_R + y_R) \bmod 64 = z_R$	z
13	9	13	9	$22 \bmod 64 = 22$	22
13	-9	13	55	$68 \bmod 64 = 4$	4
-13	9	51	9	$60 \bmod 64 = 60$	-4
-13	-9	51	55	$106 \bmod 64 = 42$	-22

THE *mod* OPERATION

- Let $w_R = x_R + y_R$. Then

$$x_R, y_R < 2^n \Rightarrow w_R < 2 \times 2^n$$

$$z_R = w_R \bmod 2^n = \begin{cases} w_R & \text{if } w_R < 2^n \\ w_R - 2^n & \text{if } 2^n \leq w_R < 2 \times 2^n \end{cases}$$

- Since $w_R < 2 \times 2^n$

$$\underline{w} = (w_n, w_{n-1}, \dots, w_0)$$

$$w_R = \begin{cases} < 2^n & \text{if } w_n = 0 \\ \geq 2^n & \text{if } w_n = 1 \end{cases}$$

Case 1. $w_R < 2^n$. Then $w_R \bmod 2^n = w_R \Leftrightarrow (w_{n-1}, \dots, w_0)$.

Case 2. $w_R \geq 2^n$

$$\begin{aligned} w_R \bmod 2^n = w_R - 2^n &\Leftrightarrow (1, w_{n-1}, \dots, w_0) - (1, 0, \dots, 0) \\ &= (w_{n-1}, \dots, w_0) \end{aligned}$$

- **CONCLUSION:** $w_R \bmod 2^n = (w_{n-1}, \dots, w_0)$

- *mod* OPERATION PERFORMED BY DISCARDING MOST-SIGNIFICANT BIT OF w
- 2'S COMPLEMENT ADDITION:
RESULT CORRESPONDS TO OUTPUT OF ADDER, DISCARDING THE CARRY-OUT

$$\underline{z} = ADD(\underline{x}, \underline{y}, 0)$$

 


Figure 10.10: TWO'S-COMPLEMENT ADDER MODULE.

EXAMPLES OF 2'S COMPLEMENT ADDITION

	Bit-level computation	Positive representation	Signed values
$n = 4$	$\underline{x} = 1011$	$x_R = 11$	$x = -5$
	$\underline{y} = 0101$	$y_R = 5$	$y = 5$
	$\underline{w} = 10000$	$w_R = 16$	
	$\underline{z} = 0000$	$z_R = 0$	$z = 0$
$n = 8$	$\underline{x} = 11011010$	$x_R = 218$	$x = -38$
	$\underline{y} = 11110001$	$y_R = 241$	$y = -15$
	$\underline{w} = 111001011$	$w_R = 459$	
	$\underline{z} = 11001011$	$z_R = 203$	$z = -53$

CHANGE OF SIGN IN TWO'S COMPLEMENT SYSTEM

- $z = -x$

$$z_R = (2^n - x_R) \text{ mod } 2^n$$

$x = 0$: since $z = -x = 0$ we have $z_R = x_R = 0$. Moreover,

$$z_R = (2^n - 0) \text{ mod } 2^n = 0$$

$x > 0$: since $z = -x$ is negative,

$$z_R = 2^n - |z| = 2^n - |x|$$

Moreover, x is positive so that

$$x_R = x$$

Substitute: $z_R = 2^n - x_R$.

$x < 0$: since $z = -x$ is positive,

$$z_R = z = -x$$

Moreover, x is negative so that

$$x_R = 2^n - |x| = 2^n + x$$

Substitute: $z_R = 2^n - x_R$.

CHANGE OF SIGN (cont.)

- DIRECT SUBTRACTION $2^n - x_R$ COMPLEX

EXAMPLE:

$$\begin{array}{r} 2^8 \quad 100000000 \\ x_R \quad 01011110 \\ \hline 10100010 \end{array}$$

- INSTEAD, USE $2^n = (2^n - 1) + 1$

$$z_R = (2^n - 1 - x_R) + 1$$

- THE COMPLEMENT WITH RESPECT TO $2^n - 1$: COMPLEMENT EACH BIT OF \underline{x}

$$\begin{array}{r} x_R = 17 \quad 010001 \\ 63 - x_R \quad 111111 - 010001 \\ 101110 \end{array}$$

CHANGE-OF-SIGN OPERATION

TWO-STEP OPERATION:

1. COMPLEMENT EACH BIT OF x denoted x' .
2. ADD 1 (set carry-in $c_0 = 1$)

● DESCRIPTION:

$$z = ADD(\underline{x'}, \underline{0}, 1)$$

EXAMPLE FOR $n = 4$, $x = -3$:

x	1101	$x = -3$
x'	0010	
0	0000	
c_0	1	
z	0011	$z = 3$

SUBTRACTION IN TWO'S COMPLEMENT SYSTEM

- $z = x - y = x + (-y)$

$$z_R = (x_R + (2^n - 1 - y_R) + 1) \bmod 2^n$$

- THE CORRESPONDING DESCRIPTION

$$z = ADD_R(\underline{x}, \underline{y}', 1)$$

EXAMPLE:

$$\begin{array}{r|l}
 \underline{x} & 01100000 \\
 \underline{y} \ 00110001 & \underline{y}' \ 11001110 \\
 & \phantom{\underline{y}' } \\
 \underline{z} & 00101111
 \end{array}$$

SUMMARY OF 2'S COMPLEMENT OPERATIONS

OPERATION	2's COMPLEMENT SYSTEM
$z = x + y$	$z = ADD(\underline{x}, \underline{y}, 0)$
$z = -x$	$z = ADD(\underline{x}', 0, 1)$
$z = x - y$	$z = ADD(\underline{x}, \underline{y}', 1)$

OVERFLOW DETECTION IN ADDITION

- OVERFLOW – result exceeds most positive or negative representable integer

$$-2^{n-1} \leq z \leq 2^{n-1} - 1$$

- BOTH OPERANDS SAME SIGN, RESULT OPPOSITE SIGN

$$v = x'_{n-1}y'_{n-1}z_{n-1} + x_{n-1}y_{n-1}z'_{n-1}$$

 


Figure 10.11: OVERFLOW IN TWO'S-COMPLEMENT SYSTEM.

TWO'S COMPLEMENT ARITHMETIC UNIT

INPUTS: $\underline{x} = (x_{n-1}, \dots, x_0), x_j \in \{0, 1\}$
 $\underline{y} = (y_{n-1}, \dots, y_0), y_j \in \{0, 1\}$
 $c_{in} \in \{0, 1\}$
 $F = (f_2, f_1, f_0)$

OUTPUTS: $\underline{z} = (z_{n-1}, \dots, z_0), z_j \in \{0, 1\}$
 $c_{out}, sgn, zero, ovf \in \{0, 1\}$

FUNCTIONS:

F	Operation		
001	ADD	add	$z = x + y$
011	SUB	subtract	$z = x - y$
101	ADDC	add with carry	$z = x + y + c_{in}$
110	CS	change sign	$z = -x$
010	INC	increment	$z = x + 1$

$sgn = 1$ **if** $z < 0$, 0 **otherwise** (the sign)

$zero = 1$ **if** $z = 0$, 0 **otherwise**

$ovf = 1$ **if** z overflows, 0 **otherwise**

 


Figure 10.12: IMPLEMENTATION OF TWO'S-COMPLEMENT ARITHMETIC UNIT.

- OPERATION IDENTIFIED BY BIT-VECTOR $F = (f_2, f_1, f_0)$
- COMPLEMENT OPERATION $\underline{a} = \text{COMPL}(\underline{b}, K)$:

$$a_i = \begin{cases} b_i & \text{if } K = 0 \\ b'_i & \text{if } K = 1 \end{cases}$$

Operation	Op-code		Control Signals		
			$f_2 f_1 f_0$	z	K_x
ADD	001	$\text{ADD}(\underline{x}, \underline{y}, 0)$	0	0	1
SUB	011	$\text{ADD}(\underline{x}, \underline{y}', 1)$	0	1	1
ADDC	101	$\text{ADD}(\underline{x}, \underline{y}, c_{\text{in}})$	0	0	1
CS	110	$\text{ADD}(\underline{x}', \underline{0}, 1)$	1	d.c.	0
INC	010	$\text{ADD}(\underline{x}, \underline{0}, 1)$	0	d.c.	0

- CONTROL SIGNALS:

$$K_x = f_2 f_1$$

$$K_y = f_1$$

$$K_{MX} = f_0$$

$$c_0 = f_1 + f_2 f_0 c_{\text{in}}$$

- *ARITHMETIC-LOGIC UNIT*
module realizing set of arithmetic and logic functions
- Why build ALUs?
 1. Use in many different applications
 2. ALU modules used in processors: function selected by control unit

TYPICAL EXAMPLE OF ALU

Control (S)	Function
ZERO	$z = 0$
ADD	$z = (x + y + c_{in}) \bmod 16$
SUB	$z = (x + y' + c_{in}) \bmod 16$
EXSUB	$z = (x' + y + c_{in}) \bmod 16$
AND	$\underline{z} = \underline{x} \cdot \underline{y}$
OR	$\underline{z} = \underline{x} + \underline{y}$
XOR	$\underline{z} = \underline{x} \oplus \underline{y}$
ONE	$\underline{z} = 1111$

a' denotes the integer represented by vector \underline{a}'
 \cdot , $+$, and \oplus are applied to the corresponding bits

4-bit ALU

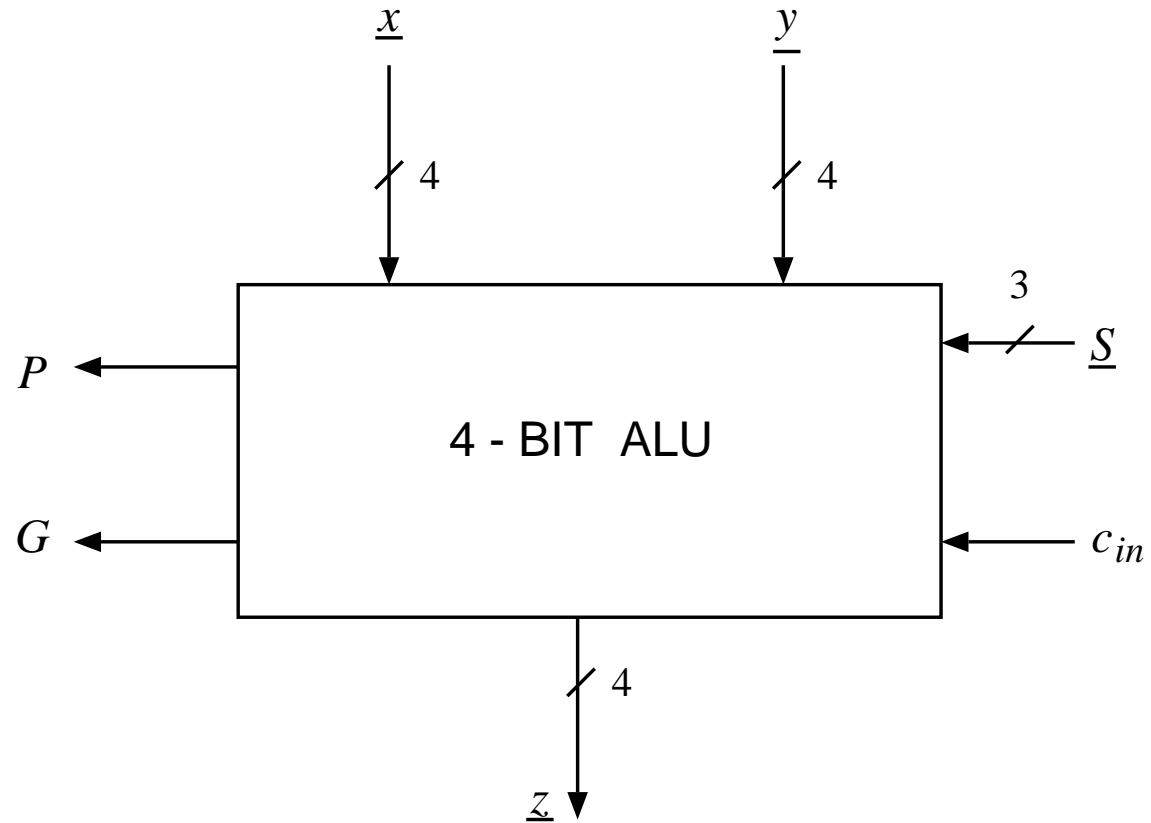


Figure 10.13: 4-bit ALU.

NETWORKS OF ALU MODULES

- MODULE HAS NO CARRY-OUT SIGNAL
 - cannot be used directly in an iterative (carry-ripple) network
 - carry-out signal implemented as

$$c_{\text{out}} = G + P \cdot c_{\text{in}}$$

- *carry-skip network*

16-bit ALU

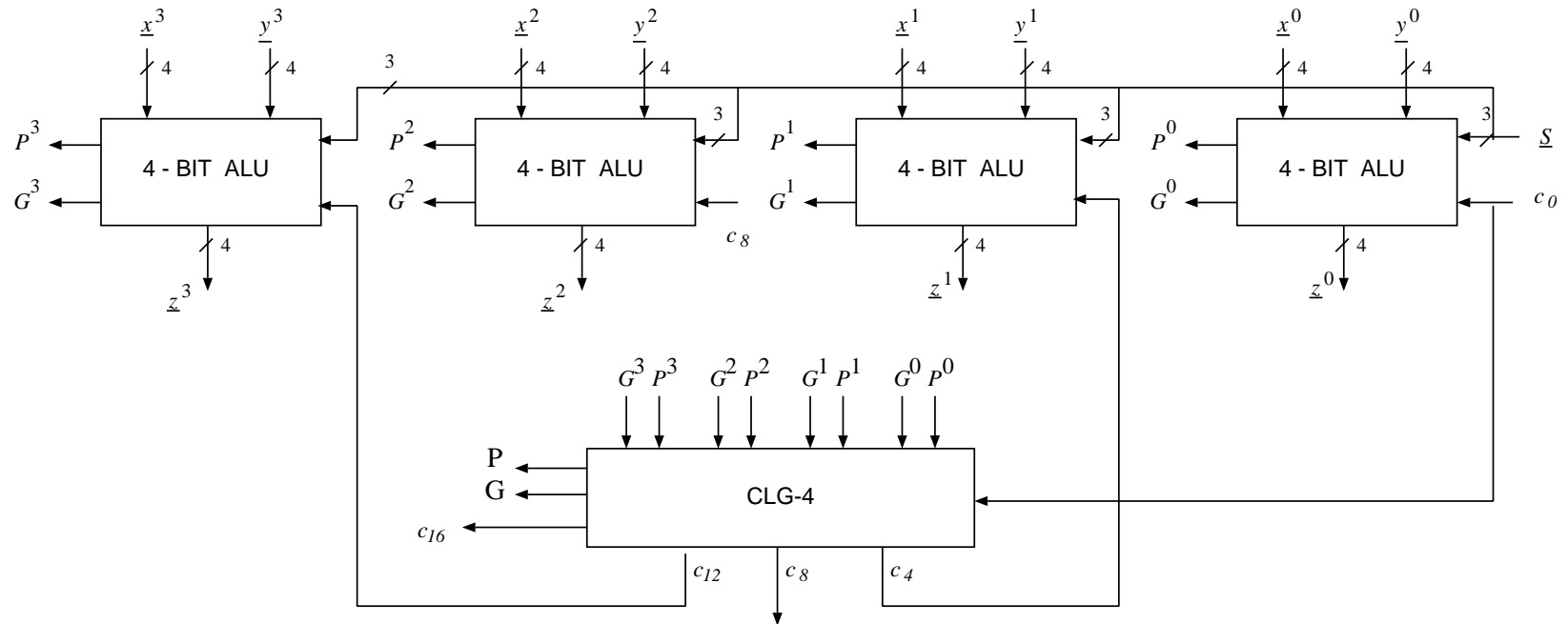


Figure 10.14: 16-bit ALU.

COMPARATOR MODULES

- HIGH-LEVEL DESCRIPTION OF AN n -BIT COMPARATOR:

INPUTS: $\underline{x} = (x_{n-1}, \dots, x_0), \quad x_j \in \{0, 1\}$

$\underline{y} = (y_{n-1}, \dots, y_0), \quad y_j \in \{0, 1\}$

$c_{in} \in \{G, E, S\}$

OUTPUT: $z \in \{G, E, S\}$

FUNCTION: $z = \begin{cases} G & \text{if } (x > y) \text{ or } (x = y \text{ and } c_{in} = G) \\ E & \text{if } (x = y) \text{ and } (c_{in} = E) \\ S & \text{if } (x < y) \text{ or } (x = y \text{ and } c_{in} = S) \end{cases}$

x and y – the integers represented \underline{x} and \underline{y}

- IMPLEMENTATION OF 4-bit COMPARATOR MODULE

$$\underline{c}_{in} = (c_{in}^G, c_{in}^E, c_{in}^S) \quad , \quad c_{in}^G, c_{in}^E, c_{in}^S \in \{0, 1\}$$

$$\underline{z} = (z^G, z^E, z^S) \quad , \quad z^G, z^E, z^S \in \{0, 1\}$$

 


Figure 10.15: 4-BIT COMPARATOR MODULE: a) block diagram; b) gate-network implementation.

$$S_i = x_i' y_i$$

$$E_i = (x_i \oplus y_i)', \quad i = 0, \dots, 3$$

$$G_i = x_i y_i'$$

$$z^G = G_3 + E_3 G_2 + E_3 E_2 G_1 + E_3 E_2 E_1 G_0 + E_3 E_2 E_1 E_0 c_{in}^G$$

$$z^E = E_3 E_2 E_1 E_0 c_{in}^E$$

$$z^S = S_3 + E_3 S_2 + E_3 E_2 S_1 + E_3 E_2 E_1 S_0 + E_3 E_2 E_1 E_0 c_{in}^S$$

ITERATIVE COMPARATOR NETWORK

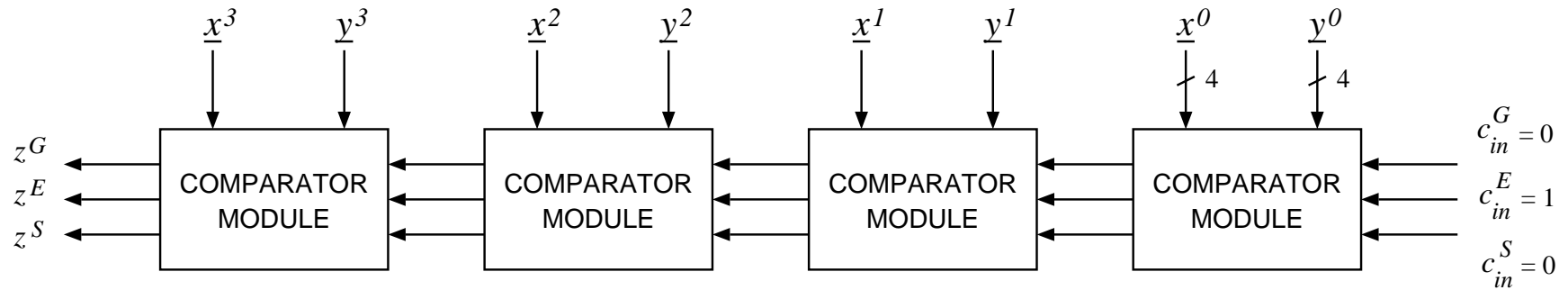


Figure 10.16: 16-BIT ITERATIVE COMPARATOR NETWORK.

TREE COMPARATOR NETWORK

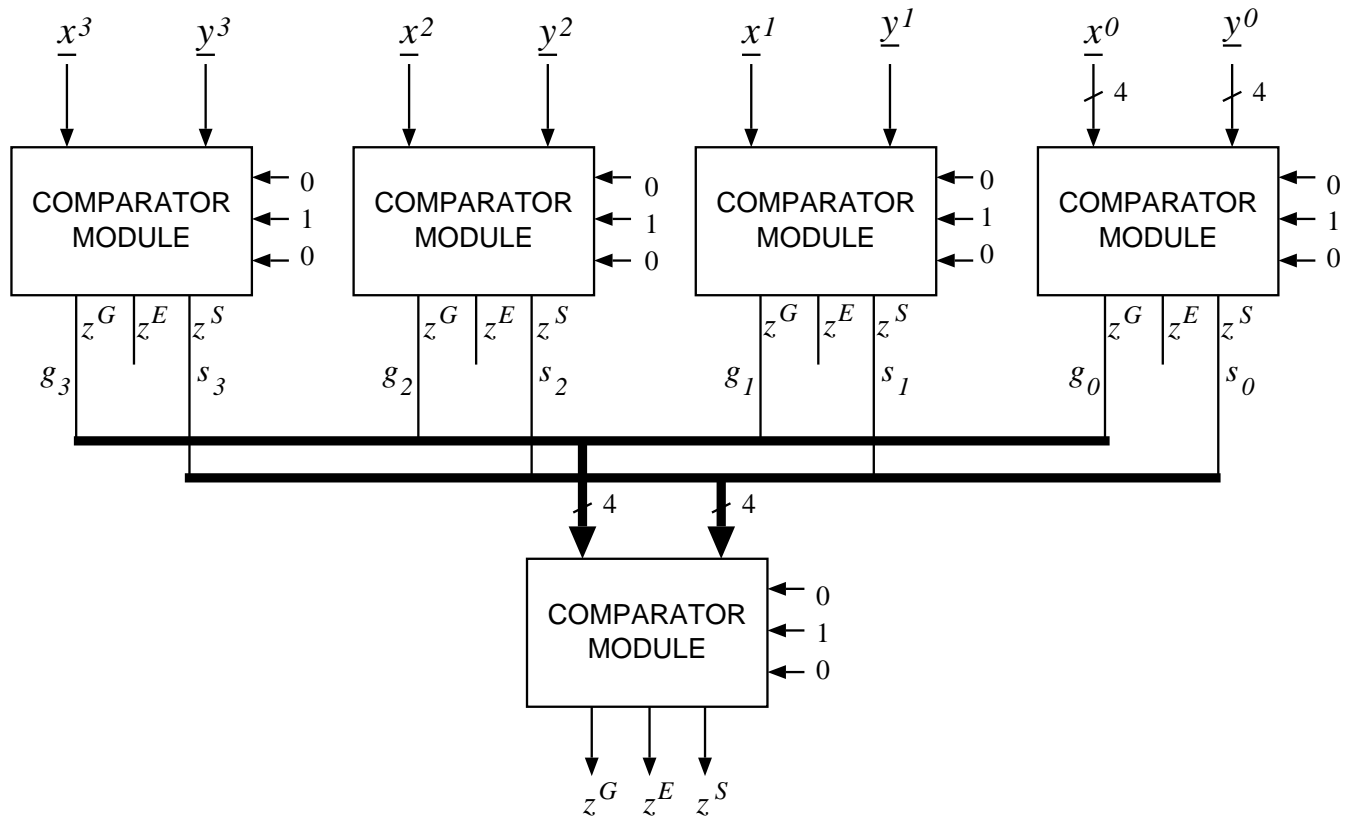


Figure 10.17: 16-BIT TREE COMPARATOR NETWORK.

TREE COMPARATOR (cont.)

$$z^G = \begin{cases} 1 & \text{if } g > s \\ 0 & \text{otherwise} \end{cases}$$

$$z^E = \begin{cases} 1 & \text{if } g = s \\ 0 & \text{otherwise} \end{cases}$$

$$z^S = \begin{cases} 1 & \text{if } g < s \\ 0 & \text{otherwise} \end{cases}$$

- g and s are the integers represented by the vectors \underline{g} and \underline{s} , respectively.

MULTIPLIERS

- $n \times m$ bits multiplier:

$$0 \leq x \leq 2^n - 1 \text{ (the multiplicand)}$$

$$0 \leq y \leq 2^m - 1 \text{ (the multiplier),}$$

$$0 \leq z \leq (2^n - 1)(2^m - 1) \text{ (the product).}$$

- The high-level function:

$$z = x \times y$$

$$z = x \left(\sum_{i=0}^{m-1} y_i 2^i \right) = \sum_{i=0}^{m-1} x y_i 2^i$$

Since y_i is either 0 or 1, we get

$$x y_i = \begin{cases} 0 & \text{if } y_i = 0 \\ x & \text{if } y_i = 1 \end{cases}$$

 


Figure 10.18: IMPLEMENTATION OF AN 8×6 MULTIPLIER: a) PRIMITIVE MODULES; b) NETWORK.

MULTIPLIER DELAY

- delay of the buffer which connects signal y_0 to the n AND gates
- delay of the AND gate
- delay of the adders

$$t_{\text{adders}} = t_c(n - 1) + t_s + (t_c + t_s)(m - 2)$$

If $t_s = t_c$, we get

$$t_{\text{adders}} = (n + 2(m - 2))t_s = (n + 2m - 4)t_s$$

FOR THE 8×6 CASE: $t_{\text{adders}} = (8 + 12 - 4)t_s = 16t_s$

EXAMPLE OF NETWORKS WITH STANDARD ARITHMETIC MODULES ⁶³

Inputs: $a[3], a[2], a[1], a[0], b[3], b[2], b[1], b[0] \in \{0, \dots, 2^{16} - 1\}$

$\underline{e} = (e_3, e_2, e_1, e_0)$, $e_i \in \{0, 1\}$

Outputs: $c[3], c[2], c[1], c[0] \in \{0, \dots, 2^{17} - 1\}$

$d \in \{0, 1, 2, 3\}$

$f \in \{0, 1\}$

Function:

$$f = \begin{cases} 1 & \text{if at least one } e_j = 1 \\ 0 & \text{otherwise} \end{cases} , \quad j = 0, 1, 2, 3$$

$$d = \begin{cases} i & \text{if } e_i \text{ is the highest priority event} \\ 0 & \text{if no event occurred} \end{cases}$$

$$c[i] = \begin{cases} a[i] + b[i] & \text{if } e_i \text{ is the highest priority event} \\ 0 & \text{otherwise} \end{cases}$$

MODULAR IMPLEMENTATION

CONSISTS OF

- a PRIORITY ENCODER to determine the highest-priority event;
- an ADDER;
- two SELECTORS (multiplexers) to select the corresponding inputs to the adder;
- a DISTRIBUTOR (demultiplexer) to send the output of the adder to the corresponding system output; and
- an OR gate to determine whether at least one event has occurred.

 


Figure 10.19: NETWORK IN EXAMPLE 10.5