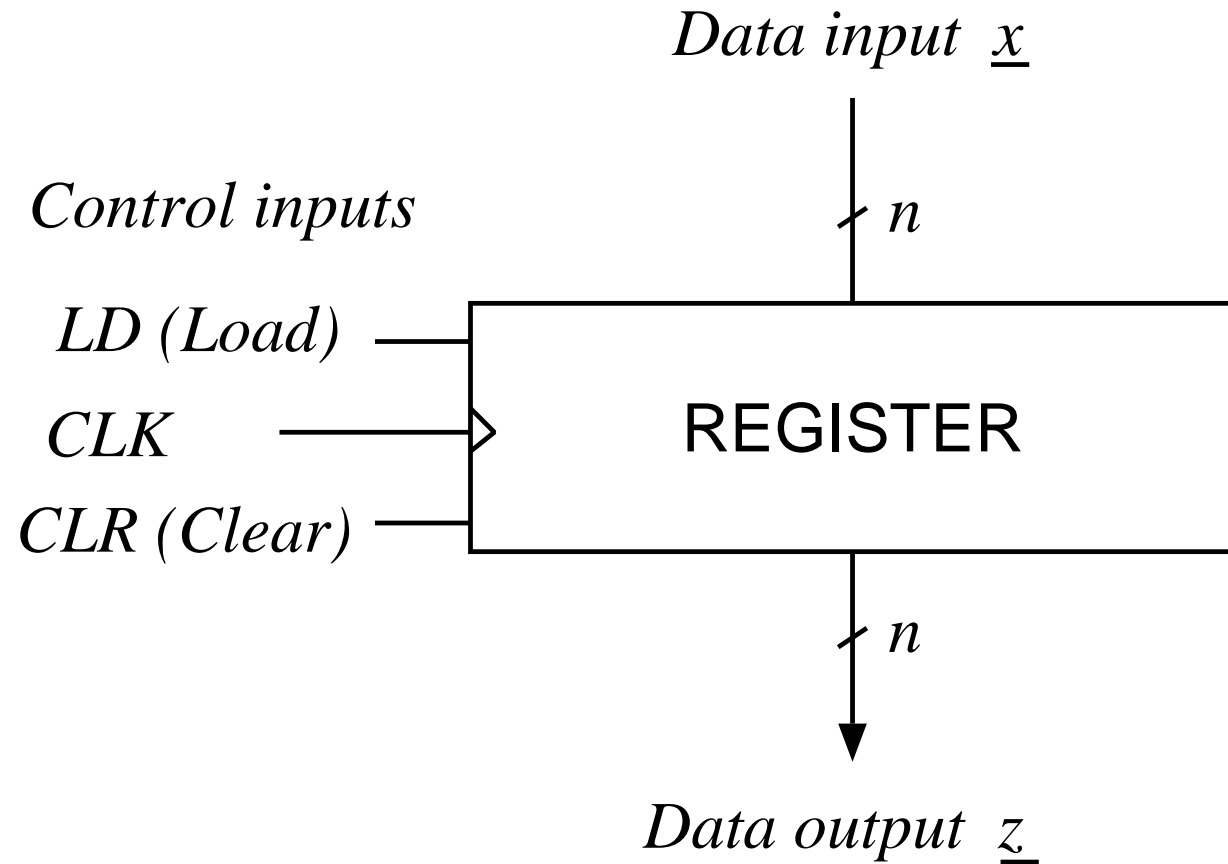


- REGISTERS
- SHIFT REGISTERS
- SYNCHRONOUS COUNTERS
- FOR EACH MODULE WE SHOW:
 - SPECIFICATION
 - IMPLEMENTATION WITH FF_s AND GATES
 - BASIC USES
 - HOW TO IMPLEMENT LARGER MODULES

Figure 11.1: n -BIT REGISTER MODULE

REGISTER: HIGH-LEVEL SPECIFICATION

3

INPUTS: $\underline{x} = (x_{n-1}, \dots, x_0), x_i \in \{0, 1\}$
 $LD, CLR \in \{0, 1\}$

OUTPUTS: $\underline{z} = (z_{n-1}, \dots, z_0), z_i \in \{0, 1\}$

STATE: $\underline{s} = (s_{n-1}, \dots, s_0), s_i \in \{0, 1\}$

FUNCTION: STATE TRANSITION AND OUTPUT FUNCTIONS

$$\underline{s}(t+1) = \begin{cases} \underline{x}(t) & \text{if } LD(t) = 1 \text{ and } CLR(t) = 0 \\ \underline{s}(t) & \text{if } LD(t) = 0 \text{ and } CLR(t) = 0 \\ (0 \dots 0) & \text{if } CLR(t) = 1 \end{cases}$$

$$\underline{z}(t) = \underline{s}(t)$$

IMPLEMENTATION OF 4-BIT REGISTER

 


Figure 11.2: IMPLEMENTATION OF 4-BIT REGISTER.

TIME-BEHAVIOR OF REGISTER

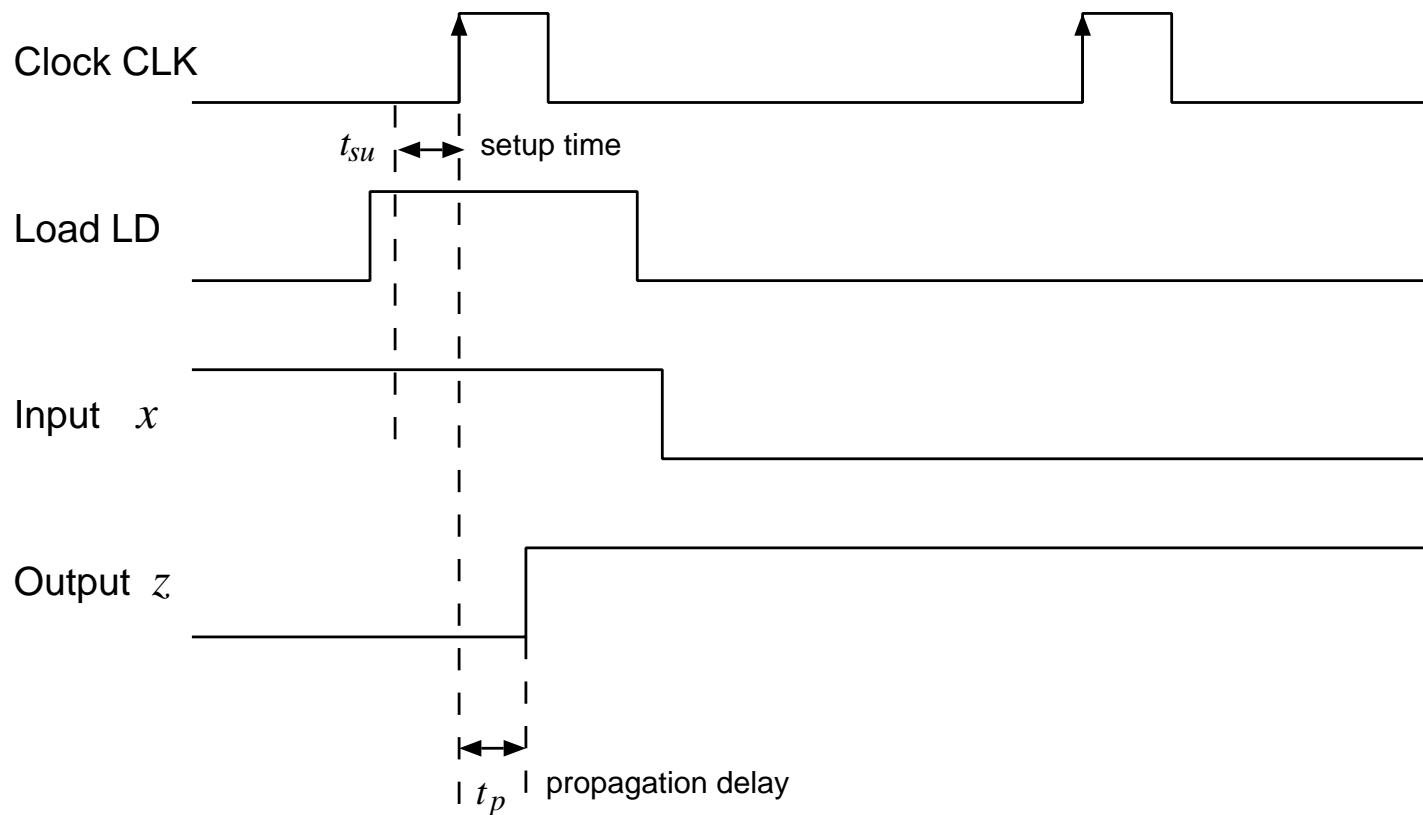


Figure 11.3: TIME-BEHAVIOR OF REGISTER.

USES OF REGISTERS: Example 11.1

INPUT: $x \in \{0, 1\}$
 OUTPUT: $(z_1, z_0), z_i \in \{0, 1\}$
 STATE: $(s_1, s_0), s_i \in \{0, 1\}$
 INITIAL STATE: $(s_1, s_0) = (0, 0)$

FUNCTION: STATE TRANSITION AND OUTPUT FUNCTIONS:

PS	Input	
	$x = 0$	$x = 1$
00	00	01
01	01	11
11	11	10
10	10	00
	NS	

$$z(t) = s(t)$$

CANONICAL IMPLEMENTATION

$$Y_1 = y_1x' + y_0x \quad Y_0 = y_0x' + y_1'x$$

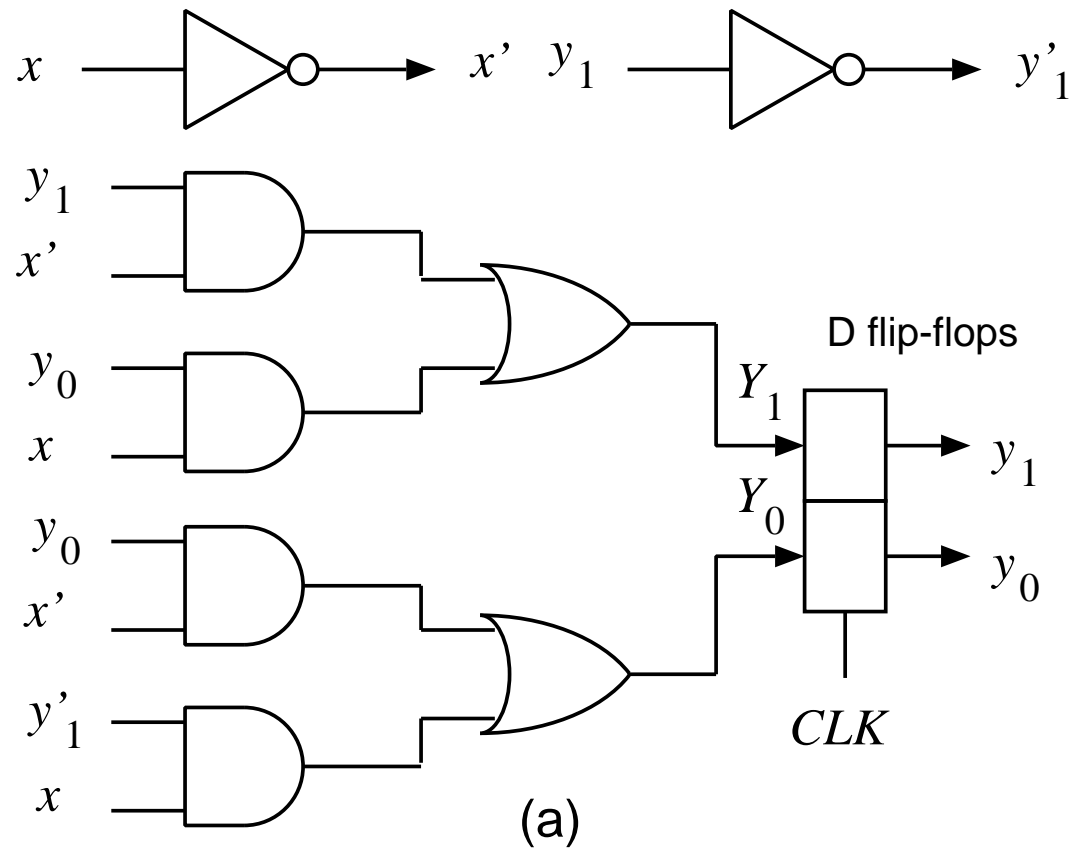


Figure 11.4: NETWORKS FOR Example 11.1: a) NETWORK WITH STATE CELLS;

IMPLEMENTATION WITH REGISTER

$$Y_1 = y_0 \quad Y_0 = y_1' \quad LD = x$$

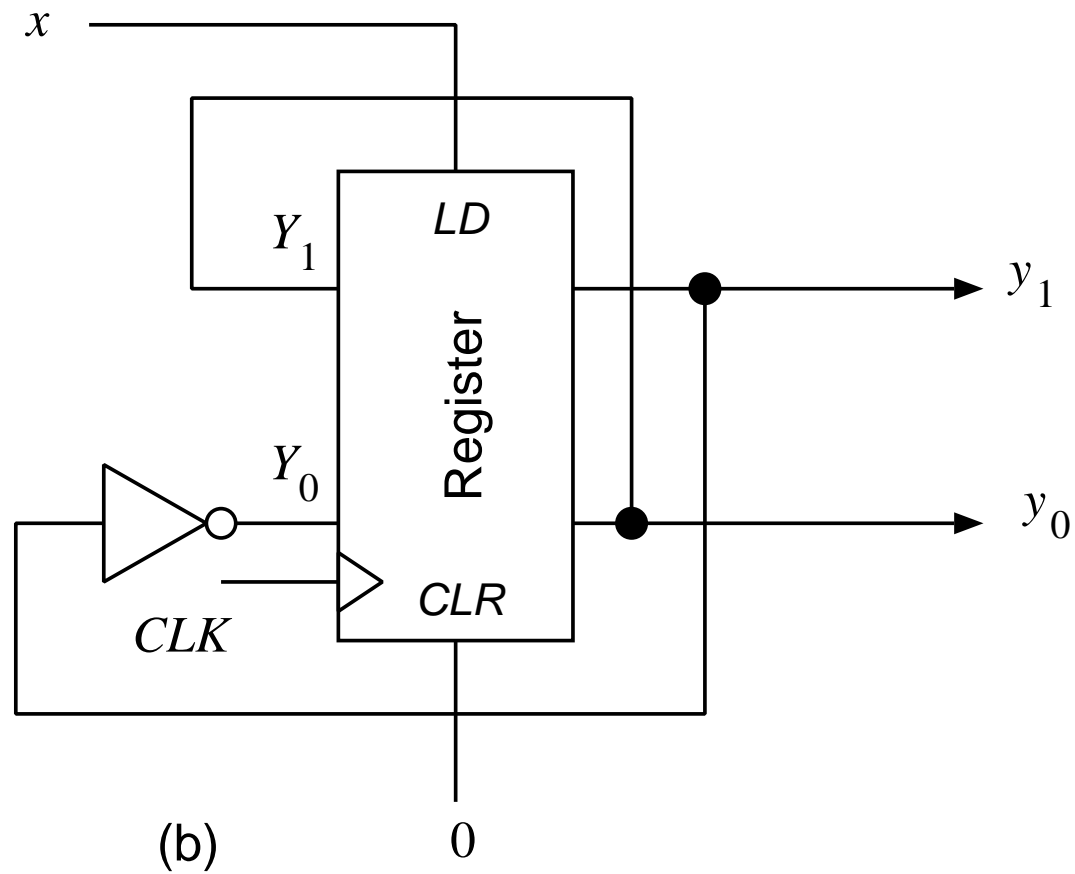


Figure 11.4: NETWORKS for Example 11.1: b) NETWORK WITH STANDARD REGISTER MODULE

SHIFT REGISTERS

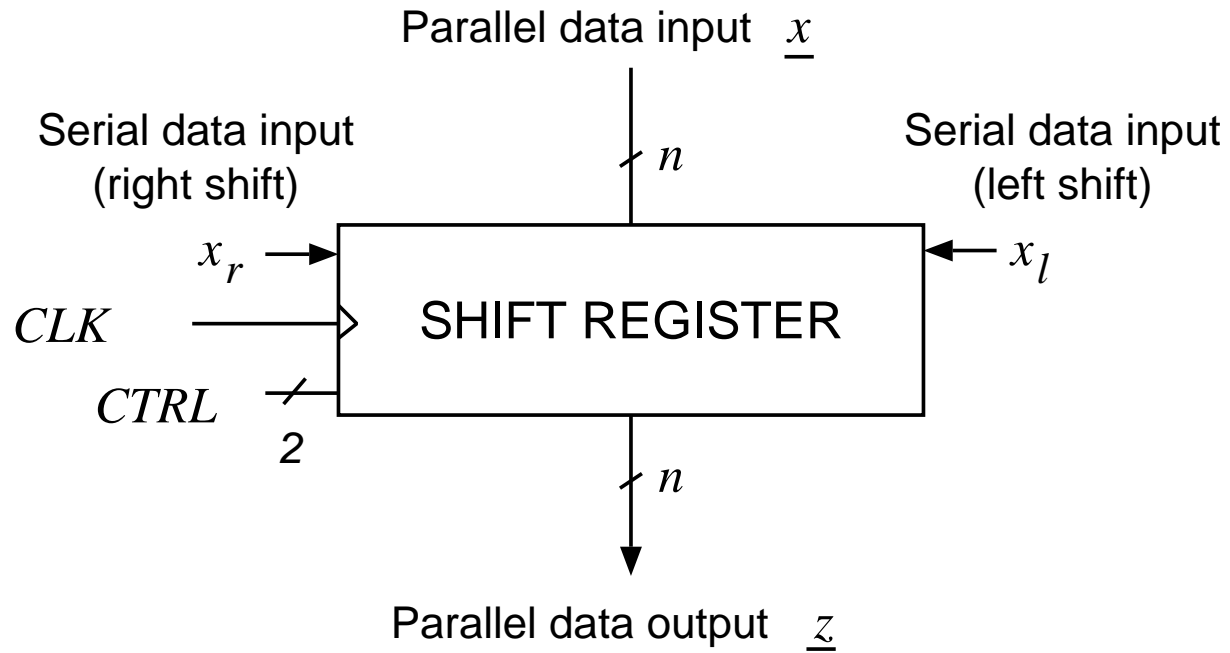


Figure 11.5: SHIFT REGISTER

PARALLEL-IN/PARALLEL-OUT BIDIRECTIONAL SHIFT REGISTER

 


Figure 11.6: PARALLEL-IN/PARALLEL-OUT BIDIRECTIONAL SHIFT REGISTER

INPUTS: $\underline{x} = (x_{n-1}, \dots, x_0), x_i \in \{0, 1\}$
 $x_l, x_r \in \{0, 1\}$
 $CTRL \in \{LOAD, LEFT, RIGHT, NONE\}$

STATE: $\underline{s} = (s_{n-1}, \dots, s_0), s_i \in \{0, 1\}$

OUTPUT: $\underline{z} = (z_{n-1}, \dots, z_0), z_i \in \{0, 1\}$

FUNCTIONS: STATE TRANSITION AND OUTPUT FUNCTIONS:

$$\underline{s}(t+1) = \begin{cases} \underline{s}(t) & \text{if } CTRL = NONE \\ \underline{x}(t) & \text{if } CTRL = LOAD \\ (s_{n-2}, \dots, s_0, x_l) & \text{if } CTRL = LEFT \\ (x_r, s_{n-1}, \dots, s_1) & \text{if } CTRL = RIGHT \end{cases}$$

$$\underline{z} = \underline{s}$$

SHIFT REGISTER CONTROL

Control		$s(t + 1) = z(t + 1)$
<i>NONE</i>		0101
<i>LOAD</i>		1110
<i>LEFT</i>	$x_l = 0$	1010
<i>LEFT</i>	$x_l = 1$	1011
<i>RIGHT</i>	$x_r = 0$	0010
<i>RIGHT</i>	$x_r = 1$	1010

<i>CTRL</i>	c_1	c_0
<i>NONE</i>	0	0
<i>LEFT</i>	0	1
<i>RIGHT</i>	1	0
<i>LOAD</i>	1	1

4-BIT BIDIRECTIONAL SHIFT-REGISTER

 


Figure 11.7: IMPLEMENTATION OF A 4-BIT BIDIRECTIONAL SHIFT REGISTER WITH D FLIP-FLOPS.

SERIAL-IN/SERIAL-OUT UNIDIRECTIONAL SHIFT REGISTER

$$z(t) = x(t - n)$$


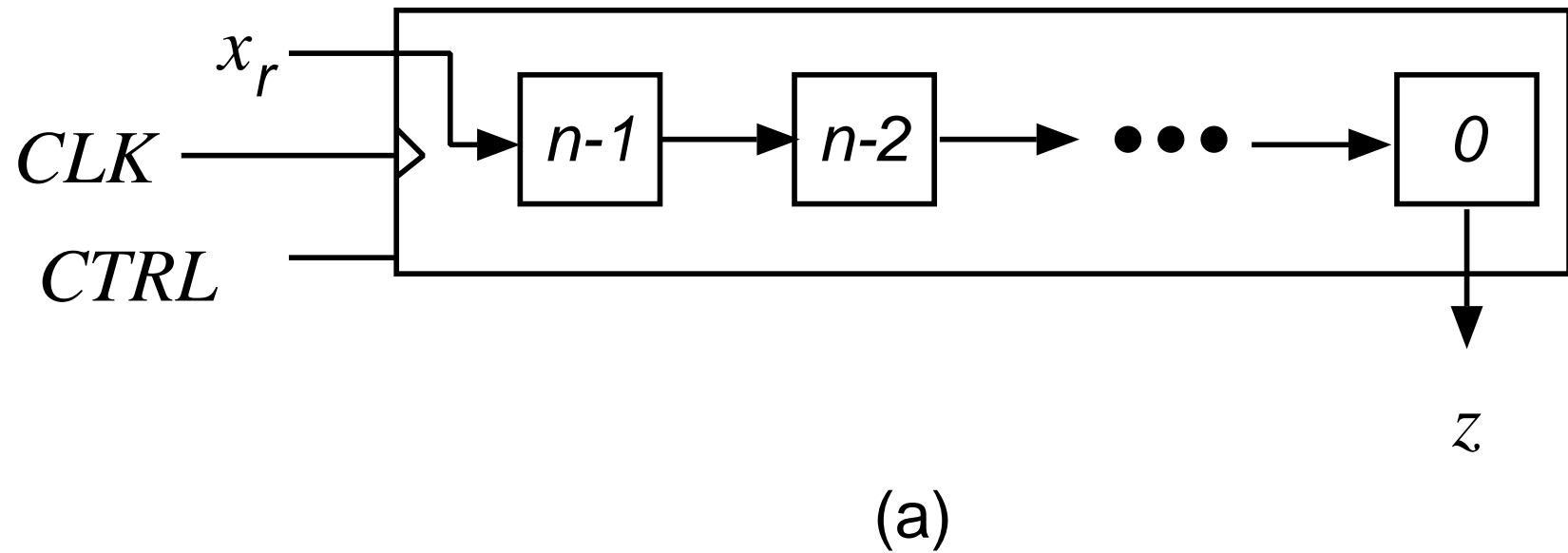


Figure 11.8: COMMON UNIDIRECTIONAL SHIFT REGISTERS: a) SERIAL-IN/SERIAL-OUT

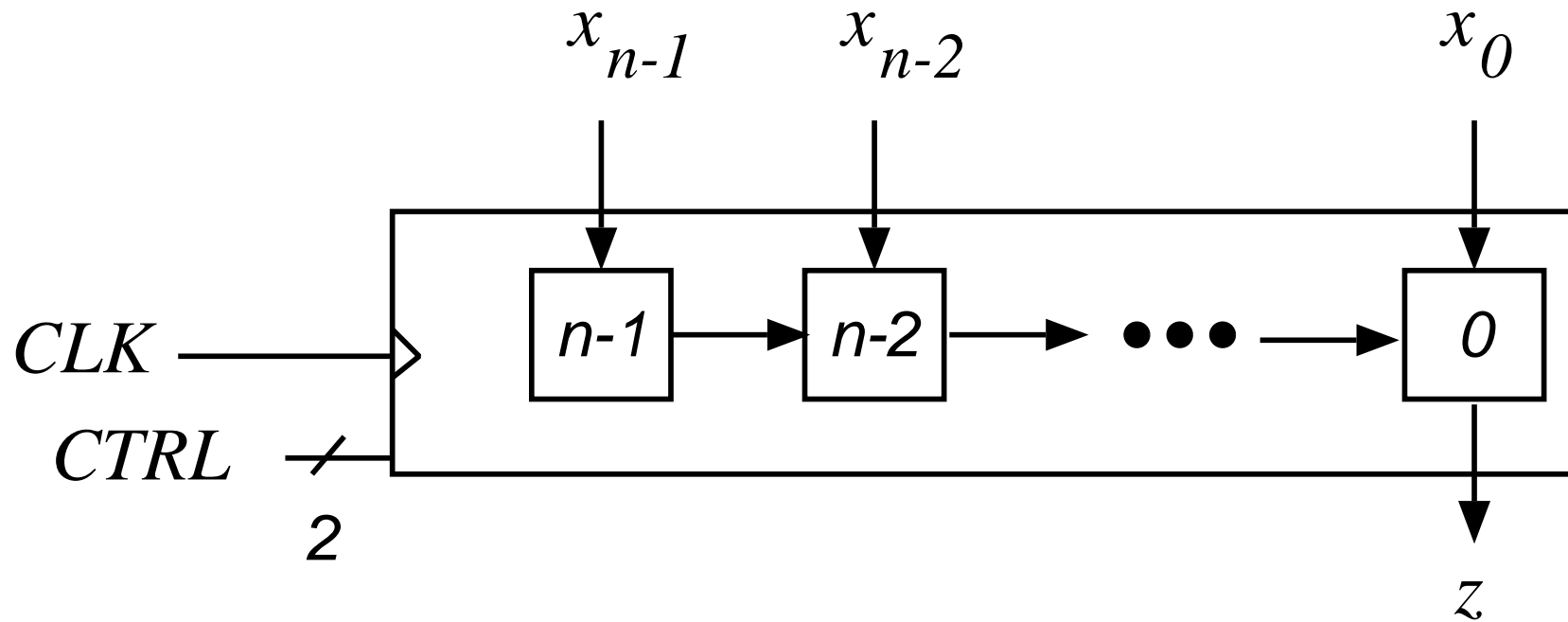PARALLEL-IN/SERIAL-OUT UNIDIRECTIONAL SHIFT REGISTER



(b)

Figure 11.8: COMMON UNIDIRECTIONAL SHIFT REGISTERS: b) PARALLEL-IN/SERIAL-OUT

SERIAL-IN/PARALLEL-OUT UNIDIRECTIONAL SHIFT REGISTER

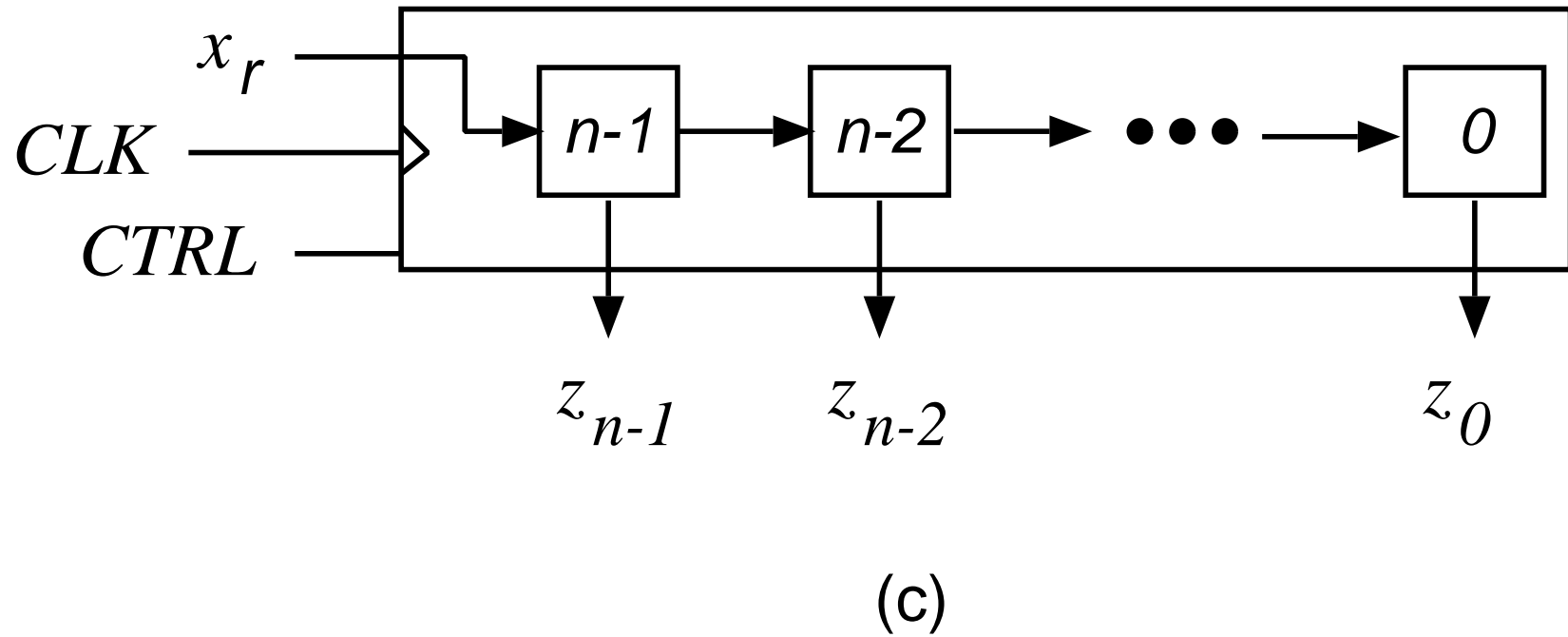


Figure 11.8: COMMON UNIDIRECTIONAL SHIFT REGISTERS: c) SERIAL-IN/PARALLEL-OUT

SUMMARY OF SHIFT-REGISTER TYPES

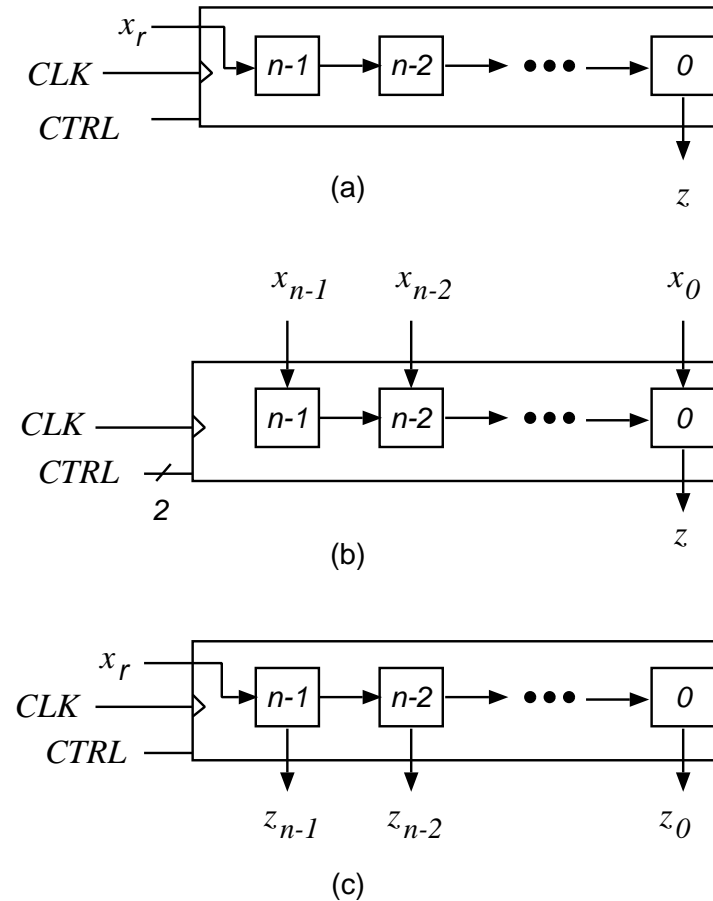


Figure 11.8: COMMON UNIDIRECTIONAL SHIFT REGISTERS: a) SERIAL-IN/SERIAL-OUT; b) PARALLEL-IN/SERIAL-OUT; c) SERIAL-IN/PARALLEL-OUT

- SERIAL INTERCONNECTION OF SYSTEMS

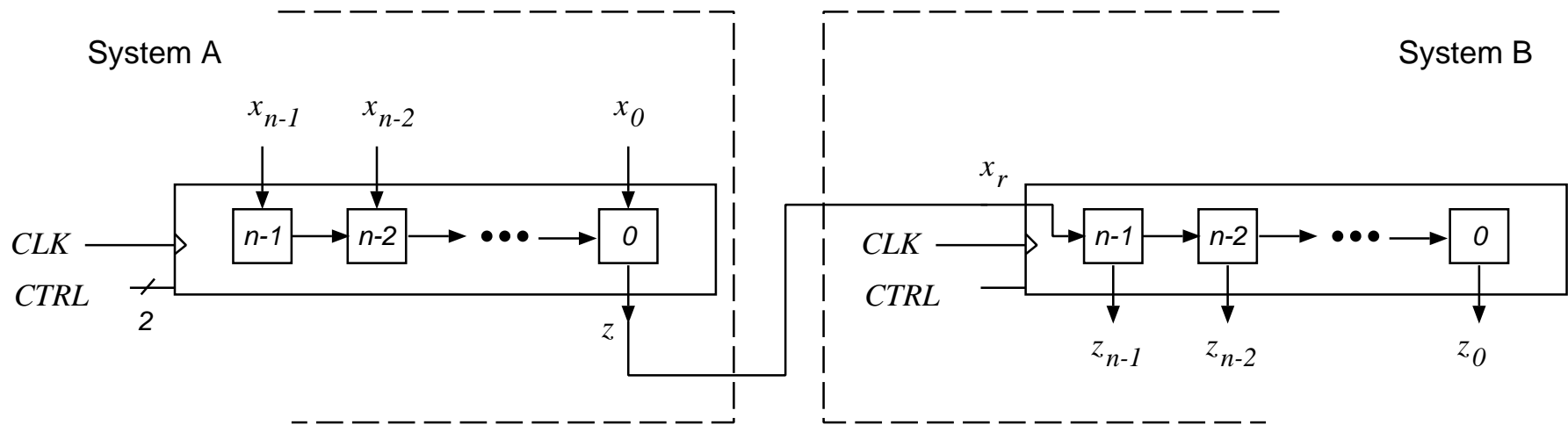


Figure 11.9: SERIAL INTERCONNECTION OF SYSTEMS USING SHIFT REGISTERS

- BIT-SERIAL OPERATIONS

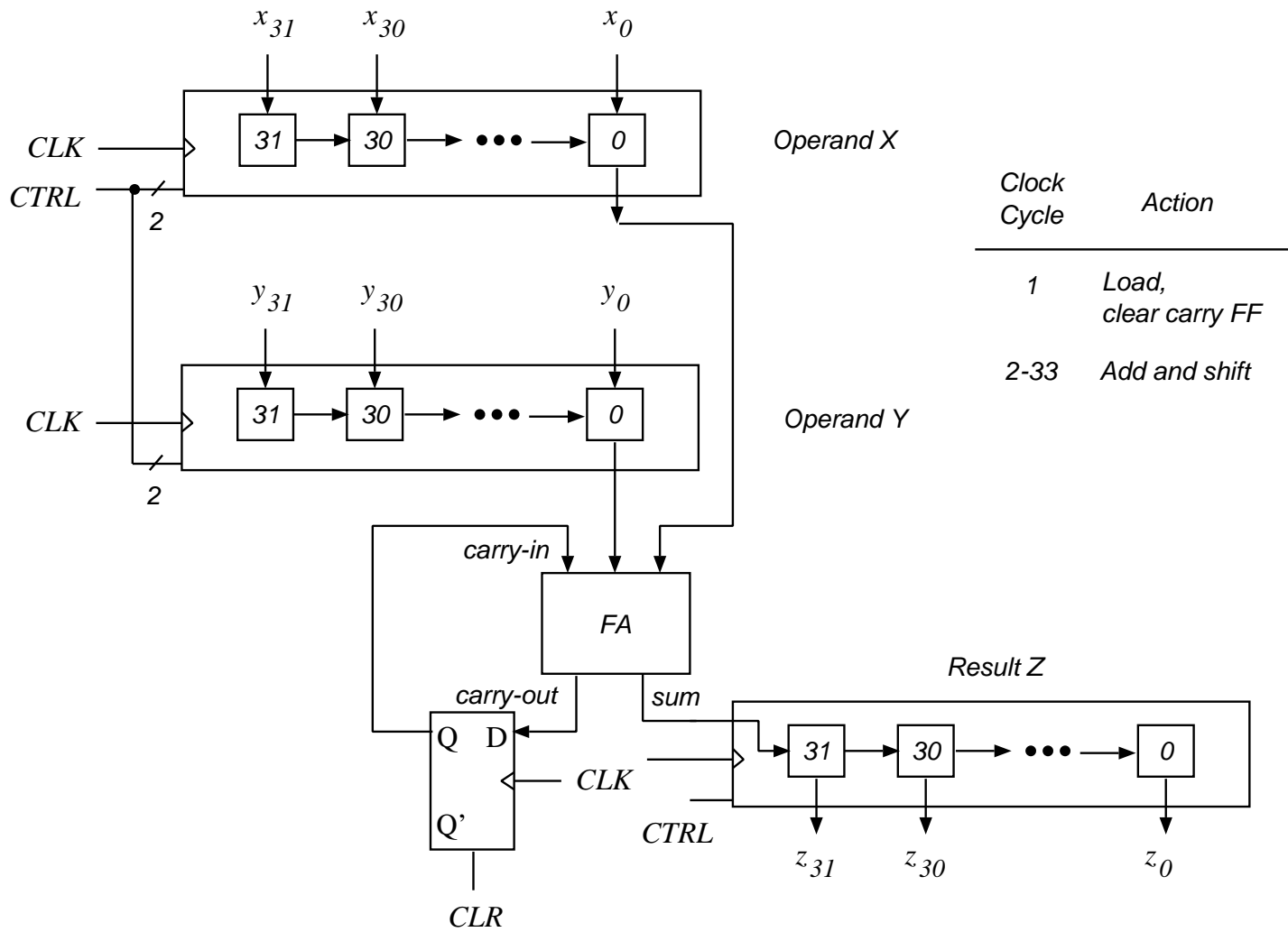


Figure 11.10: BIT-SERIAL ADDER.

USES OF SHIFT REGISTERS: STATE REGISTER

$$\begin{aligned} s_{n-1}(t+1) &= x(t) \\ s_i(t+1) &= s_{i+1}(t) \quad \mathbf{for} \quad i = n-2, \dots, 0 \end{aligned}$$

- FINITE-MEMORY SEQUENTIAL SYSTEM

Example 11.2: SHIFT REGISTER AS STATE REGISTER

$$s_7(t+1) = x(t)$$

$$s_i(t+1) = s_{i+1}(t) \quad \text{for } i = 6, \dots, 0$$

$$z(t) = x(t)s_0(t)$$

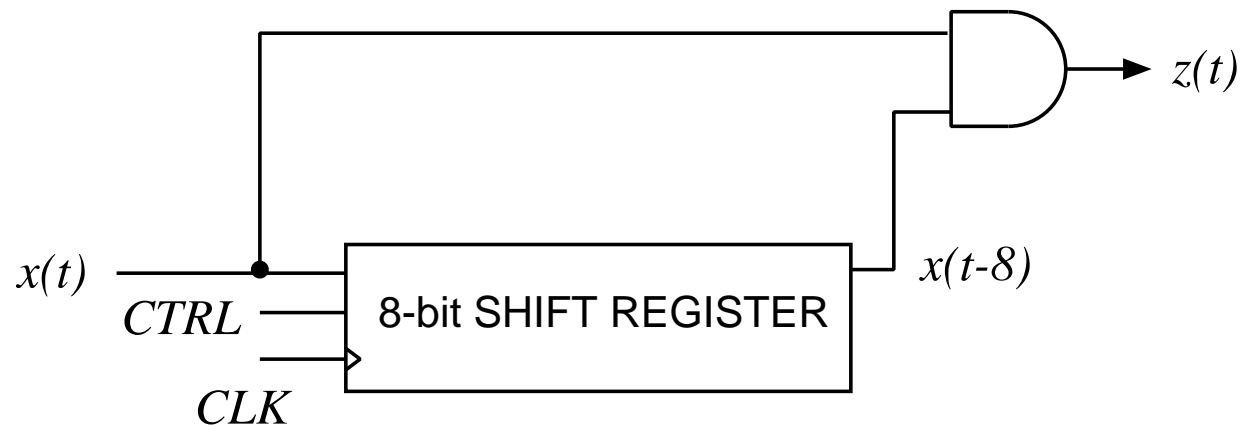


Figure 11.11: IMPLEMENTATION OF NETWORK IN Example 11.2

Example 11.3: SHIFT REGISTER AS STATE REGISTER

$$z(t) = \begin{cases} 1 & \text{if } \underline{s}(t) = 01101110 \text{ and } x(t) = 1 \\ 0 & \text{otherwise} \end{cases}$$

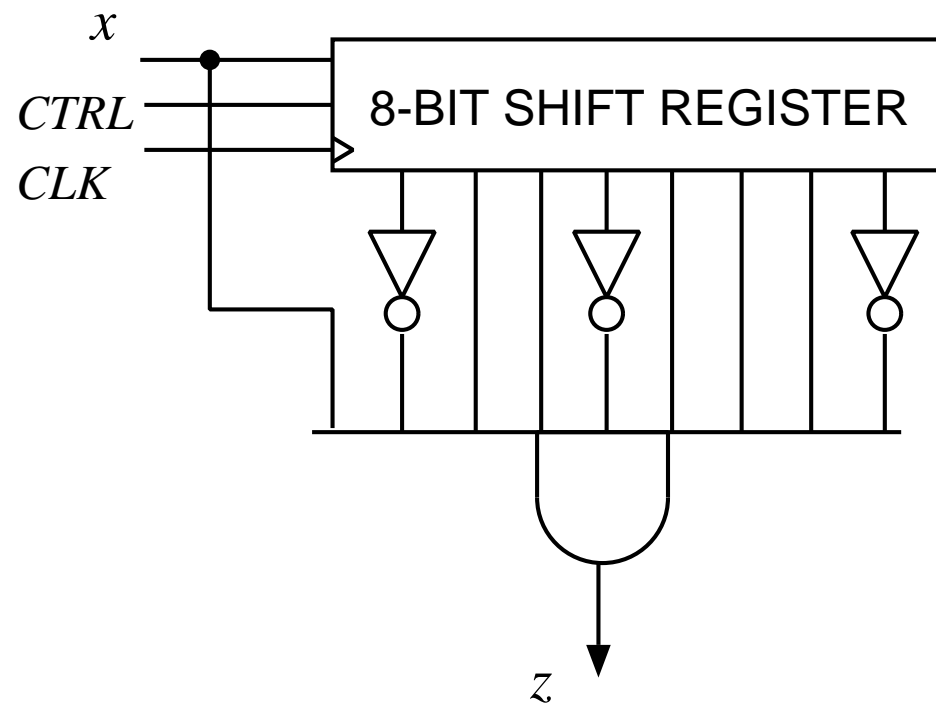


Figure 11.12: IMPLEMENTATION OF NETWORK IN Example 11.3

NETWORKS OF SHIFT REGISTERS

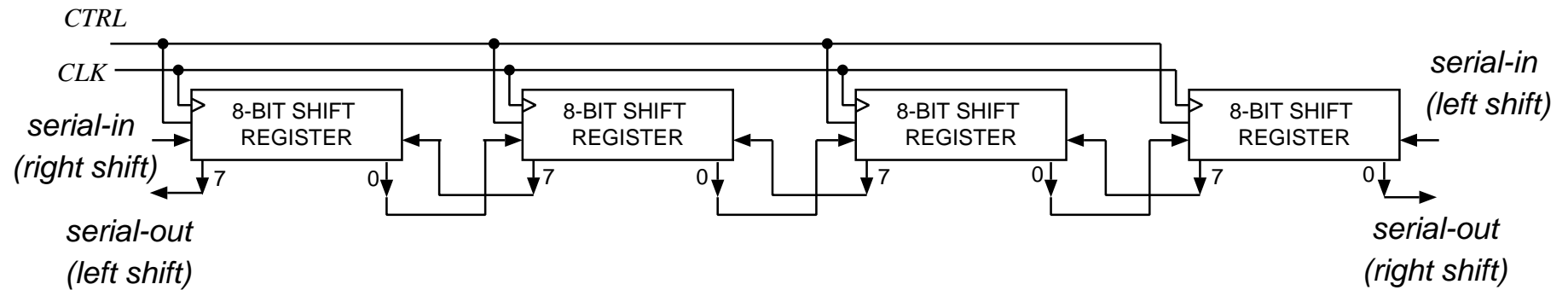


Figure 11.13: NETWORK OF SERIAL-INPUT/SERIAL-OUTPUT SHIFT REGISTER MODULES

- MODULO- p COUNTER

$$s(t + 1) = (s(t) + x) \bmod p$$

 


Figure 11.14: STATE DIAGRAM OF A MODULO- p COUNTER

A HIGH-LEVEL DESCRIPTION OF A MODULO- p COUNTER

INPUT: $x \in \{0, 1\}$
 OUTPUTS: $z \in \{0, 1, \dots, p - 1\}$
 $TC \in \{0, 1\}$
 STATE: $s \in \{0, 1, \dots, p - 1\}$

FUNCTION: STATE TRANSITION AND OUTPUT FUNCTIONS

$$\begin{aligned}
 s(t + 1) &= (s(t) + x) \bmod p \\
 z(t) &= s(t) \\
 TC(t) &= \begin{cases} 1 & \text{if } s(t) = p - 1 \text{ and } x(t) = 1 \\ 0 & \text{otherwise} \end{cases}
 \end{aligned}$$

TYPES OF COUNTERS

- UP or DOWN COUNTERS

State	Binary	BCD	Excess-3	Gray	Ring	Twisted Tail
0	000	0000	0011	000	00000001	0000
1	001	0001	0100	001	00000010	0001
2	010	0010	0101	011	00000100	0011
3	011	0011	0110	010	00001000	0111
4	100	0100	0111	110	00010000	1111
5	101	0101	1000	111	00100000	1110
6	110	0110	1001	101	01000000	1100
7	111	0111	1010	100	10000000	1000
8		1000	1011			
9		1001	1100			

RING and TWISTED-TAIL COUNTERS

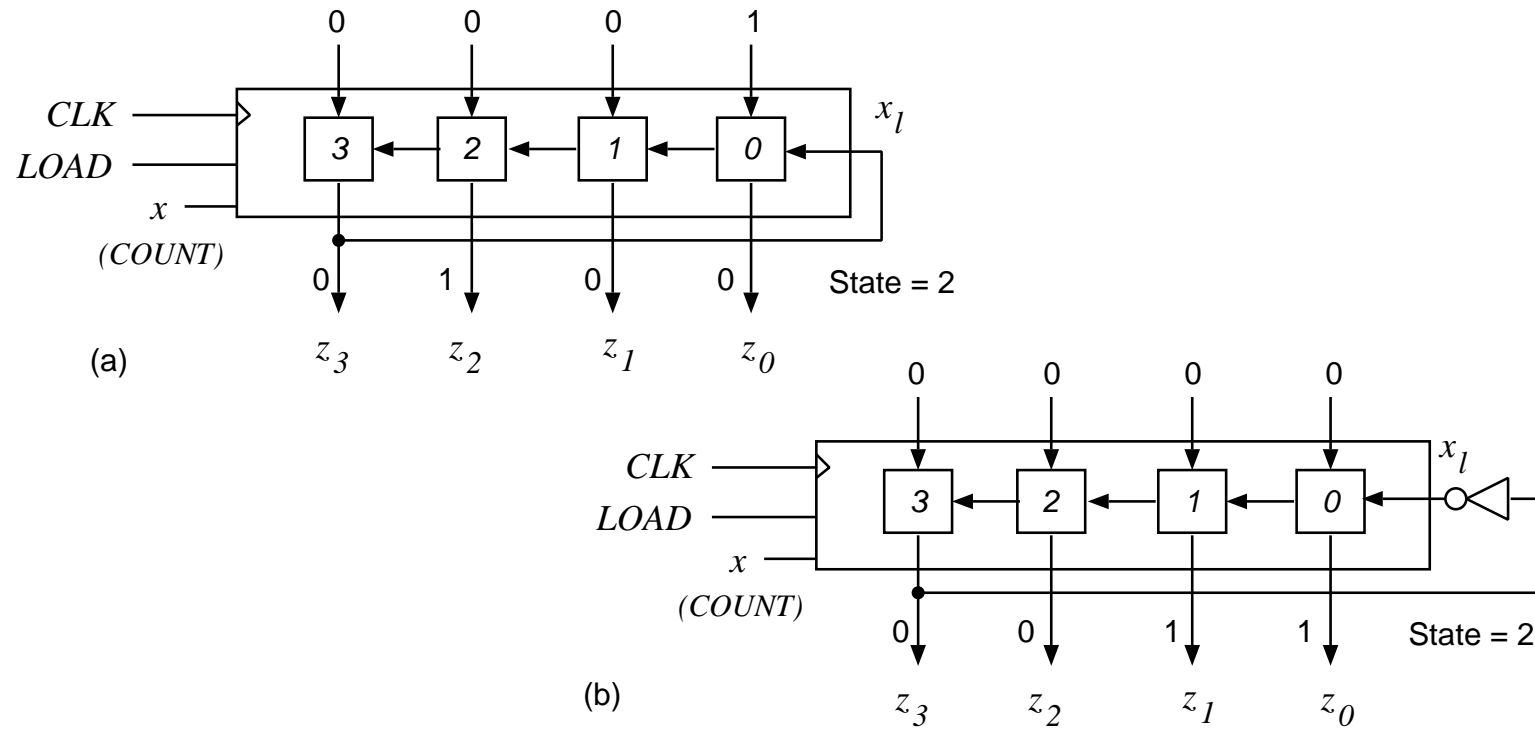


Figure 11.15: a) MODULO-4 RING COUNTER; b) MODULO-8 TWISTED-TAIL COUNTER

BINARY COUNTER WITH PARALLEL INPUT

INPUTS: $\underline{I} = (I_3, \dots, I_0), I_j \in \{0, 1\}, I \in \{0, 1, \dots, 15\}$
 $CLR, LD, CNT \in \{0, 1\}$

STATE: $\underline{s} = (s_3, \dots, s_0), s_j \in \{0, 1\}, s \in \{0, 1, \dots, 15\}$

OUTPUT: $\underline{s} = (s_3, \dots, s_0), s_j \in \{0, 1\}, s \in \{0, 1, \dots, 15\}$
 $TC \in \{0, 1\}$

FUNCTION: STATE-TRANSITION AND OUTPUT FUNCTIONS

$$s(t+1) = \begin{cases} 0 & \text{if } CLR = 1 \\ I & \text{if } LD = 1 \\ (s(t) + 1) \bmod 16 & \text{if } CNT = 1 \text{ and } LD = 0 \\ s(t) & \text{otherwise} \end{cases}$$

$$TC = \begin{cases} 1 & \text{if } s(t) = 15 \text{ and } CNT = 1 \\ 0 & \text{otherwise} \end{cases}$$

MODULO-16 COUNTER

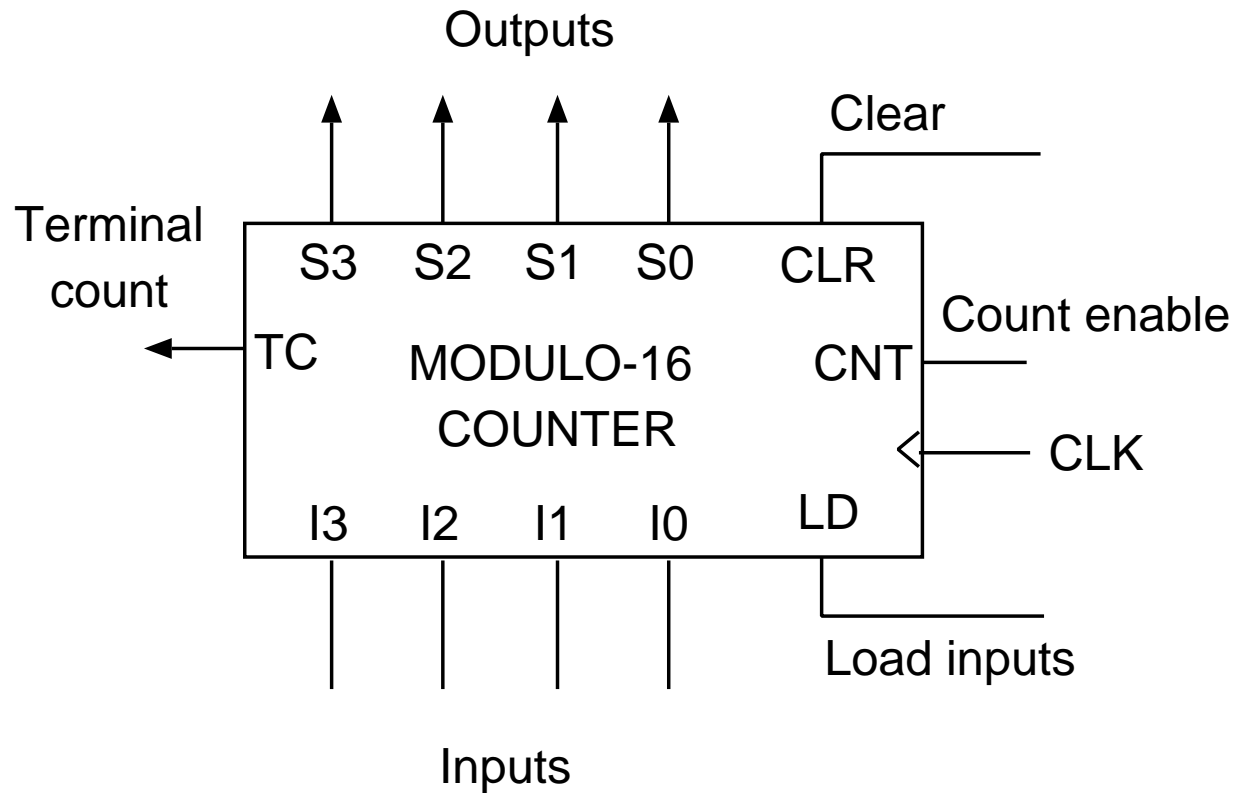


Figure 11.16: A MODULO-16 BINARY COUNTER WITH PARALLEL INPUT

MODULO- k COUNTER ($1 \leq k \leq 16$)

$$CNT = x$$

$$LD = \begin{cases} 1 & \text{if } (s = k - 1) \text{ and } (x = 1) \\ 0 & \text{otherwise} \end{cases}$$

$$I = 0$$

$$TC = LD$$

MODULO- k COUNTER ($1 \leq k \leq 16$)(cont.)

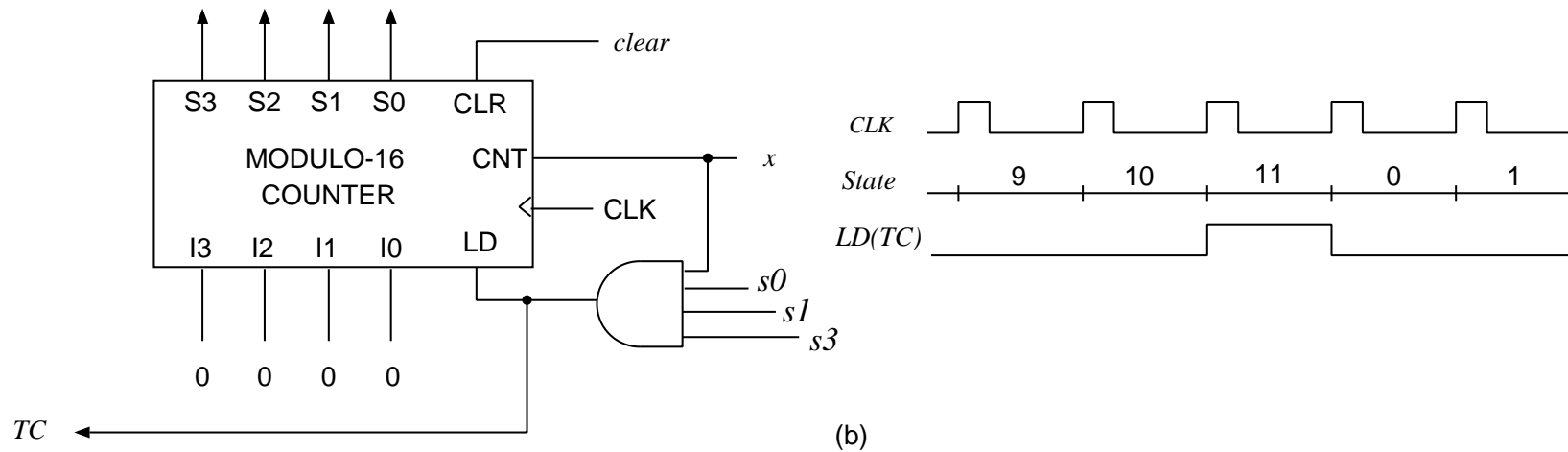
 


Figure 11.17: a) STATE DIAGRAM OF MODULO- k COUNTER ($1 \leq k \leq 16$); b) MODULO-12 COUNTER AND ITS TIME BEHAVIOR ($x = 1$)

a -to- b COUNTER ($0 \leq a, b \leq 15$)

$$CNT = x$$

$$LD = \begin{cases} 1 & \text{if } (s = b) \text{ and } (x = 1) \\ 0 & \text{otherwise} \end{cases}$$

$$I = a$$

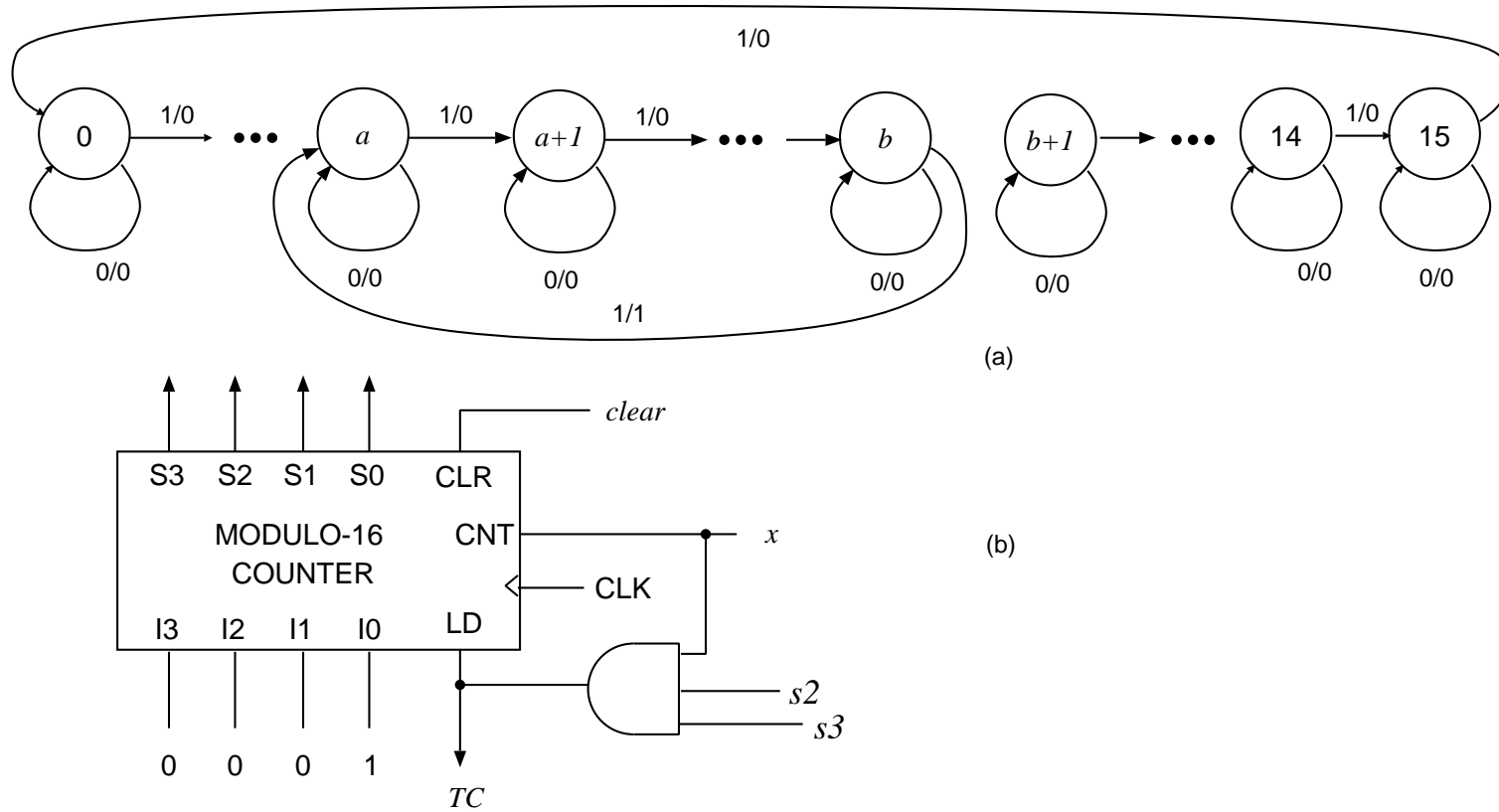


Figure 11.18: a) STATE DIAGRAM OF a -to- b COUNTER; b) A 1-to-12 COUNTER

MODULO- k FREQUENCY DIVIDER ($1 \leq k \leq 16$)

$$CNT = x$$

$$LD = \begin{cases} 1 & \text{if } TC = 1 \\ 0 & \text{otherwise} \end{cases}$$

$$I = 16 - k$$

$$z = TC$$


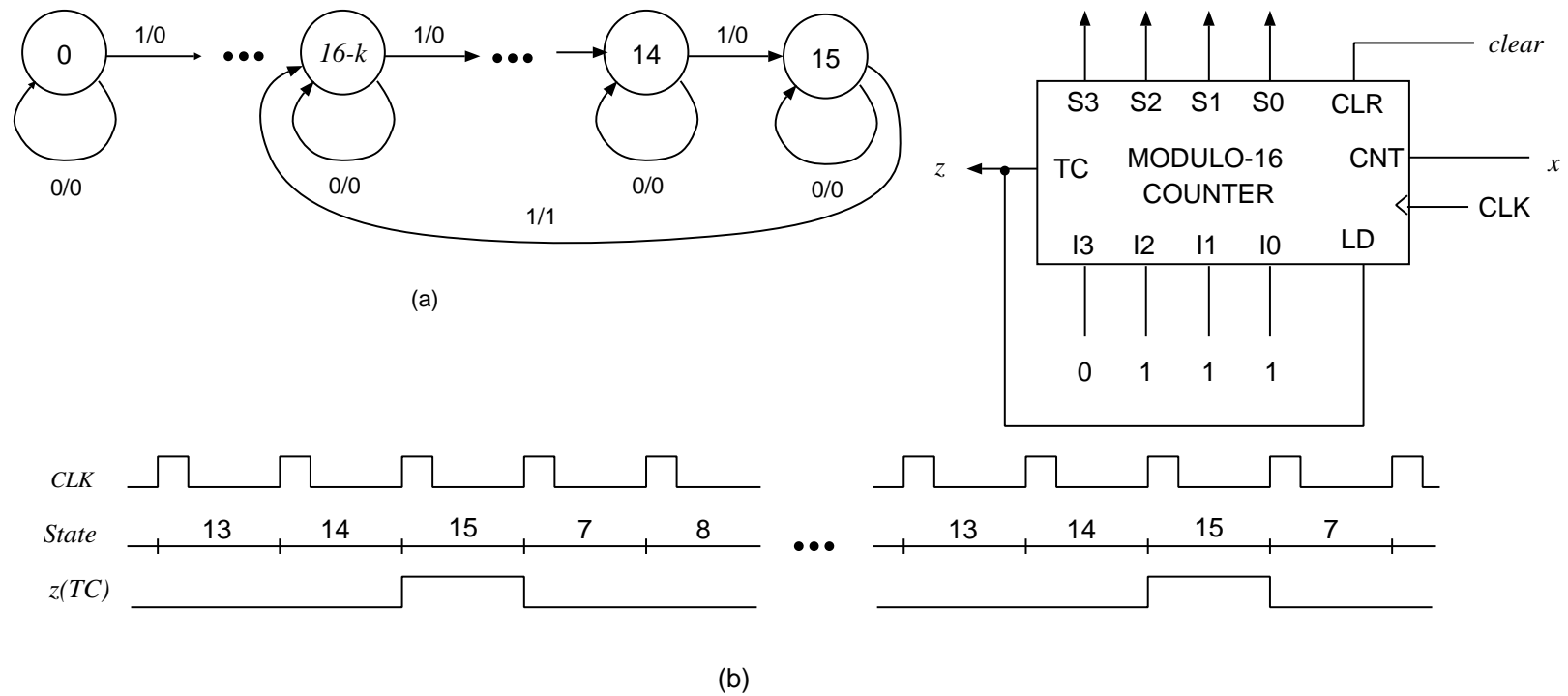


Figure 11.19: a) STATE DIAGRAM OF MODULO- k FREQUENCY DIVIDER; b) MODULO-9 FREQUENCY DIVIDER AND ITS TIME BEHAVIOR ($x = 1$)

USES OF COUNTERS

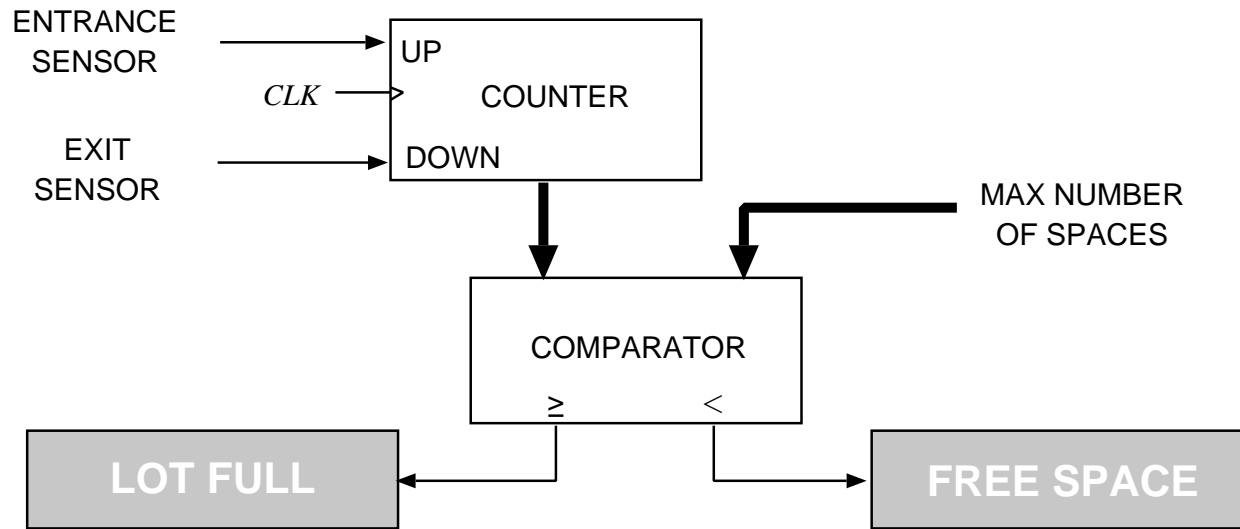
- COUNT THE NUMBER OF TIMES THAT A CERTAIN EVENT TAKES PLACE;
- CONTROL A FIXED SEQUENCE OF ACTIONS
- GENERATE TIMING SIGNALS
- GENERATE CLOCKS OF DIFFERENT FREQUENCIES
- STATE REGISTER



(a)

Sequence of actions:

 - 0: CLEAR ALL REGISTERS
- 1: INPUT A
- 2: INPUT B
- 3: COMPUTE
- 4: COMPUTE
- 5: OUTPUT C



(b)

Figure 11.20: a) EXAMPLE OF EVENT COUNTER; b) EXAMPLE OF CONTROLLER.

USES OF COUNTERS (cont.)

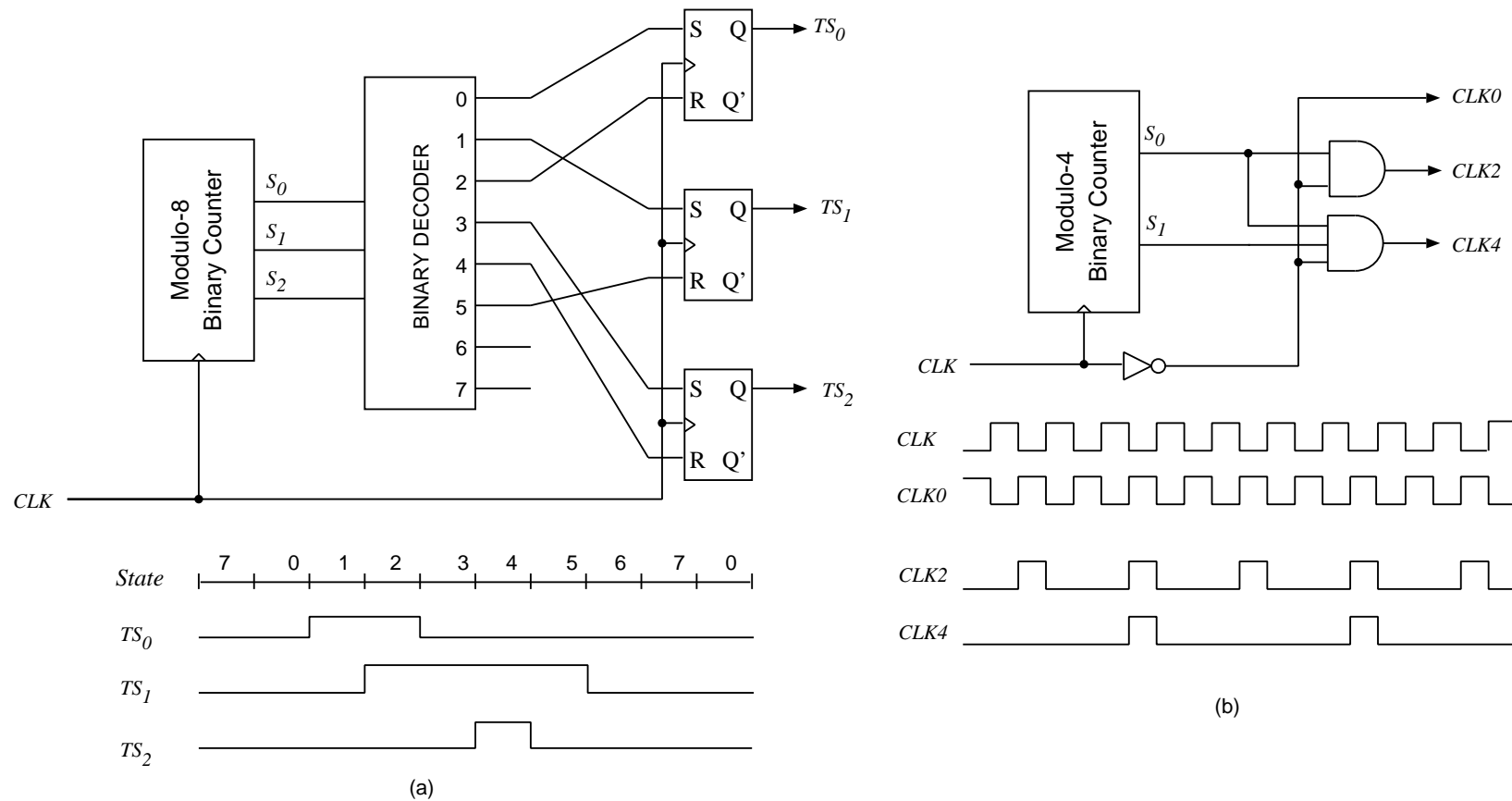


Figure 11.21: EXAMPLES OF NETWORKS FOR GENERATING a) TIMING SIGNALS; b) CLOCKS WITH DIFFERENT FREQUENCIES.

COUNTER AS STATE REGISTER

Counting $s(t + 1) = (s(t) + 1) \bmod p$
 No change $s(t + 1) = s(t)$
 Arbitrary $s(t + 1) \neq (s(t) + 1) \bmod p$ **and** $s(t + 1) \neq s(t)$

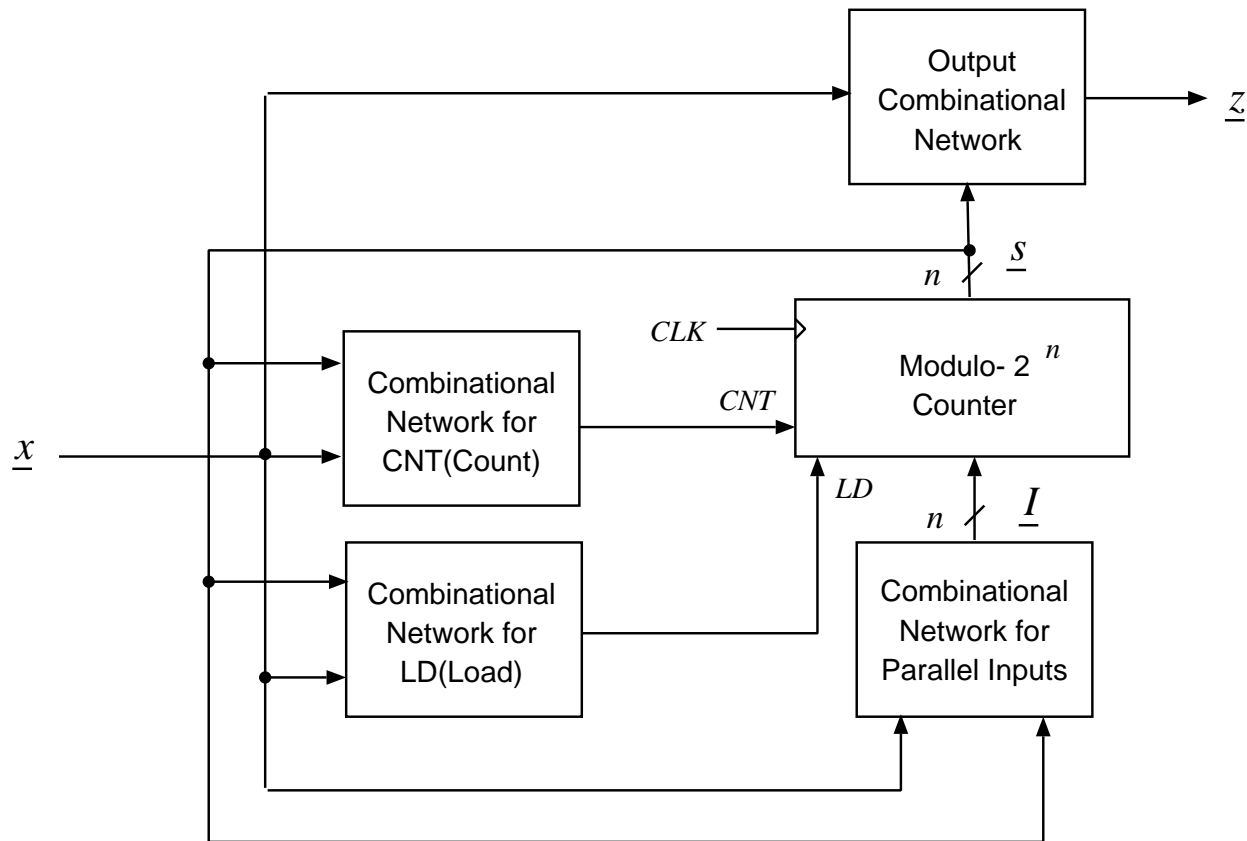


Figure 11.22: IMPLEMENTATION OF SEQUENTIAL SYSTEM WITH COUNTER AND COMBINATIONAL NETWORKS.

COUNTER AS STATE REGISTER (cont.)

$$CNT = \begin{cases} 1 & \text{if } s(t+1) = (s(t) + 1) \bmod p \text{ and } x = 1 \\ 0 & \text{otherwise} \end{cases}$$

$$LD = \begin{cases} 1 & \text{if } s(t+1) \neq s(t) \text{ and} \\ & s(t+1) \neq (s(t) + 1) \bmod p \text{ and } x = 1 \\ 0 & \text{otherwise} \end{cases}$$

$$I = \begin{cases} s(t+1) & \text{if } LD = 1 \\ - & \text{otherwise} \end{cases}$$

Example 11.4

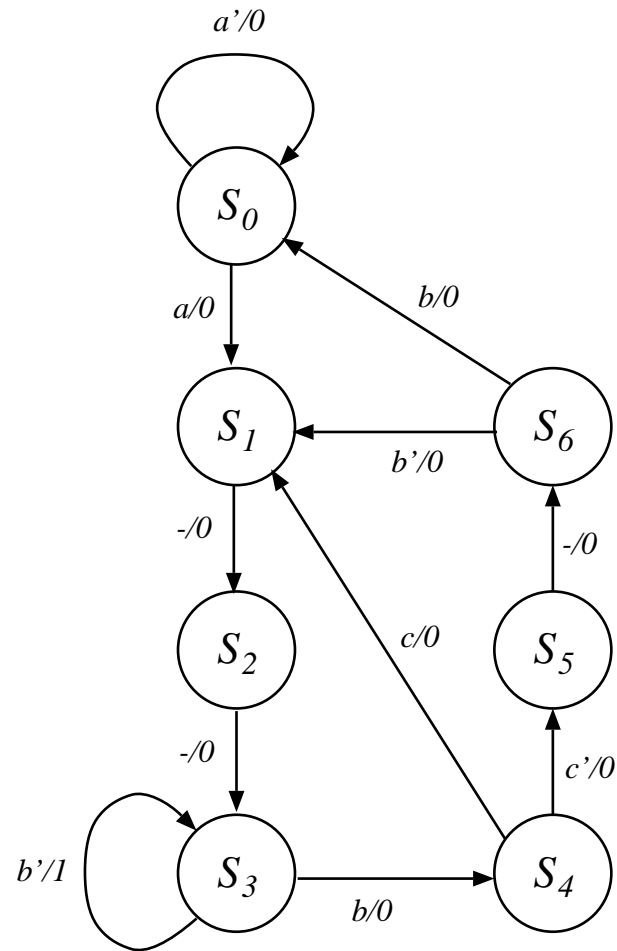


Figure 11.23: STATE DIAGRAM for Example 11.4

Example 11.4 (cont.)

$$CNT = S_0a + S_1 + S_2 + S_3b + S_4c' + S_5$$

$$LD = CNT'$$

$$(I_3, I_2, I_1, I_0) = \begin{cases} (0, 0, 0, 0) & \text{if } S_0a' + S_6b \\ (0, 0, 0, 1) & \text{if } S_4c + S_6b' \\ (0, 0, 1, 1) & \text{if } S_3b' \end{cases}$$

SWITCHING EXPRESSIONS FOR PARALLEL INPUTS

$$I_3 = 0$$

$$I_2 = 0$$

$$I_1 = Q_0$$

$$I_0 = Q_0 + Q_2Q_1' + Q_2b'$$

OUTPUT z

$$z = Q_1Q_0b'$$

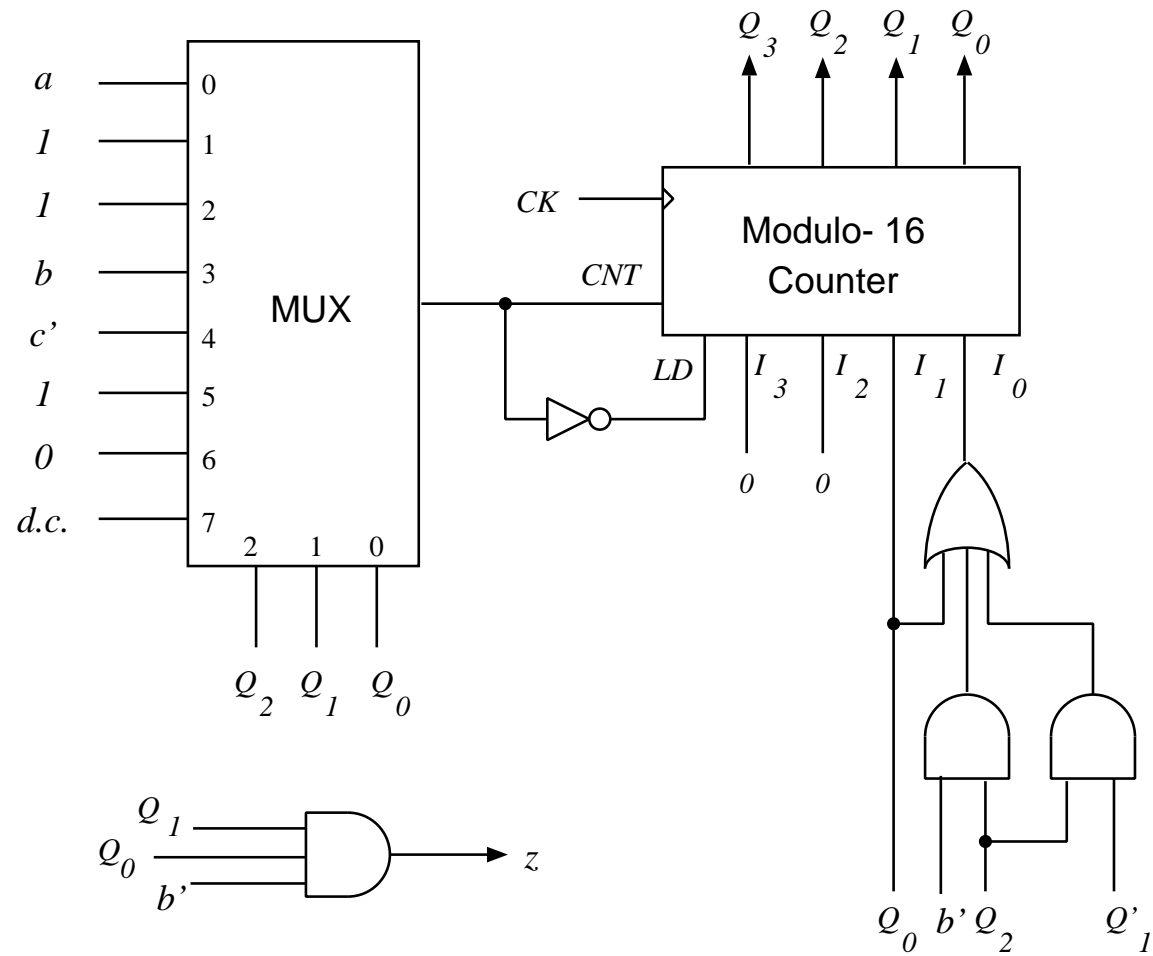


Figure 11.24: SEQUENTIAL NETWORK FOR Example 11.4

- CASCADE COUNTERS

$$TC = \begin{cases} 1 & \text{if } (s = p - 1) \text{ and } (CNT = 1) \\ 0 & \text{otherwise} \end{cases}$$

- FOR THE i -th MODULE

$$CNT^i = \begin{cases} 1 & \text{if } (s^{(j)} = p - 1) \text{ and } (x = 1) \\ & \text{(for all } j < i) \\ 0 & \text{otherwise} \end{cases}$$

where $s^{(j)}$ is the state of counter j .

CASCADE COUNTERS (cont.)

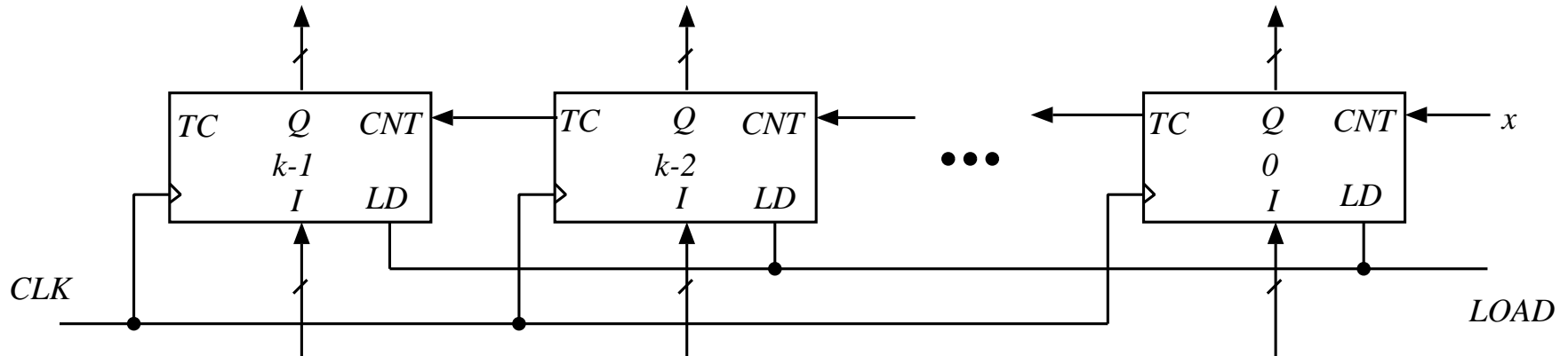


Figure 11.26: CASCADE IMPLEMENTATION OF A MODULO- p^k COUNTER

- THE WORST-CASE DELAY

$$T_{\text{worst-case}} = (k - 1)t_{tc} + t_{su} + t_p$$

- THE MAXIMUM CLOCK FREQUENCY POSSIBLE

$$f_{\text{max}} = 1/[(k - 1)t_{tc} + t_{su} + t_p]$$

Example 11.5

$$t_{su} = 4.5[ns] \text{ (including the delay of the gates used to produce the inputs to the cells)}$$

$$t_p = 2[ns]$$

$$t_{tc} = 3.5[ns]$$

MIN CLOCK PERIOD:

with one module $T = 6.5[ns]$ ($153[MHz]$)

with 8 modules $T = 31[ns]$ ($32[MHz]$)

FASTER COUNTERS

- INTRODUCE *CEF* (Count Enable First)

$$s(t + 1) = \begin{cases} (s(t) + 1) \bmod p & \text{if } CEF = 1 \text{ and } CNT = 1 \\ s(t) & \text{otherwise} \end{cases}$$

- *TC* SIGNAL NOT INFLUENCED BY *CEF*,

$$TC = \begin{cases} 1 & \text{if } (s(t) = p - 1) \text{ and } (CNT = 1) \\ 0 & \text{otherwise} \end{cases}$$

FASTER CASCADE COUNTER

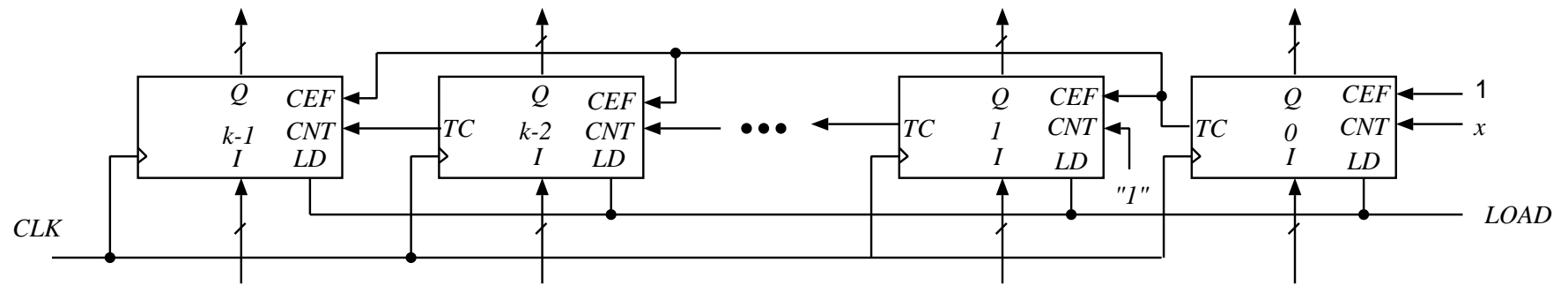


Figure 11.27: A FASTER VERSION OF A CASCADE COUNTER

WORST-CASE DELAY

$$T_{\text{worst-case}} = (k - 2)t_{tc} + t_{su} + t_p$$

⇒ SMALL REDUCTION IN THE DELAY

* Note: propagation of TC can span several clock cycles

CONSEQUENTLY, IF T IS THE CLOCK PERIOD,

$$pT \geq (k - 2)t_{tc} + t_{su} + t_p$$

$$T \geq t_{tc} + t_{su} + t_p$$

COMBINING

$$T \geq \max(t_{tc} + t_{su} + t_p, ((k - 2)t_{tc} + t_{su} + t_p)/p)$$

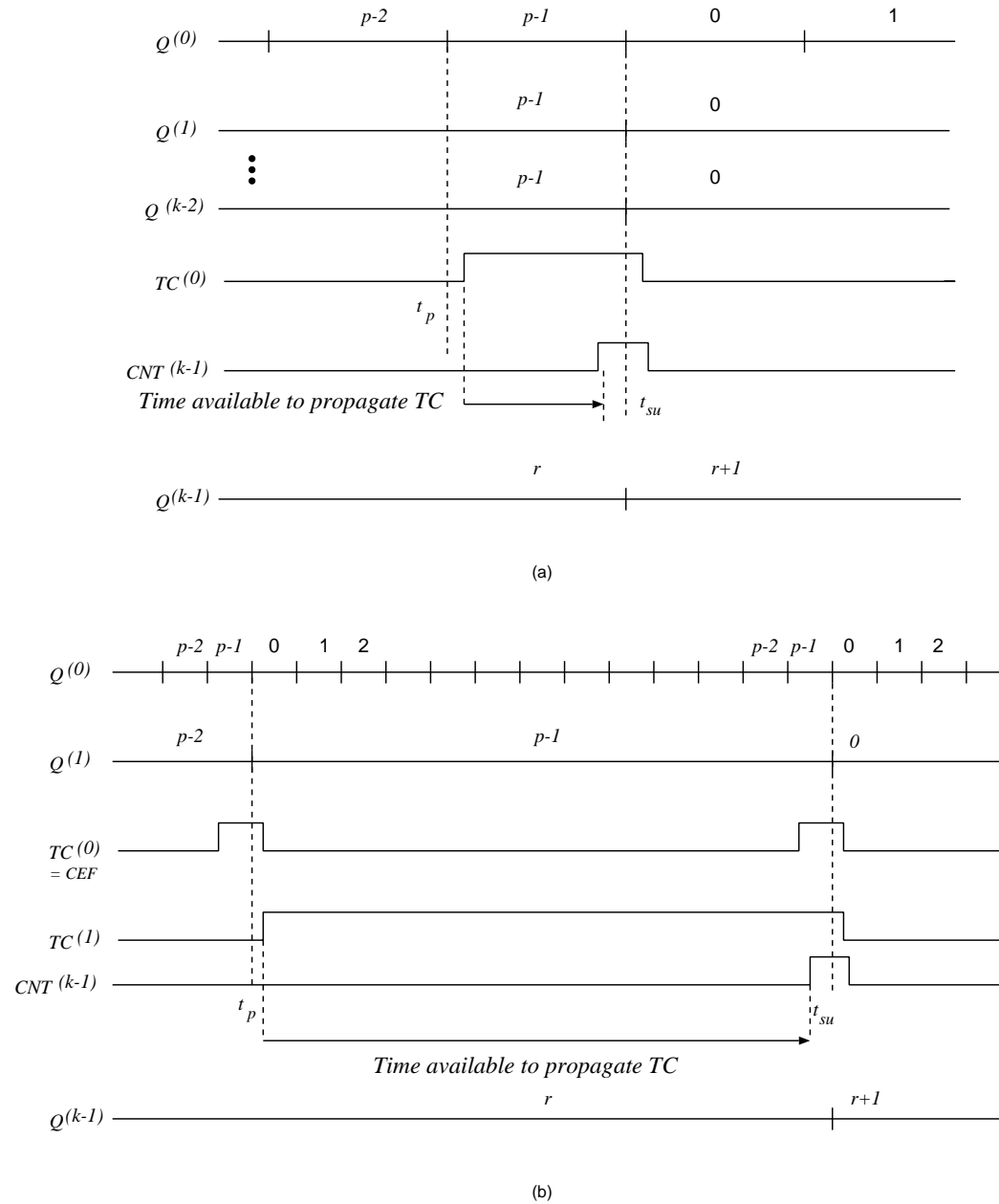


Figure 11.28: TIMING RELATIONS: a) Without *CEF*; b) With *CEF*

Modulo-504 counter: $7 \times 8 \times 9$ states

000, 111, 222, 333, 444, 555, 666, 077, 108, 210, 321, 432, ...

PARALLEL MODULO-($7 \times 8 \times 9$) COUNTER

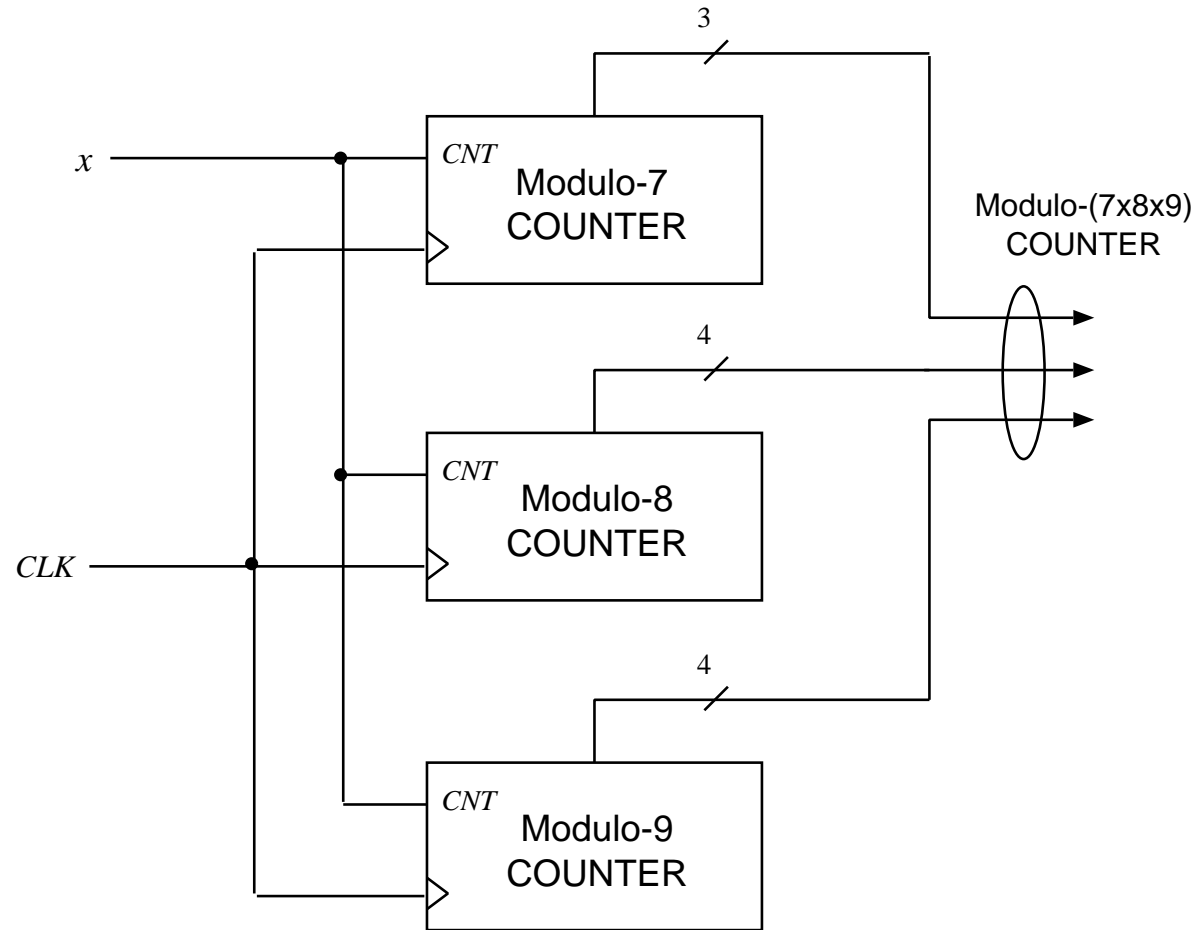


Figure 11.29: PARALLEL IMPLEMENTATION OF MODULO-($7 \times 8 \times 9$) COUNTER.


- Complex sequential system \Rightarrow several interacting sequential subsystems

Example 11.6: BLOCK PATTERN RECOGNIZER

- INPUT SEQUENCE: blocks of k symbols
- FUNCTION: check for pattern P in each block
- IMPLEMENTATION: counter + recognizer
- OUTPUT OF THE COUNTER:

$$TC(t) = \begin{cases} 1 & \text{if } t \bmod k = k - 1 \text{ and CHECK} = 1 \\ 0 & \text{otherwise} \end{cases}$$

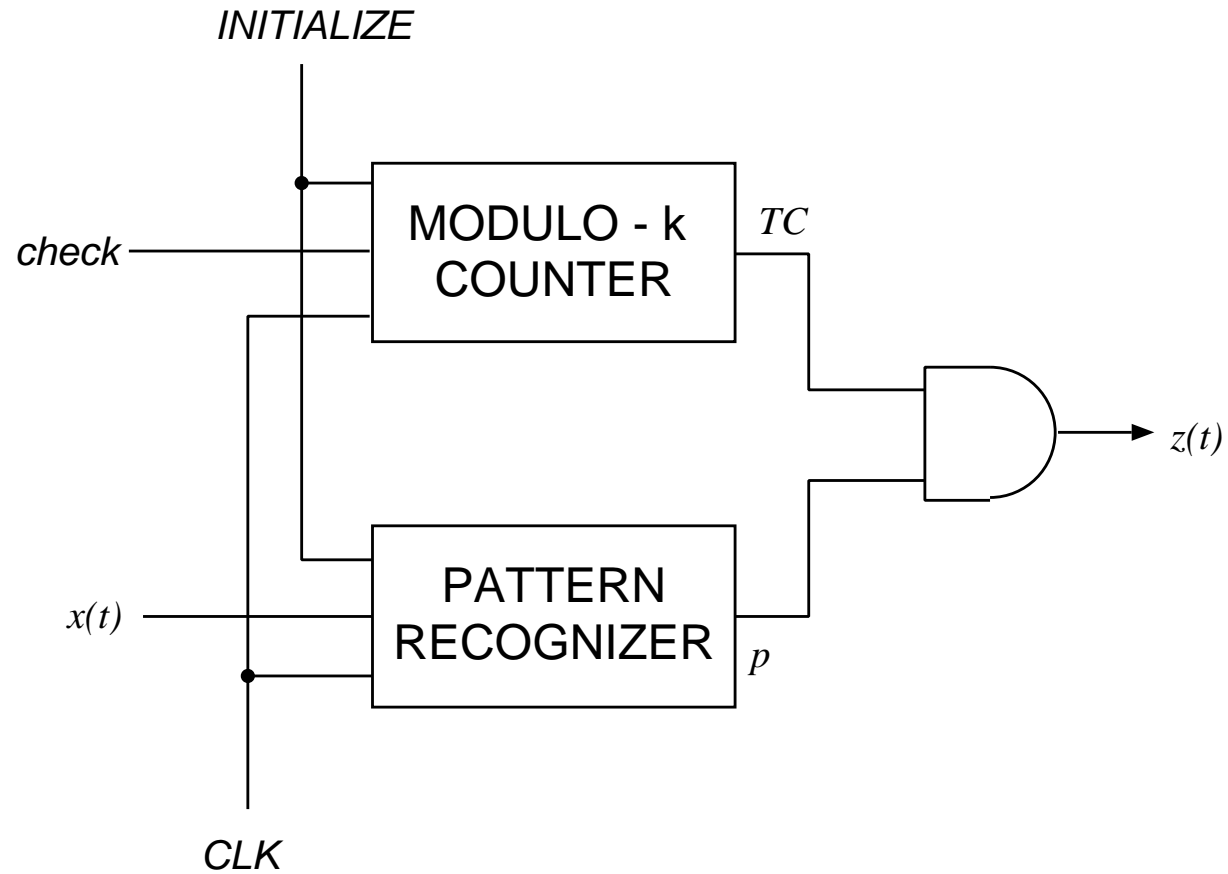- OUTPUT OF THE SYSTEM: $z(t) = p(t) \cdot TC(t)$



(a)

Figure 11.30: BLOCK PATTERN RECOGNIZER

Example 11.6: ILLUSTRATION

t	0	1	2	3	4	5	6	7	8	9	10	11
x	5	3	7	4	1	0	3	7	4	3	7	4
TC	0	0	1	0	0	1	0	0	1	0	0	1
p	0	0	0	1	0	0	0	0	1	0	0	1
z	0	0	0	0	0	0	0	0	1	0	0	1

Example 11.7

- count the number of instances of pattern P in blocks of k symbols

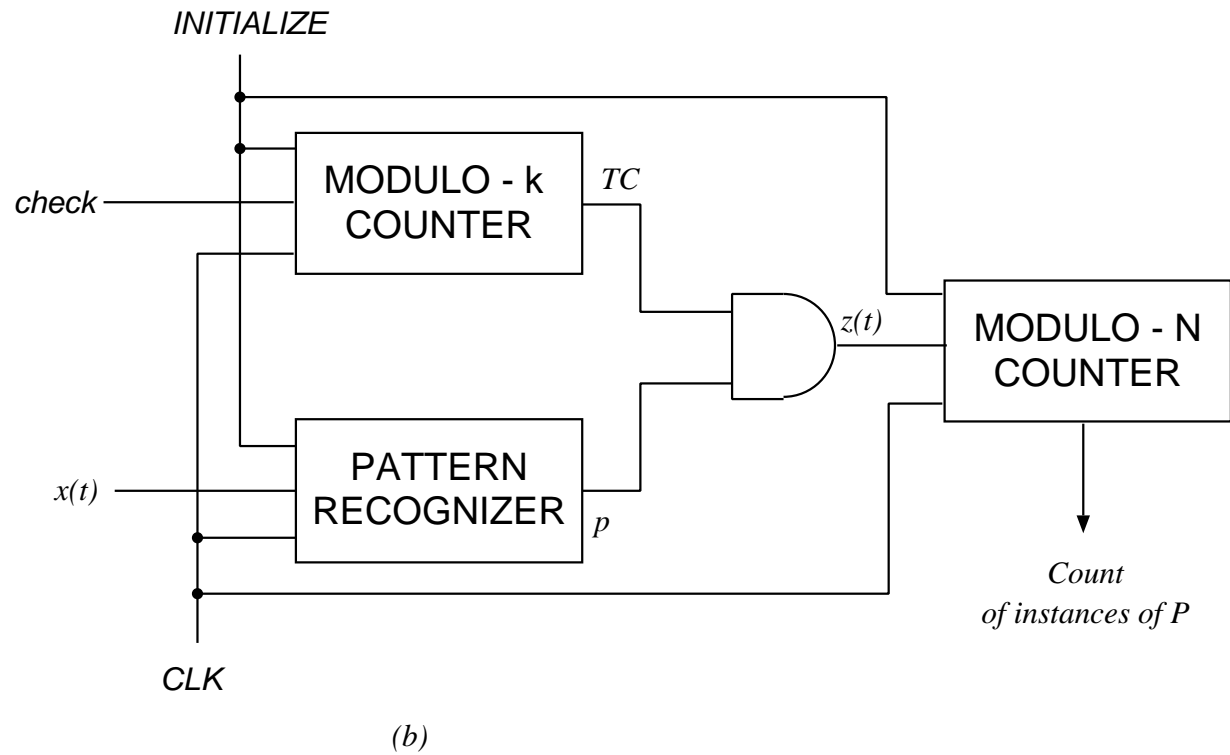


Figure 11.30: BLOCK PATTERN RECOGNIZER.