

- 
- SPECIFICATION OF PROGRAMMABLE COMBINATIONAL AND SEQUENTIAL MODULES
    1. PSA
    2. ROM
    3. FPGA
  - THE WAY THE MODULES ARE PROGRAMMED
  - NETWORKS OF PROGRAMMABLE MODULES
  - EXAMPLES OF USES

# PROGRAMMABLE SEQUENTIAL ARRAYS (PSA)

 


Figure 12.1: PROGRAMMABLE SEQUENTIAL ARRAY (PSA).

## Example 12.1: IMPLEMENTATION OF SEQUENTIAL SYSTEMS USING PSAs<sup>3</sup>

---

- SEQUENCE GENERATOR

INPUTS:  $x \in \{0, 1\}$

OUTPUTS:  $z \in \{0, 1, 3, 6, 7, 10, 14\}$

FUNCTION: The transition and output functions

$x = 0 : z = 0 \rightarrow 10 \rightarrow 14 \rightarrow 7 \rightarrow 0 \dots$

$x = 1 : z = 1 \rightarrow 10 \rightarrow 3 \rightarrow 6 \rightarrow 1 \dots$

$x = 0 : z = 0000 \rightarrow 1010 \rightarrow 1110 \rightarrow 0111 \rightarrow 0000 \dots$

$x = 1 : z = 0001 \rightarrow 1010 \rightarrow 0011 \rightarrow 0110 \rightarrow 0001 \dots$

 
 


Figure 12.2: TIMING SEQUENCES IN Example 12.1.

## Example 12.1 (cont.)

---

$y$	$k = 0$	$k = 1$	
0	10	—	$k$
1	—	10	$k$
3	—	6	$x$
6	0	1	$k$
7	0	1	$k$
10	14	3	$k$
14	7	—	$x$
	$Y$		$K$

$y \in \{2, 4, 5, 8, 9, 11, 12, 13, 15\}$  – don't care states


$$K = xy_3y_2 + xy_3'y_2'y_1 + ky_1' + ky_3'y_2 + ky_3y_2'$$

$$Y_3 = y_1' + y_2'k'$$

$$Y_2 = y_3'y_2'y_1 + y_3k'$$

$$Y_1 = y_2' + y_3$$

$$Y_0 = y_3k + y_2k + y_3y_2$$

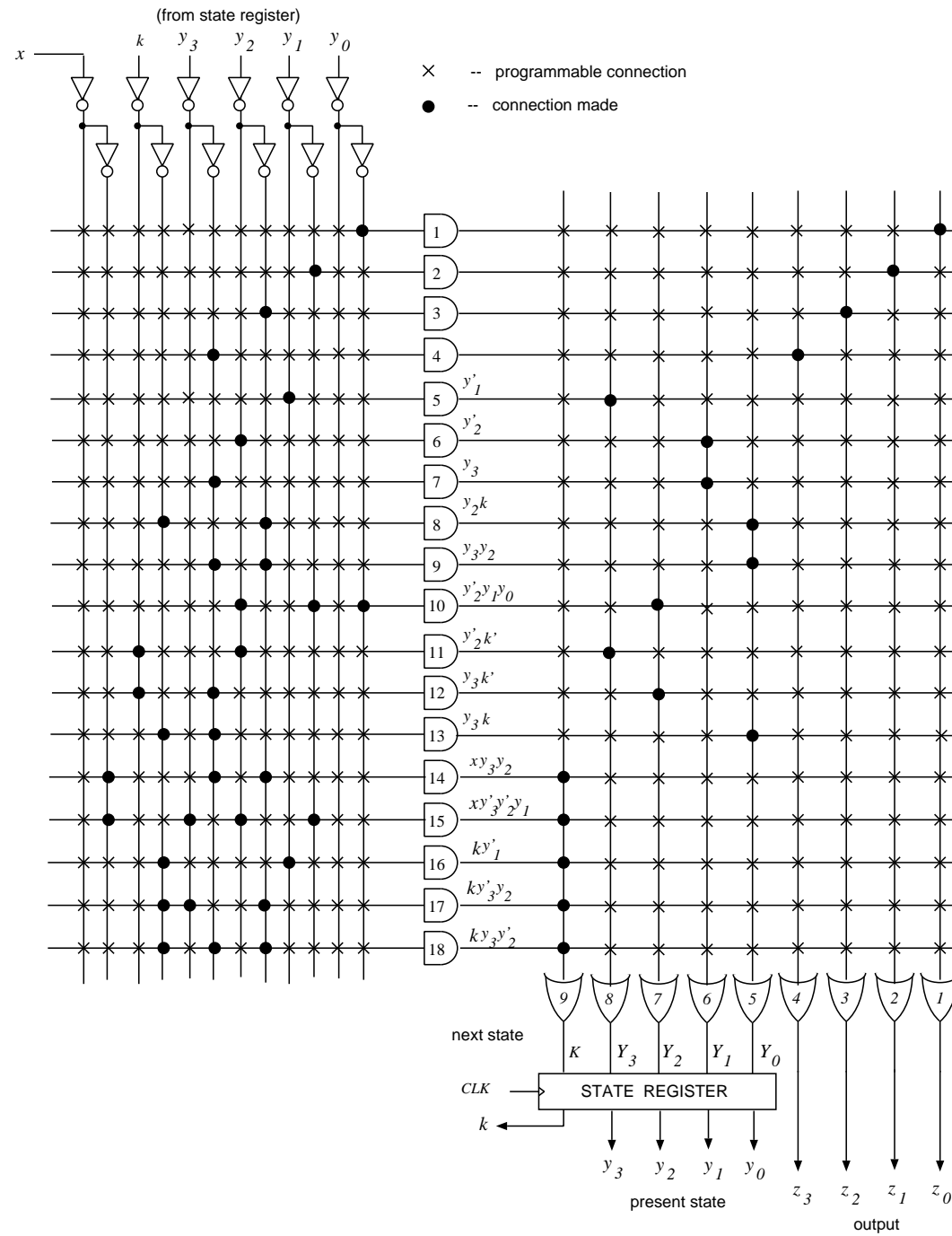

# READ-ONLY MEMORIES (ROM)

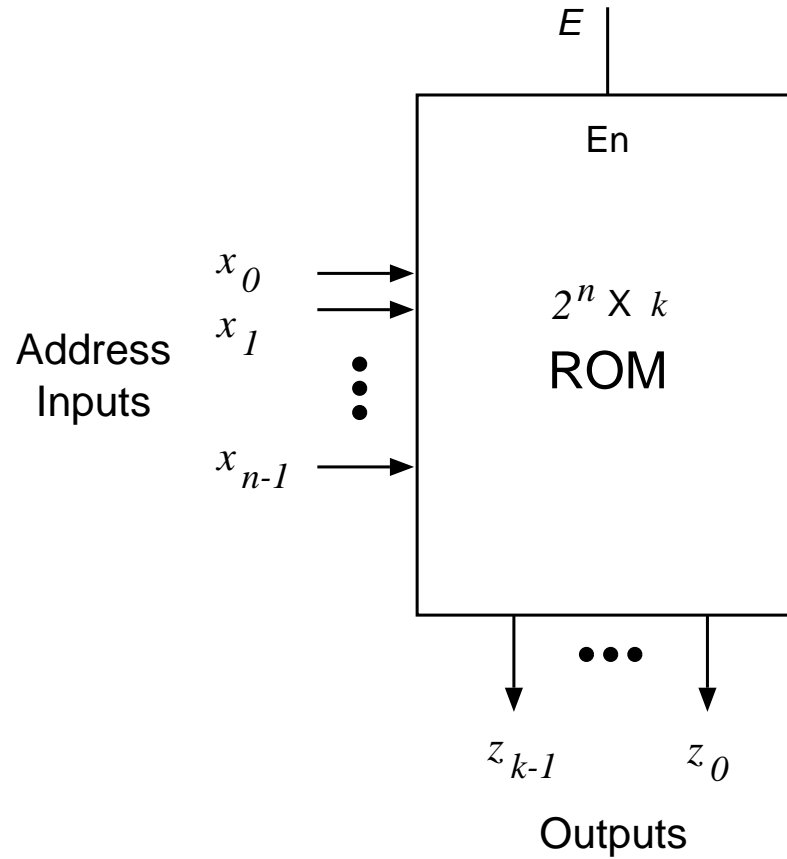


Figure 12.4: READ-ONLY MEMORY (ROM)

## EXAMPLE 12.2

---

Address	Contents
$x$	$z$
000	1011
001	1101
<b>010</b>	<b>0111</b>
011	1000
100	0000
101	1111
110	1111
111	1011



 


Figure 12.5: MOS IMPLEMENTATION OF A  $4 \times 4$  READ-ONLY MEMORY: a) THE FUNCTION; b) THE CIRCUIT.

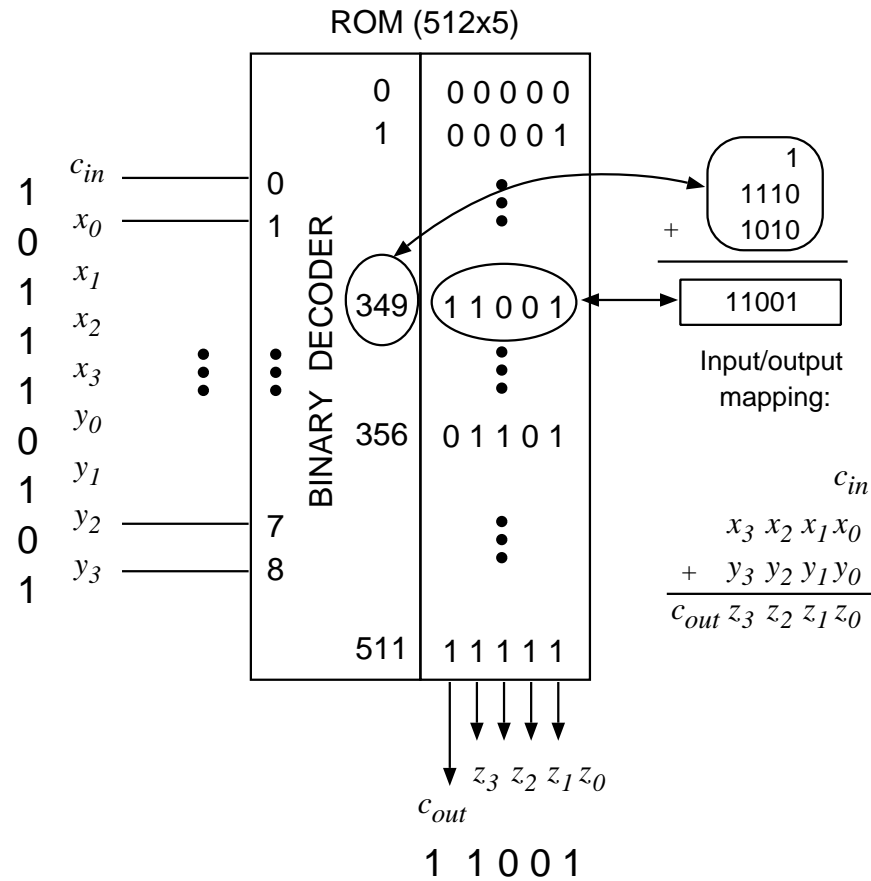


Figure 12.6: ROM-BASED IMPLEMENTATION OF A 4-BIT ADDER.

INPUTS:  $\underline{x} = (x_1, x_0), \quad x_i \in \{0, 1\}$

OUTPUTS:  $z \in \{0, 1, \}$

STATE:  $\underline{y} = (y_1, y_0), \quad y_i \in \{0, 1, \}$

FUNCTION: The transition and output function

$PS$	$x_1x_0$		
$y_1y_0$	01	10	11
00	01,0	10,1	10,0
01	00,0	11,1	11,0
10	11,0	10,0	00,1
11	10,0	00,0	11,1
	$Y_1Y_0, z$		
	$NS, \text{Output}$		

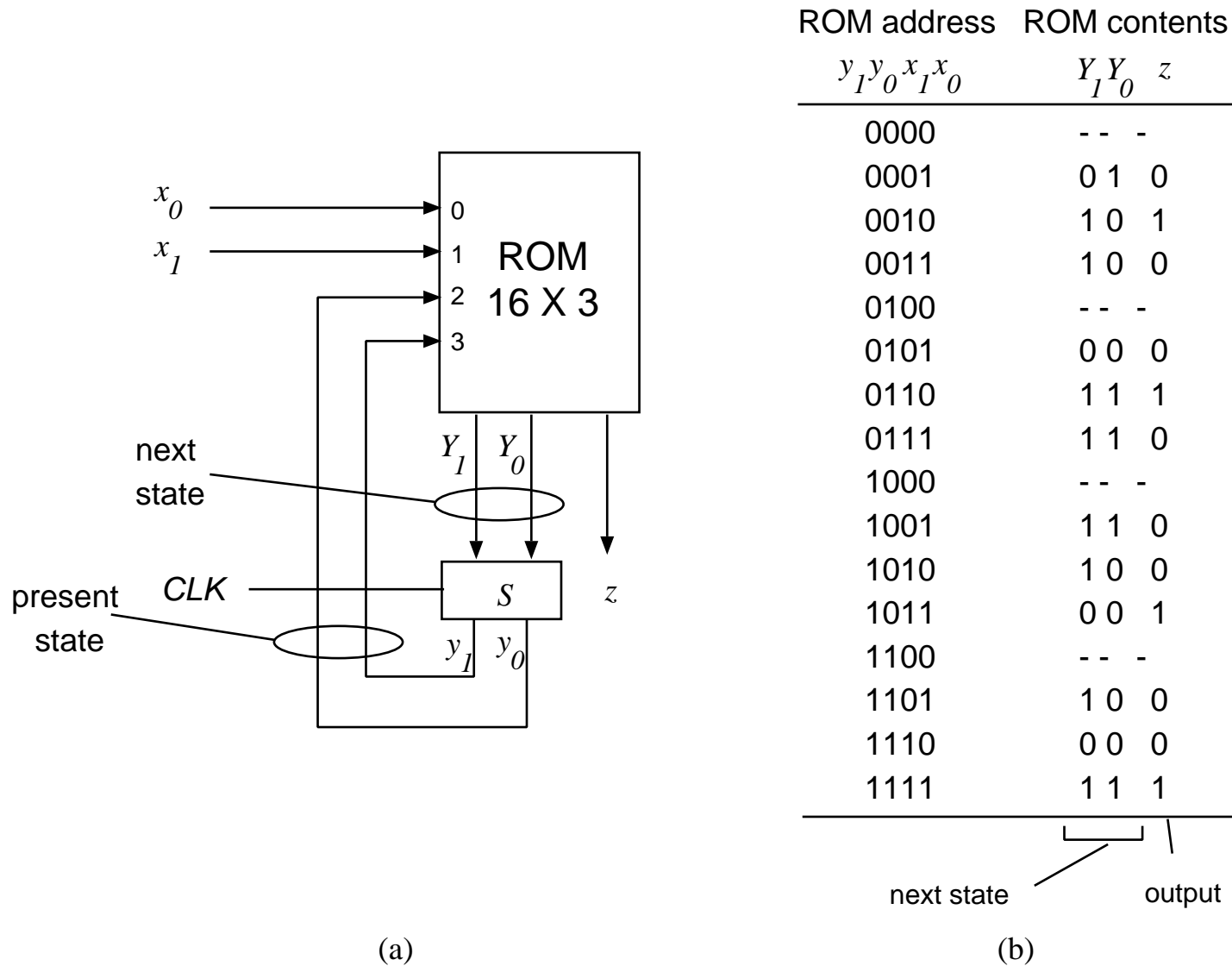


Figure 12.7: ROM-based implementation of a sequential system: a) network; b) ROM contents.

## TYPES OF ROM MODULES

---

- MASK-PROGRAMMED ROM
- FIELD-PROGRAMMABLE ROM (PROMs)
- ERASABLE ROM (EPROM)
- ELECTRICALLY ERASABLE ROM(*flash-memory*) or EEPROM

$$f_1(x_4, x_3, x_2, x_1, x_0) = \text{one-set}(0, 3, 11, 12, 16, 23, 27)$$

$$f_0(x_4, x_3, x_2, x_1, x_0) = \text{one-set}(5, 7, 19, 21, 31)$$

ROM MODULE:  $8 \times 2$

$$\begin{aligned} \underline{x} &= (\underline{x}^{(0)}, \underline{x}^{(1)}) \\ \underline{x}^{(0)} &= (x_4, x_3) \\ \underline{x}^{(1)} &= (x_2, x_1, x_0) \end{aligned}$$

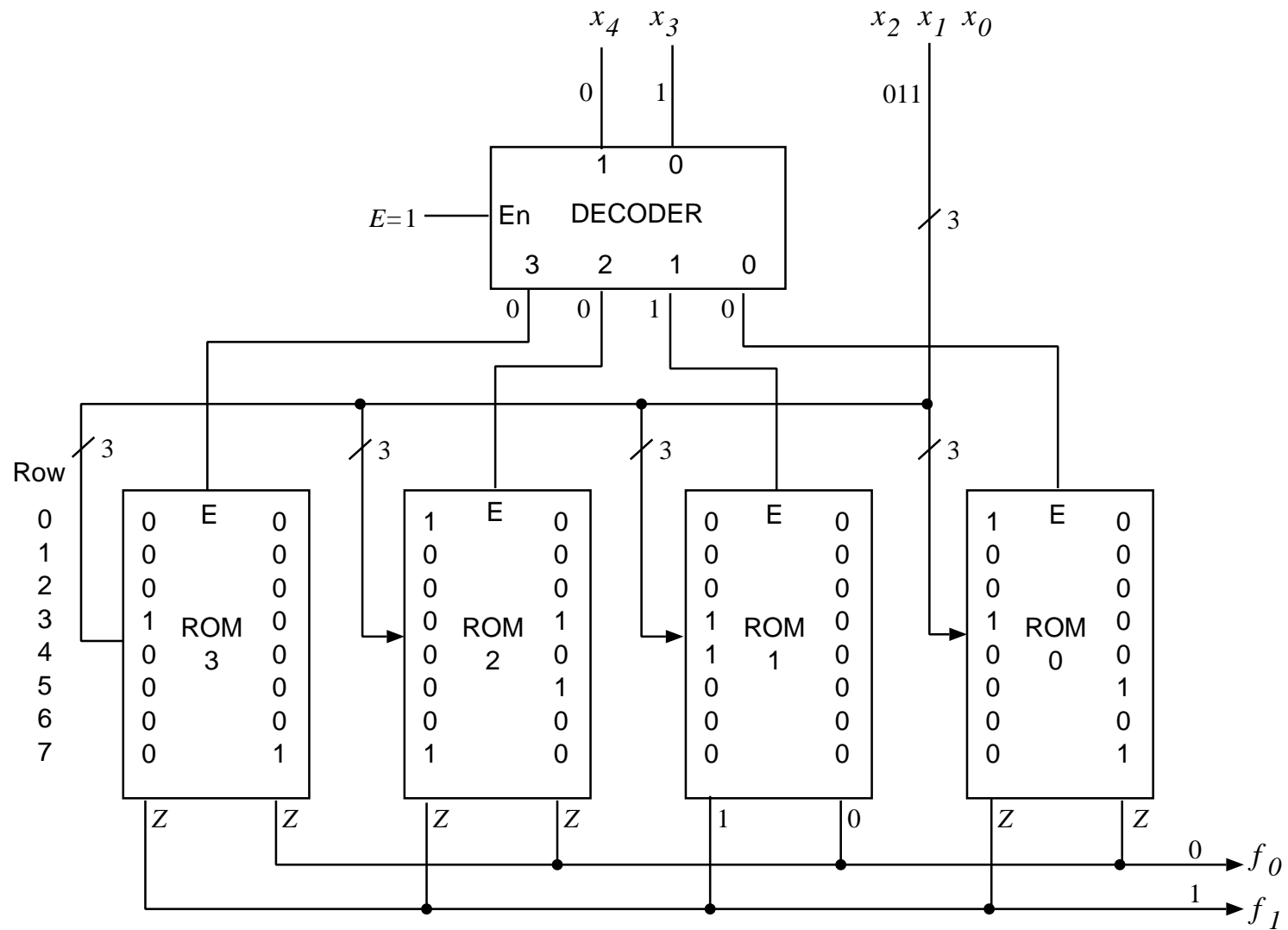


Figure 12.8: ROM-BASED NETWORK FOR THE IMPLEMENTATION OF TWO FUNCTIONS.

 


Figure 12.9: IMPLEMENTATIONS OF FUNCTIONS WITH  $n$  VARIABLES: a) ROMs AND DECODER; b) ROMs AND MULTIPLEXER



 


Figure 12.10: ROM-BASED IMPLEMENTATION OF LARGE NUMBER OF SWITCHING FUNCTIONS.

# FIELD PROGRAMMABLE GATE ARRAYS (FPGA)

 


Figure 12.11: ORGANIZATION OF AN FPGA chip.

- ON-CHIP STATIC RAM LOADED WITH CONFIGURATION BIT PATTERNS (SRAM-FPGAs). (volatile)
- ANTIFUSE-PROGRAMMED DEVICES PROGRAMMED ELECTRICALLY TO PROVIDE CONNECTIONS THAT DEFINE CHIP CONFIGURATION
- ARRAY-STYLE EPROM and EEPROM PROGRAMMED DEVICES USING SEVERAL PLAs AND A SHARED INTERCONNECT MECHANISM

 


Figure 12.12: SRAM FPGA PROGRAMMABLE COMPONENTS: (a) Switch. (b) 4-input multiplexer. (c) Look-up table (LUT).

# Example: XILINX XC2000

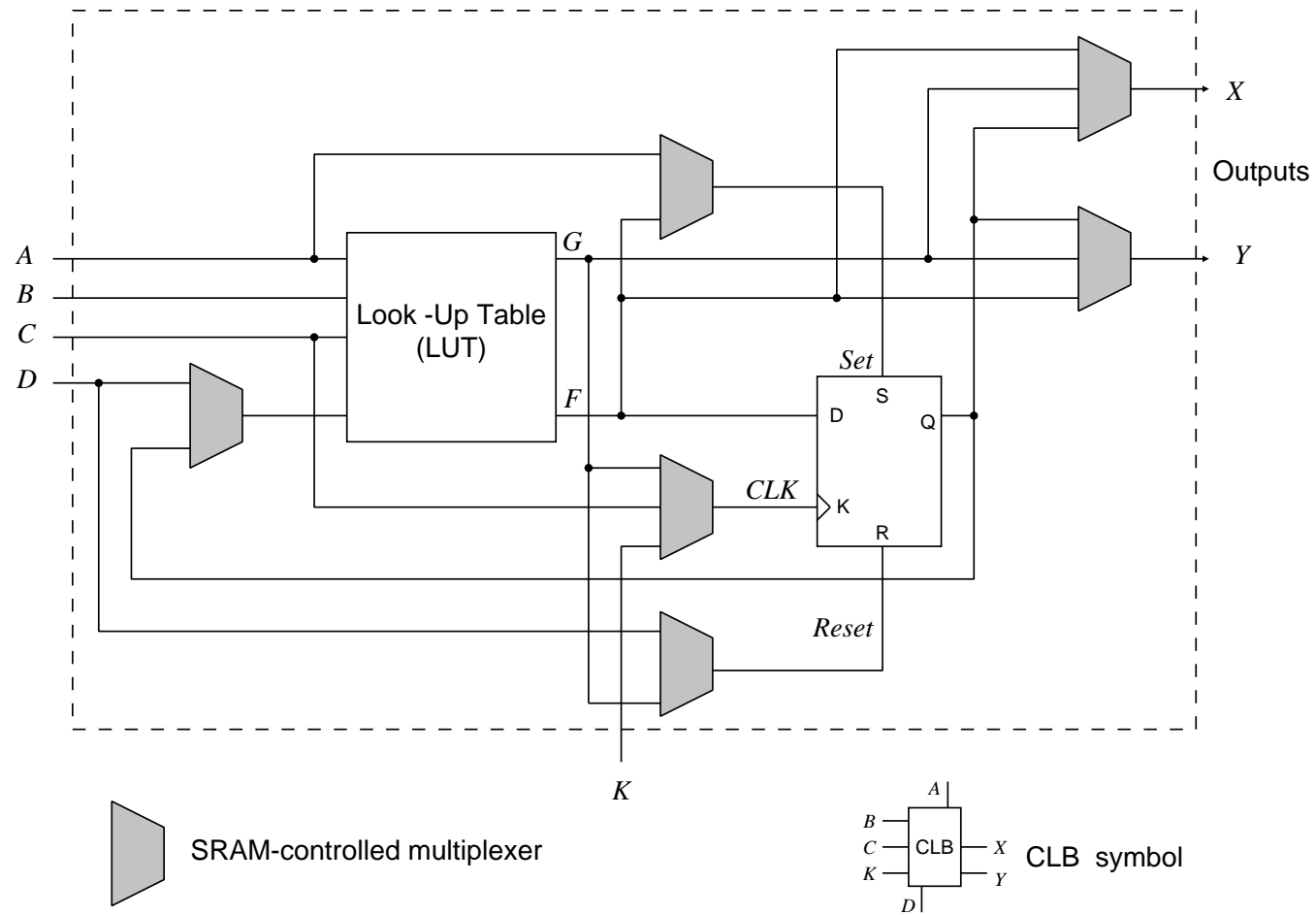


Figure 12.13: A CONFIGURABLE LOGIC BLOCK (CLB) (Courtesy of Xilinx, Inc.)

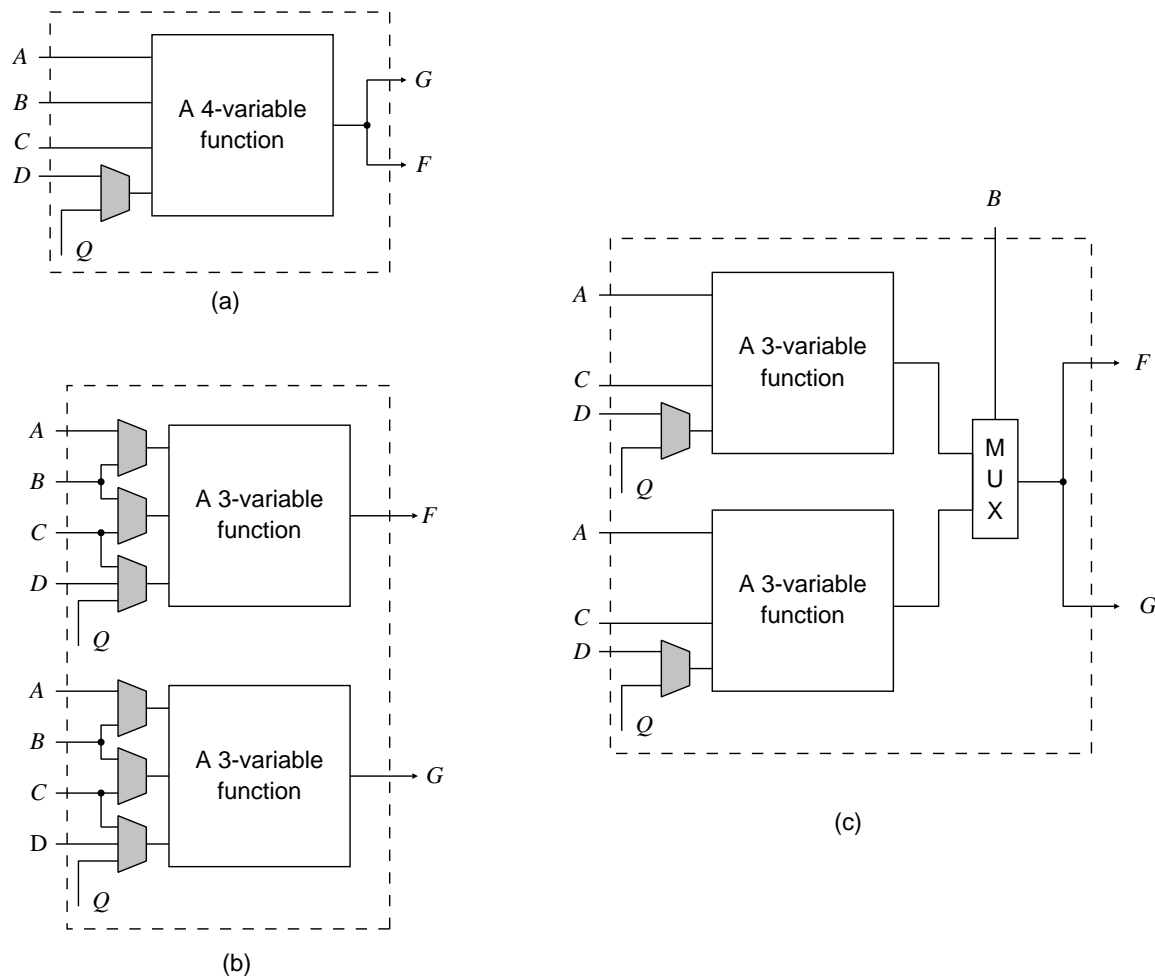


Figure 12.14: SRAM-FPGA options in generating functions: (a) One 4-variable function. (b) Two 3-variable functions. (c) Selection between two functions of 3 variables. (Courtesy of Xilinx, Inc.)

1. DIRECT INTERCONNECTIONS BETWEEN HORIZONTALLY AND VERTICALLY ADJACENT  $CLBs$ – PROVIDE FAST SIGNAL PATHS BETWEEN ADJACENT MODULES
2. GENERAL-PURPOSE INTERCONNECT CONSISTS OF VERTICAL AND HORIZONTAL WIRING SEGMENTS BETWEEN SWITCH MATRICES
3. LONG VERTICAL AND HORIZONTAL LINES SPAN THE WHOLE  $CLB$  ARRAY

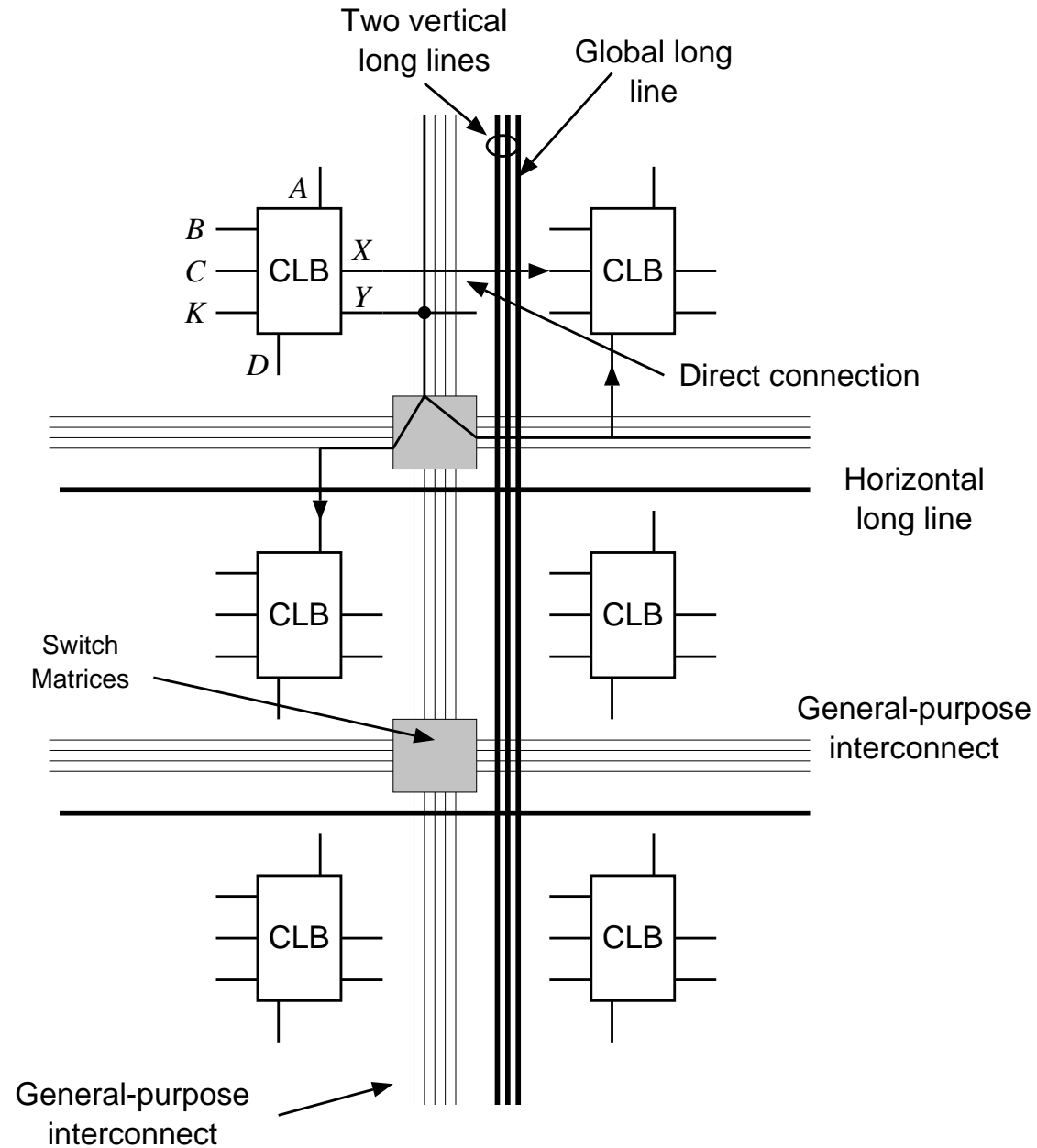


Figure 12.15: PROGRAMMABLE INTERCONNECT. (Courtesy of Xilinx, Inc.)



## Example 12.5: BCD ADDER MODULE

---

- IMPLEMENT A ONE-DIGIT BCD ADDER USING A SRAM-FPGAMODULE OF XC2000 TYPE

INPUTS:  $\underline{x} = (x_3, x_2, x_1, x_0)$ ,  $x_j \in \{0, 1\}$ ,  $x \in \{0, \dots, 9\}$   
 $\underline{y} = (y_3, y_2, y_1, y_0)$ ,  $y_j \in \{0, 1\}$ ,  $y \in \{0, \dots, 9\}$   
 $c_{in} \in \{0, 1\}$

OUTPUTS:  $\underline{s} = (s_3, s_2, s_1, s_0)$ ,  $s_j \in \{0, 1\}$ ,  $s \in \{0, \dots, 9\}$   
 $c_{out} \in \{0, 1\}$

FUNCTION:  $x + y + c_{in} = 10c_{out} + s$

- COMPUTE  $16u + v = x + y + c_{in} \in \{0, \dots, 19\}$  using a 4-bit binary adder

## Example 12.5 (cont.)

---

- THREE CASES:

$$u = 0 \quad v \leq 9 \quad s = v \quad c_{out} = 0$$

$$u = 0 \quad v > 9 \quad s = v - 10 = (v + 6) \bmod 16 \quad c_{out} = 1$$

$$u = 1 \quad s = v + 16 - 10 = v + 6 \quad c_{out} = 1$$

⇒ BCD OUTPUT

$$s = \begin{cases} (v + 6) \bmod 16 & \mathbf{if} \quad u = 1 \text{ or } v \geq 10 \\ v & \mathbf{otherwise} \end{cases}$$

$$c_{out} = \begin{cases} 1 & \mathbf{if} \quad u = 1 \text{ or } v \geq 10 \\ 0 & \mathbf{otherwise} \end{cases}$$

THE CONDITION  $u = 1 \text{ or } v \geq 10$  CORRESPONDS TO SWITCHING EXPRESSION

$$t = u + v_3v_2 + v_3v_1$$

 


Figure 12.16: IMPLEMENTATION OF BCD ADDER MODULE

## Example 12.5 (cont.)

---

- SIMPLIFICATION OF THE 3-BIT ADDER

$$s_3 = v_3 \oplus t(v_2 + v_1)$$


$$s_2 = v_2 \oplus tv'_1$$

$$s_1 = v_1 \oplus t$$

MOREOVER,

$$s_0 = v_0$$

$$c_{out} = t$$

 

INVOLVES INTENSIVE USE OF CAD TOOLS AND MODULE LIBRARIES

**Design entry** : A SCHEMATIC ENTRY OR A BEHAVIORAL DESCRIPTION

**Implementation** :

- PARTITION OF DESIGN INTO SUBMODULES THAT CAN BE MAPPED ONTO CLBs,
- PLACEMENT OF SUBMODULES ONTO CHIP, AND
- ROUTING OF SIGNALS TO CONNECT THE SUBMODULES

**Design verification** :

- IN-CIRCUIT TESTING
- SIMULATION, AND
- TIMING ANALYSIS