

- 
- CANONICAL FORM OF SEQUENTIAL NETWORKS
  - LATCHES AND EDGE-TRIGGERED CELLS. D FLIP-FLOP
  - TIMING CHARACTERISTICS
  - ANALYSIS AND DESIGN OF CANONICAL NETWORKS
  - SR, JK and T FLIP-FLOP
  - ANALYSIS OF FLIP-FLOP NETWORKS
  - DESIGN OF FLIP-FLOP NETWORKS. EXCITATION FUNCTIONS
  - SPECIAL STATE ASSIGNMENTS: ONE-FLIP-FLOP-PER-STATE AND SHIFTING REGISTER

# CANONICAL FORM OF SEQUENTIAL NETWORKS (Huffman-Moore)

State-transition function  $s(t + 1) = G(s(t), x(t))$   
 Output function  $z(t) = H(s(t), x(t))$

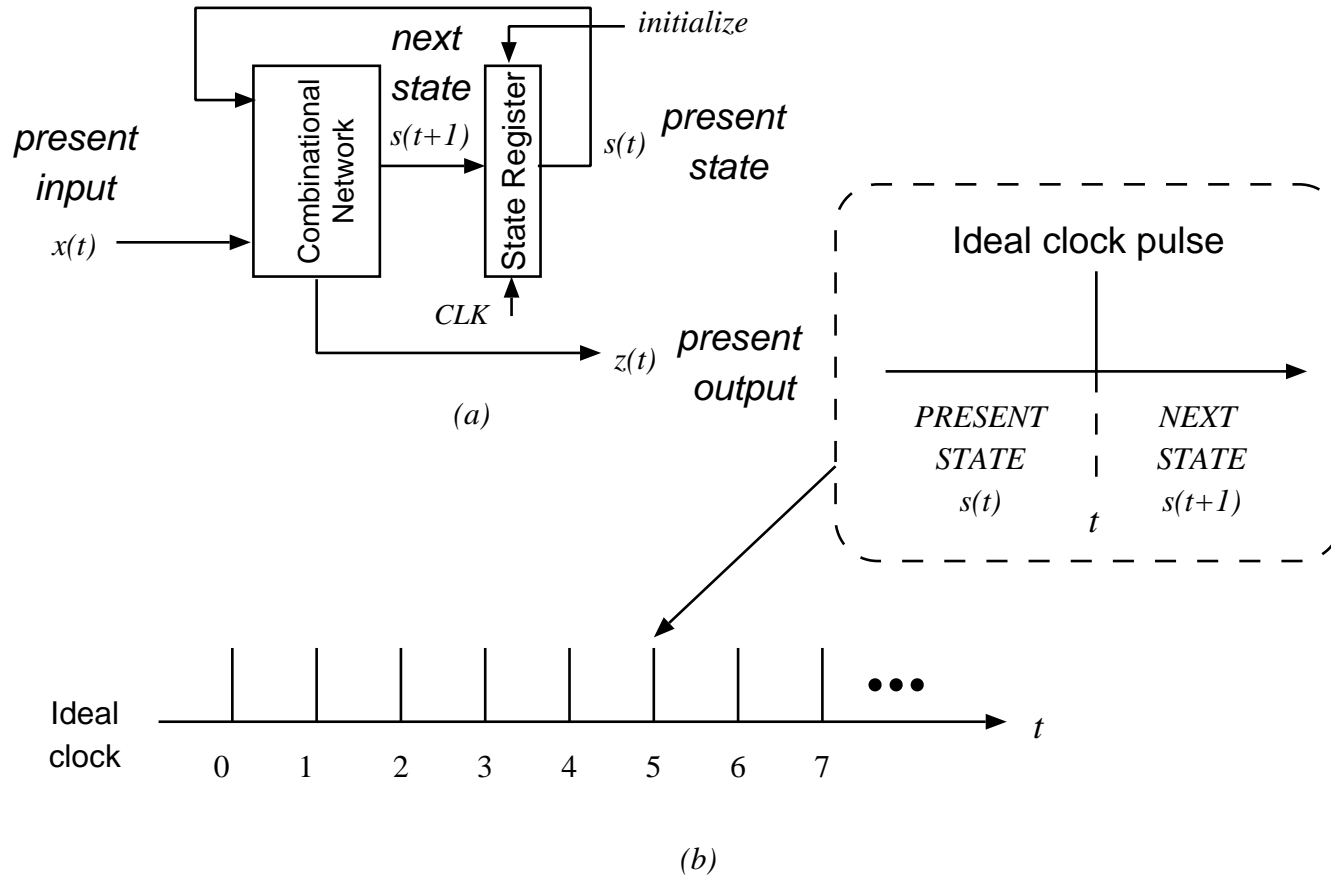


Figure 8.1: a) CANONICAL IMPLEMENTATION OF SEQUENTIAL NETWORK. b) IDEAL CLOCK SIGNAL AND ITS INTERPRETATION.

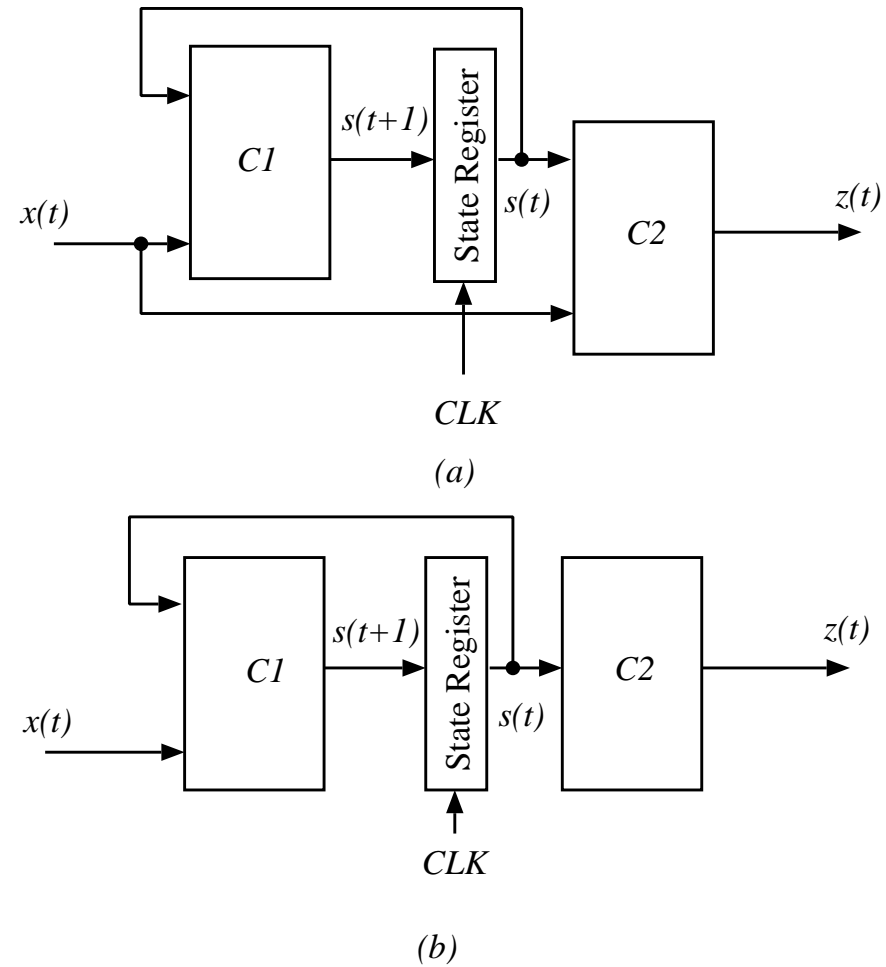


Figure 8.2: CANONICAL IMPLEMENTATIONS: a) MEALY MACHINE. b) MOORE MACHINE.

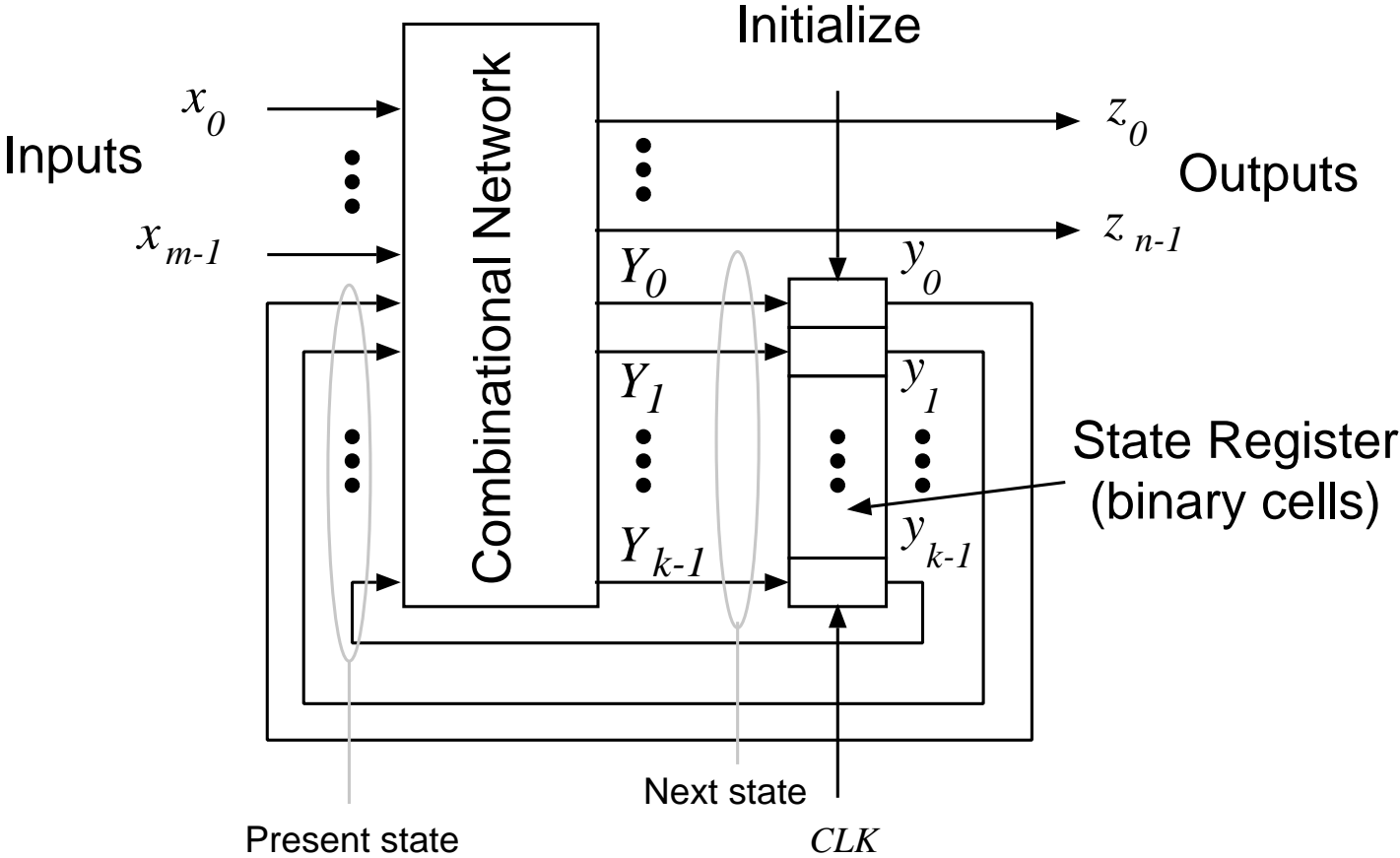


Figure 8.3: CANONICAL IMPLEMENTATION WITH BINARY VARIABLES.

## EXAMPLE 8.1

---

Input:  $\underline{x}(t) = (x_1, x_0), \quad x_i \in \{0, 1\}$   
 Output:  $z(t) \in \{0, 1\}$   
 State:  $\underline{y}(t) = (y_3, y_2, y_1, y_0), \quad y_i(t) \in \{0, 1\}$   
 Initial state:  $\underline{y}(0) = (0, 0, 0, 0)$

Function: The transition and output functions

$$Y_3 = y_2 x_1' x_0$$

$$Y_2 = (y_1 + y_2) x_0' + y_3 x_1$$

$$Y_1 = (y_0 + y_3) x_1' x_0 + (y_0 + y_1) x_1$$

$$Y_0 = (y_0 + y_3) x_0' y_1 x_1' x_0 + y_2 x_1$$

$$z = y_3 + y_2 + y_1 + y_0$$

EXAMPLE 8.1 (cont.)

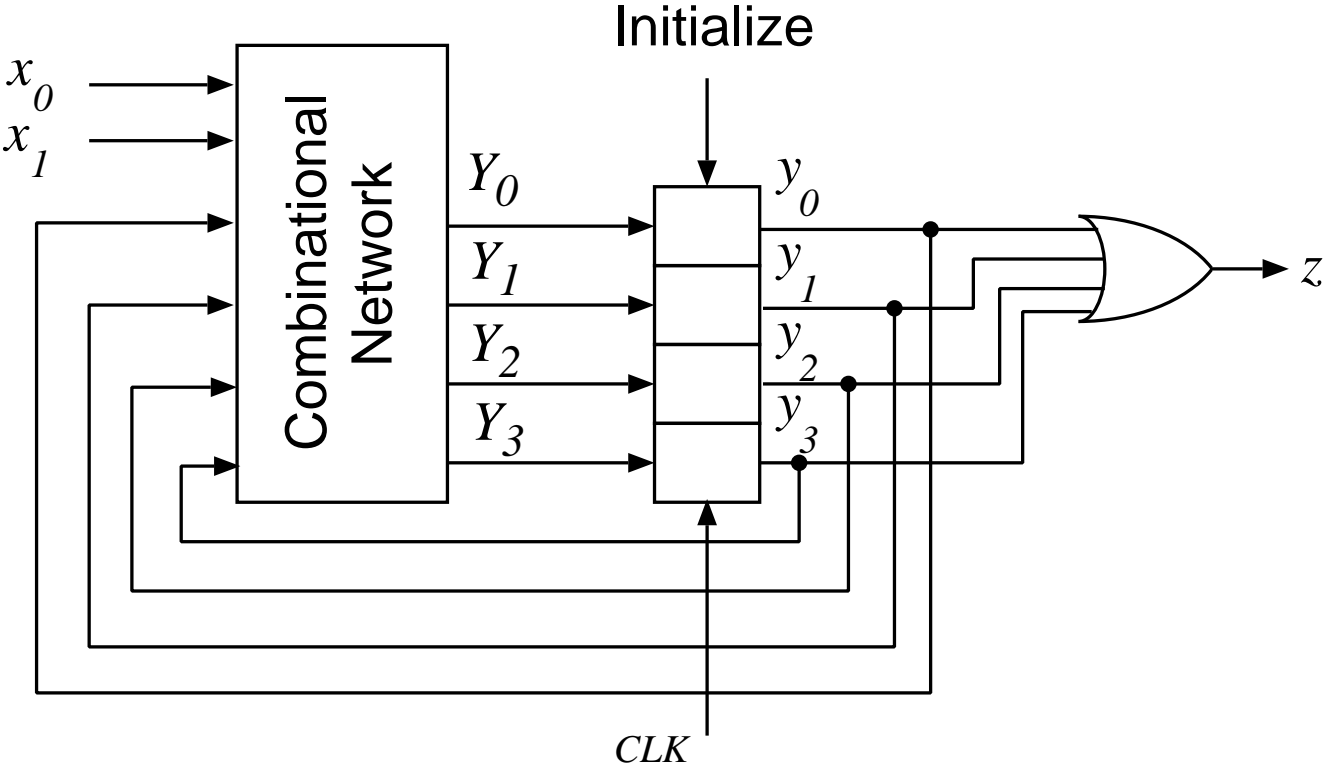


Figure 8.4: CANONICAL NETWORK FOR EXAMPLE 8.1.

- clock period  $T$
- clock frequency  $f = 1/T$
- (clock) pulse width  $t_w$

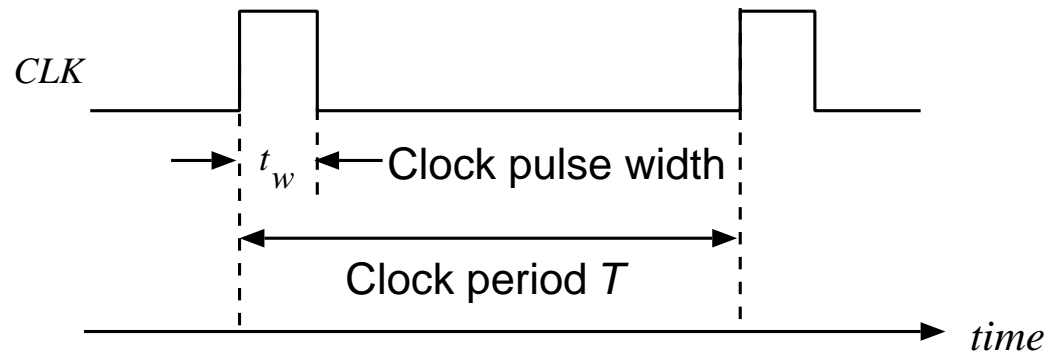


Figure 8.5: PULSE WIDTH AND CLOCK PERIOD.

# GATED LATCH - FIRST TRY

 



Figure 8.6: a) GATED-LATCH. b) TIMING BEHAVIOR.

$$Q(t + t_p) = D(t) \cdot E(t) + Q(t) \cdot E'(t)$$


- LEVEL-SENSITIVE: when  $E = 1$  then  $Q = D$



# NOR-NOR LATCH

 

(a)

 


\*  $c$  kept in 0 even when  $b=0$  +  $Q$  kept in 0 even when  $d=0$


(b)

Figure 8.7: a) IMPLEMENTATION OF GATED-LATCH WITH NOR GATES. b) TIMING DIAGRAM.

# LATCH WITH TRANSMISSION GATES

 

(a)

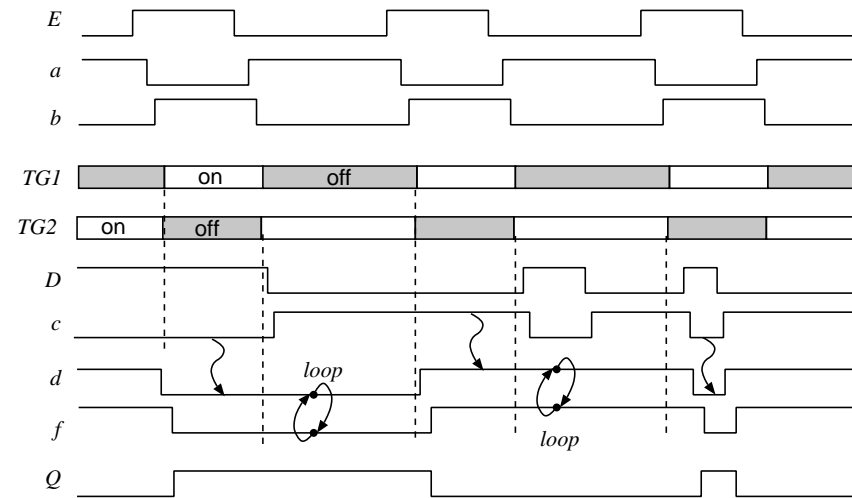

(b)

Figure 8.8: a) IMPLEMENTATION OF GATED-LATCH WITH TRANSMISSION GATES. b) TIMING DIAGRAM.

# LIMITATIONS OF GATED-LATCH

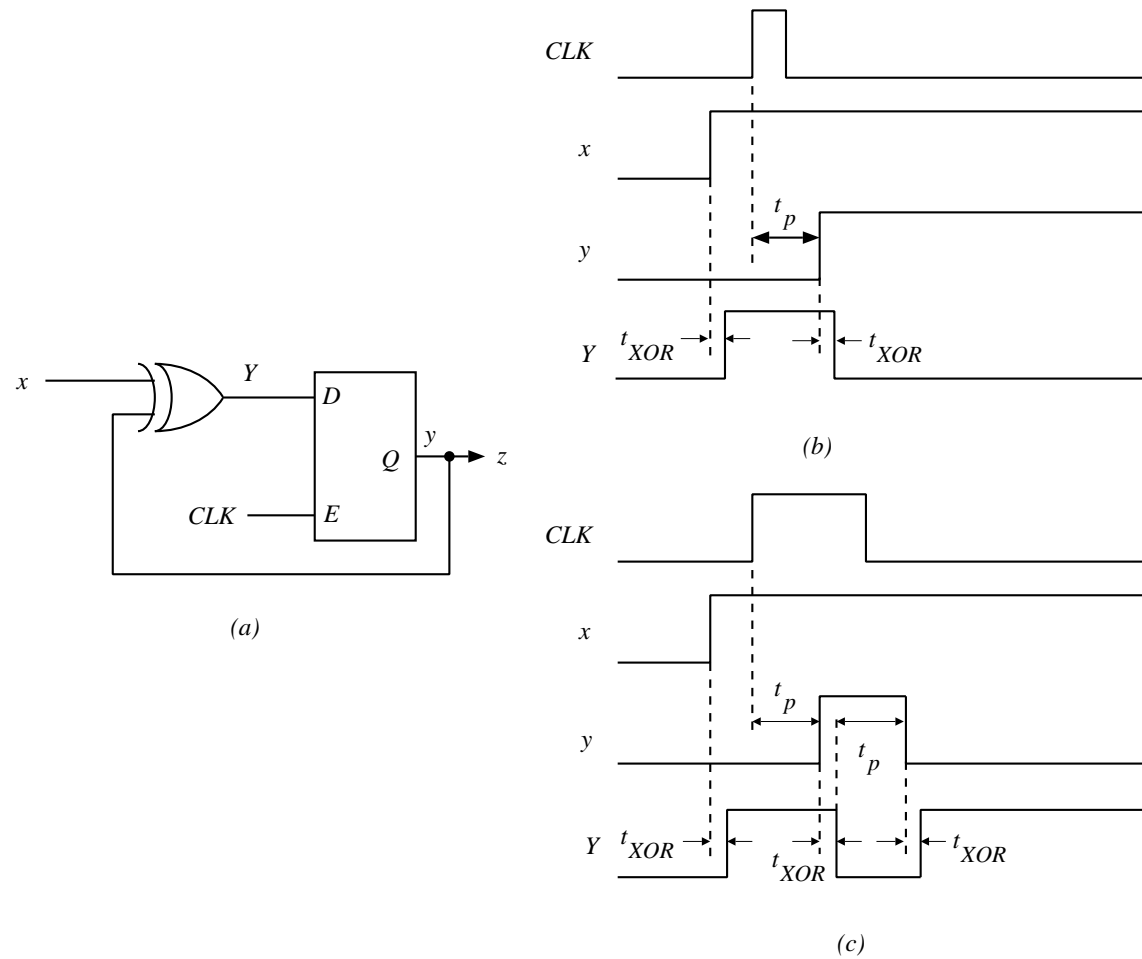


Figure 8.9: a) SEQUENTIAL NETWORK. b) CORRECT TIMING BEHAVIOR. c) INCORRECT TIMING BEHAVIOR.

# A SOLUTION: EDGE-TRIGGERED CELL

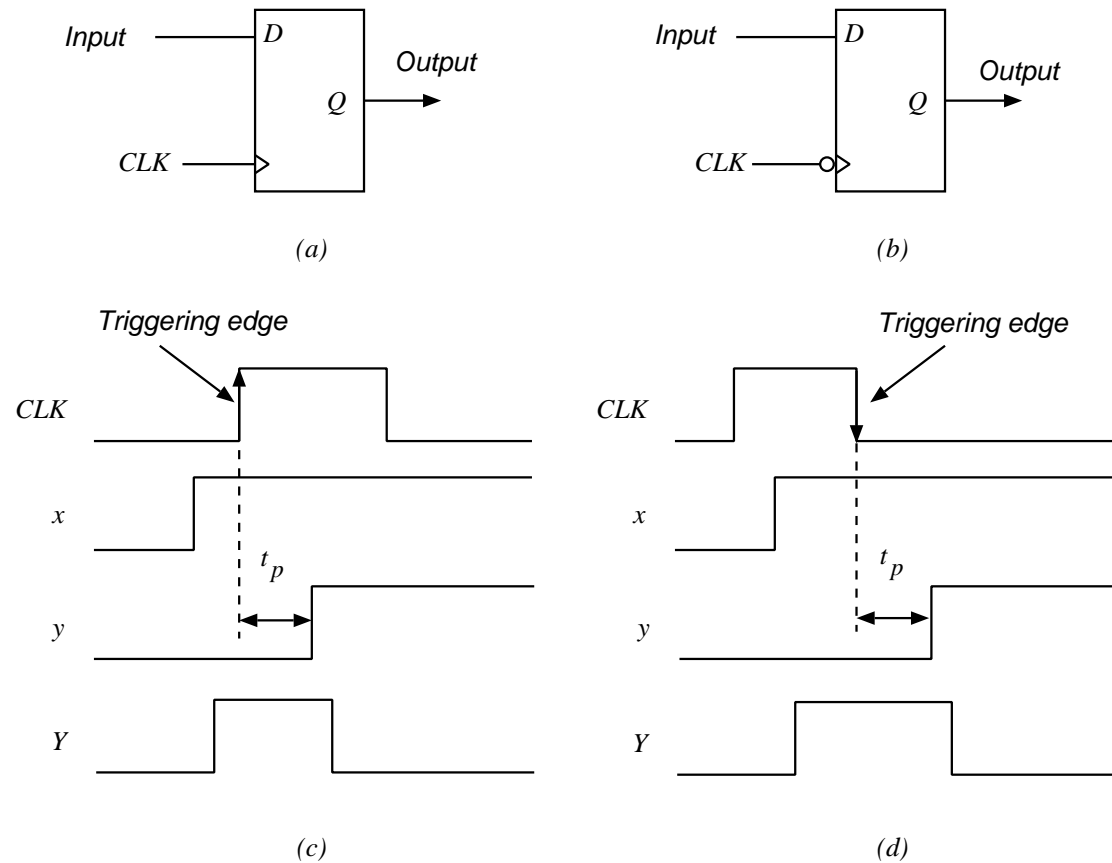


Figure 8.10: EDGE-TRIGGERED CELL: a) LEADING-EDGE-TRIGGERED CELL. b) TRAILING-EDGE-TRIGGERED CELL. c) LEADING-EDGE-TRIGGERED CELL IN NETWORK OF Figure 8.9. d) TRAILING-EDGE-TRIGGERED CELL IN NETWORK OF Figure 8.9.

# IMPLEMENTATION: MASTER-SLAVE CELL

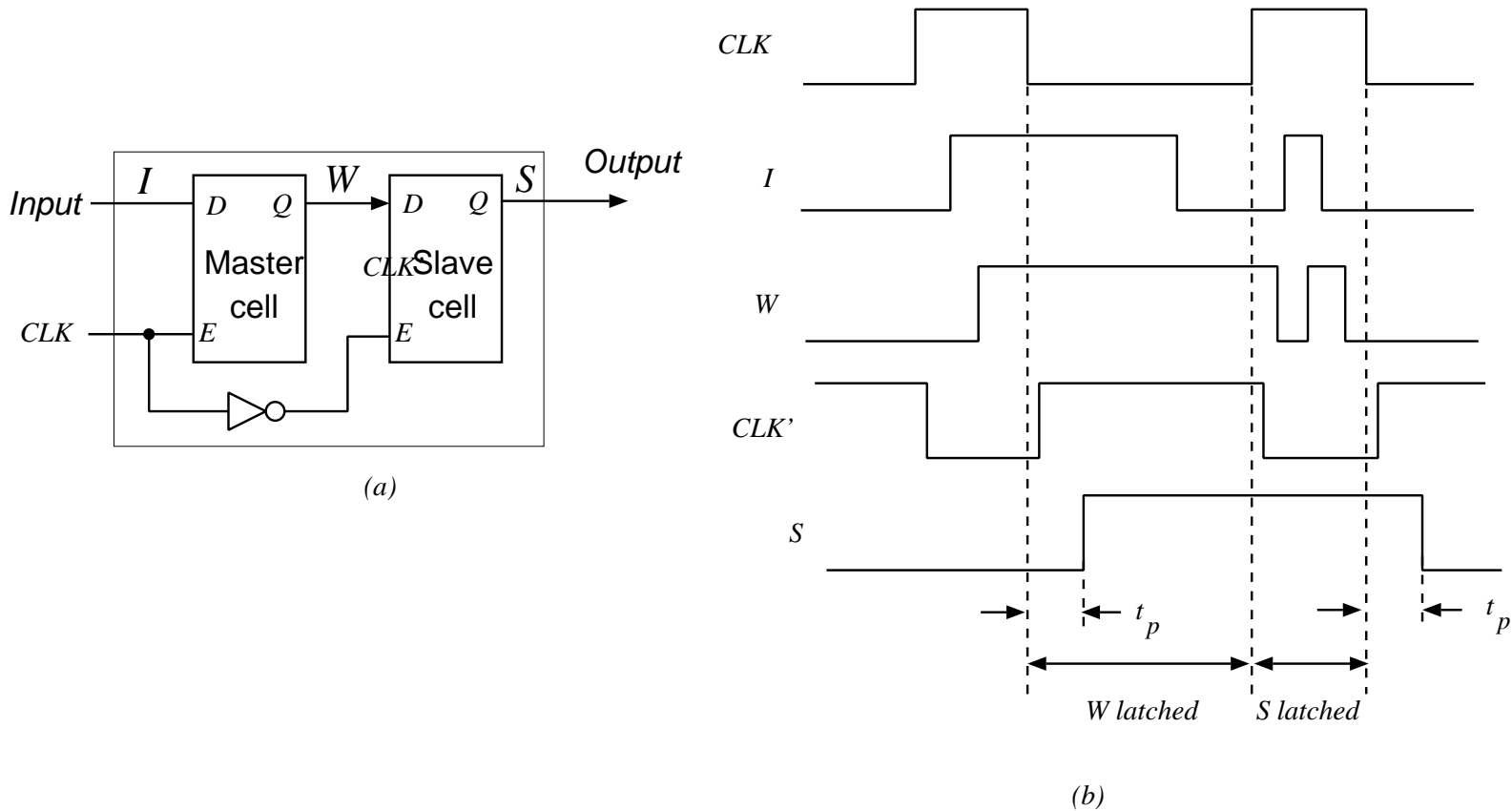


Figure 8.11: a) MASTER-SLAVE IMPLEMENTATION OF TRAILING-EDGE-TRIGGERED CELL. b) MASTER-SLAVE STATE CHANGE PROCESS.

# PRACTICAL BASIC CELL: D flip-flop

 


Figure 8.12: D FLIP-FLOP AND ITS STATE DIAGRAM.

$PS = Q(t)$	$D(t)$	
	0	1
0	0	1
1	0	1
$NS = Q(t + 1)$		

$$Q(t + 1) = D(t)$$

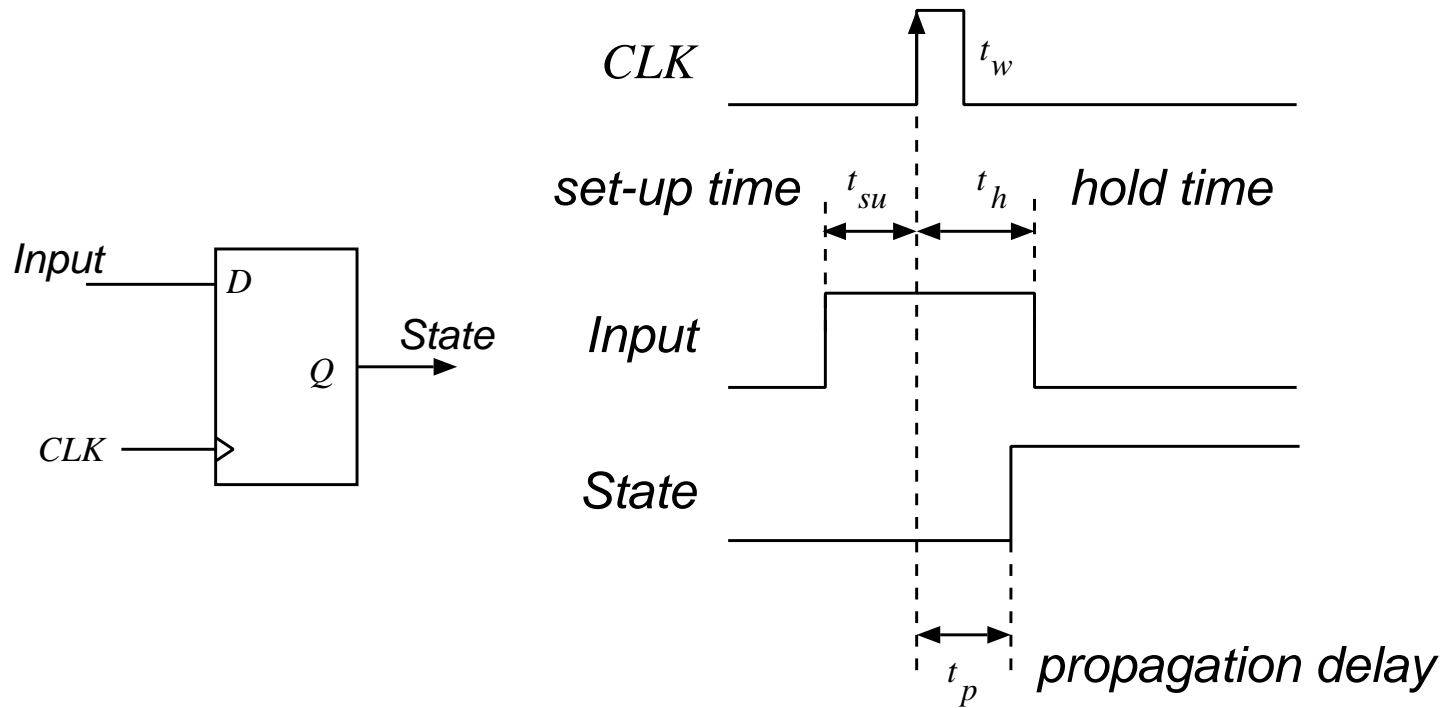


Figure 8.13: TIME BEHAVIOR OF CELL.

## CHARACTERISTICS OF A CMOS D flip-flop

---

Delays					Input factor	Size
$t_{pLH}$ [ns]	$t_{pHL}$ [ns]	$t_{su}$ [ns]	$t_h$ [ns]	$t_w$ [ns]	[std. loads]	[equiv. gates]
$0.49 + 0.038L$	$0.54 + 0.019L$	0.30	0.14	0.2	1	6

$L$ : output load of the flip-flop

- THIS FLIP-FLOP HAS ONLY THE UNCOMPLEMENTED OUTPUT



- NETWORK SET-UP TIME:**  $t_{su}^x(net) = d1^x + t_{su}(cell)$

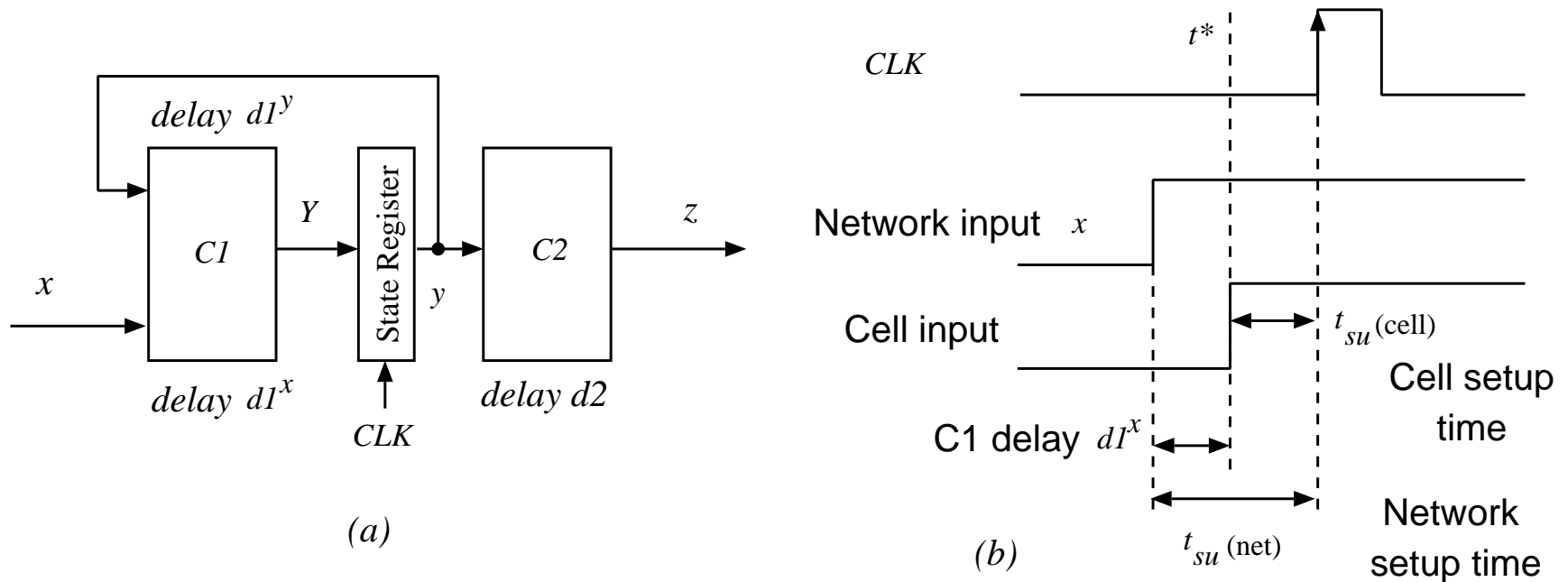


Figure 8.14: TIMING FACTORS IN SEQUENTIAL NETWORKS: a) THE NETWORK. b) NETWORK SET-UP TIME.

## TIMING FACTORS (cont.)

- NETWORK HOLD TIME:  $t_h(net) = t_h(cell)$

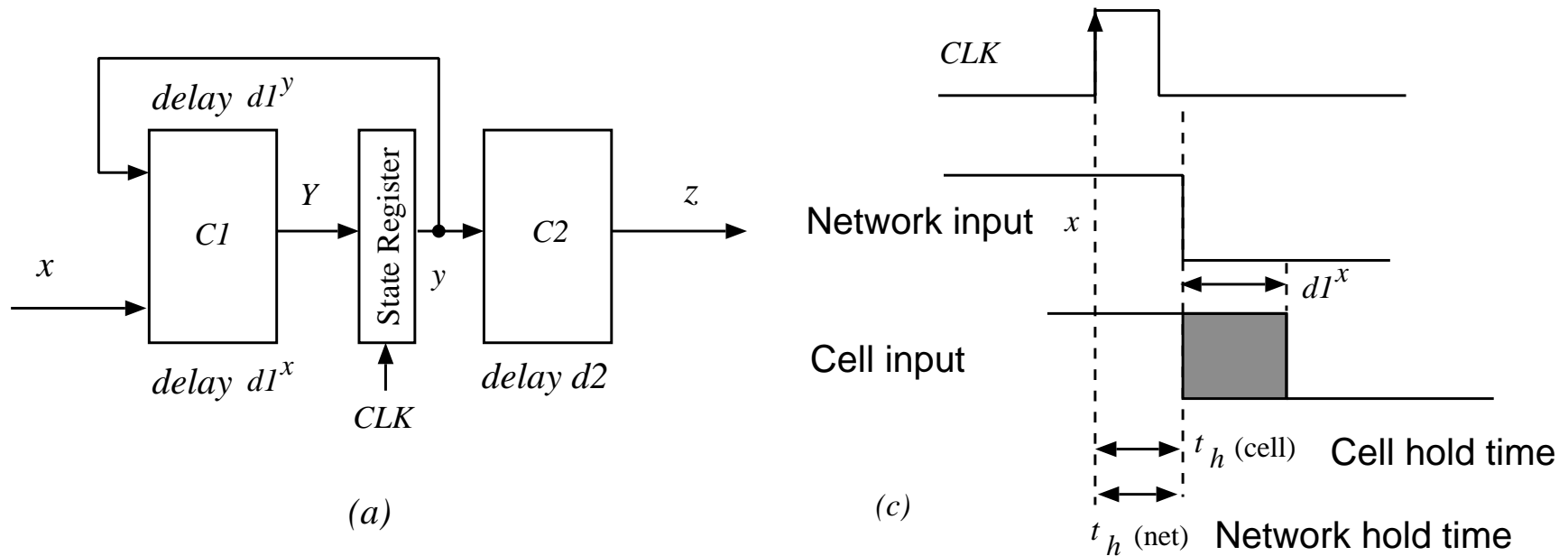


Figure 8.14: TIMING FACTORS IN SEQUENTIAL NETWORKS: a) THE NETWORK. c) NETWORK HOLD TIME.

- NETWORK PROPAGATION DELAY:  $t_p(net) = t_p(cell) + d2$

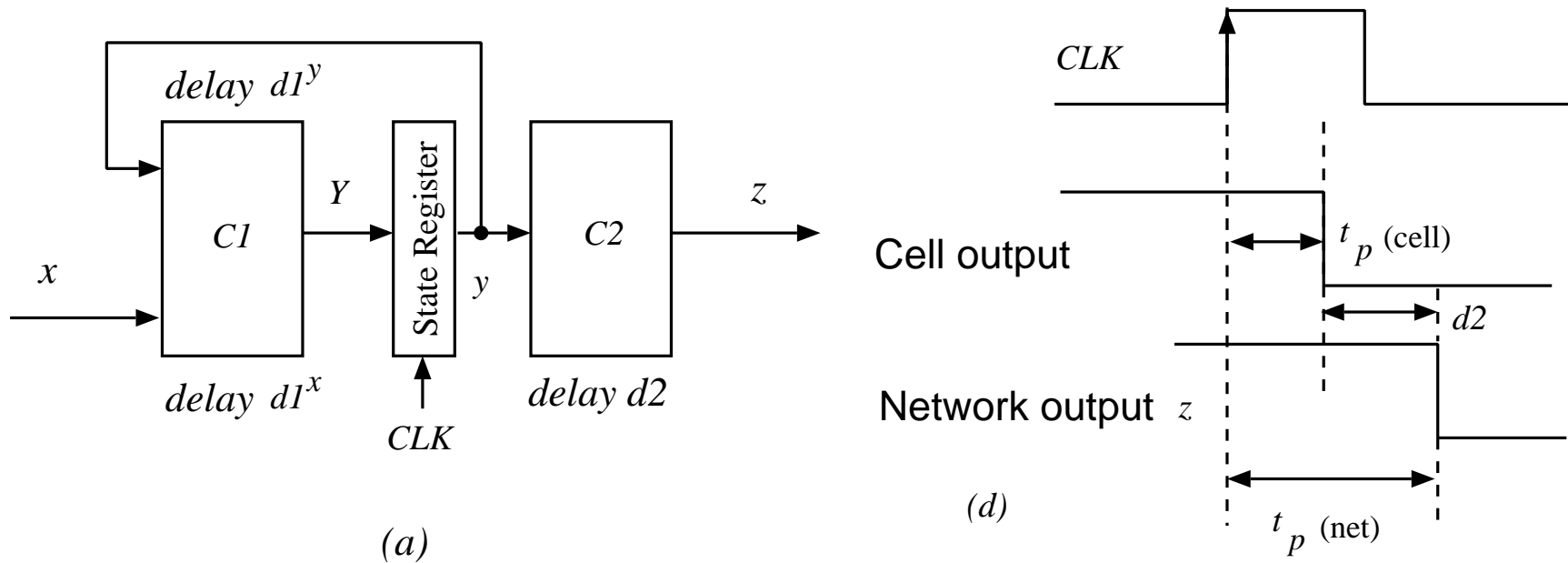


Figure 8.14: TIMING FACTORS IN SEQUENTIAL NETWORKS: a) THE NETWORK. d) NETWORK PROPAGATION DELAY.

# MAXIMUM CLOCK FREQUENCY

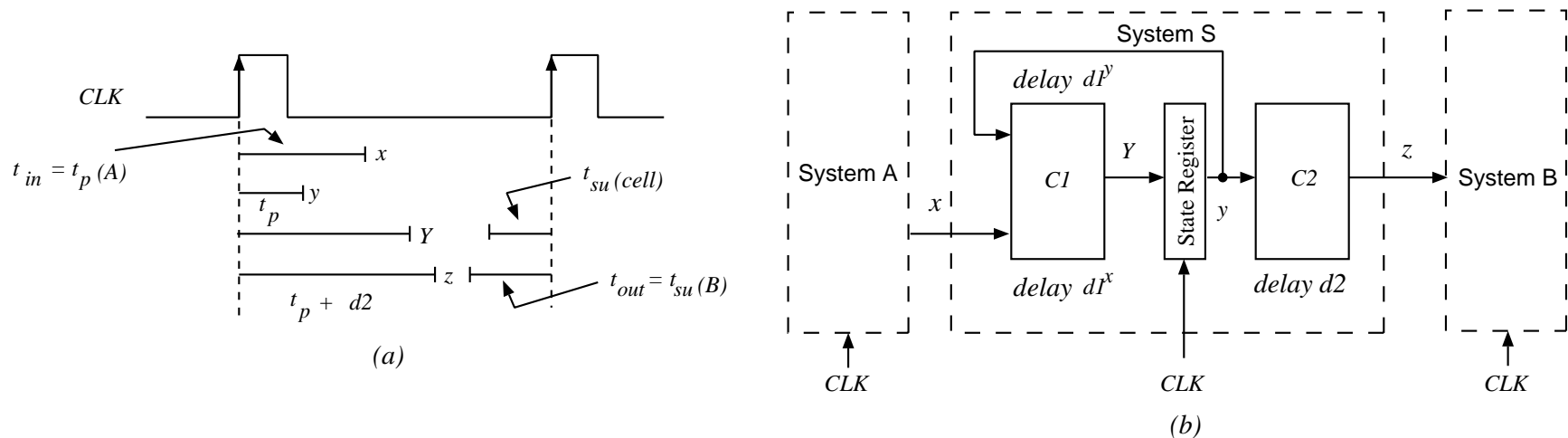


Figure 8.15: MAXIMUM CLOCK FREQUENCY: a) CLOCK PERIOD AND SIGNAL DELAYS. b) THE NETWORK.

- $t_{in}$  - TIME BETWEEN TRIGGERING EDGE OF CLOCK AND STABILIZATION OF INPUT  $x$
- $t_{out}$  - TIME BETWEEN STABILIZATION OF OUTPUT  $z$  AND NEXT CLOCK TRIGGERING EDGE

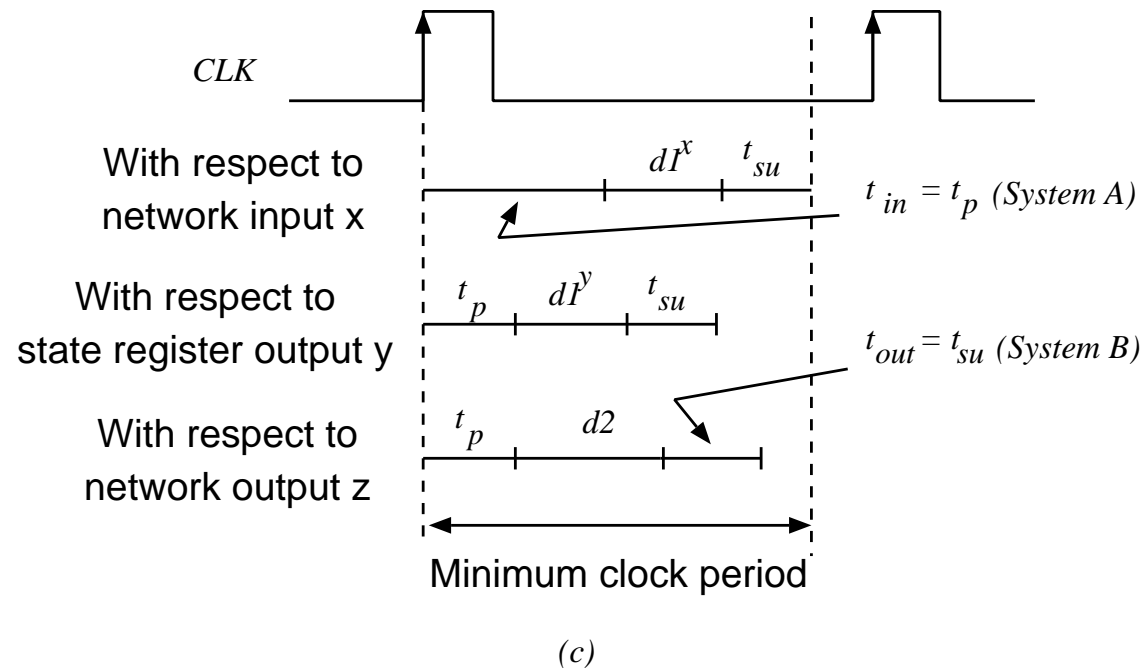
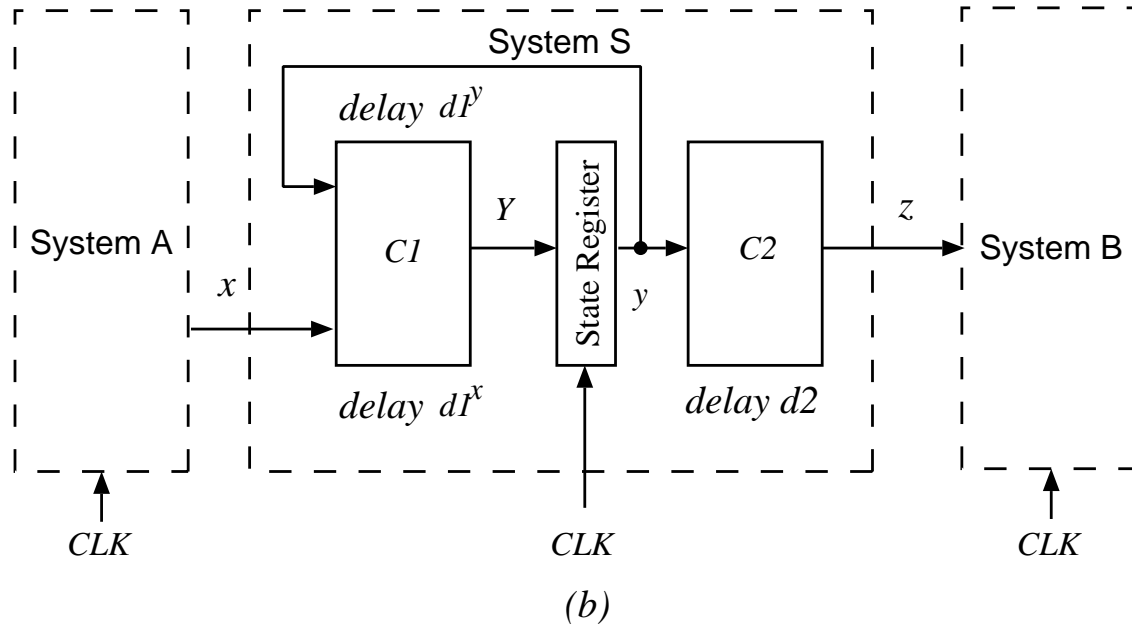


Figure 8.15: MAXIMUM CLOCK FREQUENCY: b) THE NETWORK. c) MINIMUM CLOCK PERIOD.

MAXIMUM CLOCK FREQUENCY (cont.)

---

$$T_{\min} = 1/f_{\max}$$

$$T_{\min} = \max[(t_{in} + t_{su}^x(net)), (t_p(cell) + t_{su}^y(net)), (t_p(net) + t_{out})]$$

$$t_h(cell) \leq t_p(cell)$$

$$T_{\min} = \max[(t_{in} + d1^x + t_{su}(cell)), (t_p(cell) + d1^y + t_{su}(cell)), (t_p(cell) + d2 + t_{out})]$$

## EXAMPLE 8.3

---

DETERMINE THE MAXIMUM CLOCK FREQUENCY

$$d1^x = d1^y = 2.5ns$$

$$d2 = 3ns$$

$$t_{su} = 0.3ns$$

$$t_p = 1ns$$

$$t_{in} = 2ns$$

$$t_{out} = 3ns$$

THE MINIMUM CLOCK PERIOD

$$T_{\min} = \max[(2 + 2.5 + 0.3), (1 + 2.5 + 0.3), (1 + 3 + 3)] = 7[ns]$$

THE MAXIMUM FREQUENCY

$$f_{\max} = \frac{1}{7 \times 10^{-9}} \approx 140(\text{MHz})$$

# CLOCK SKEW

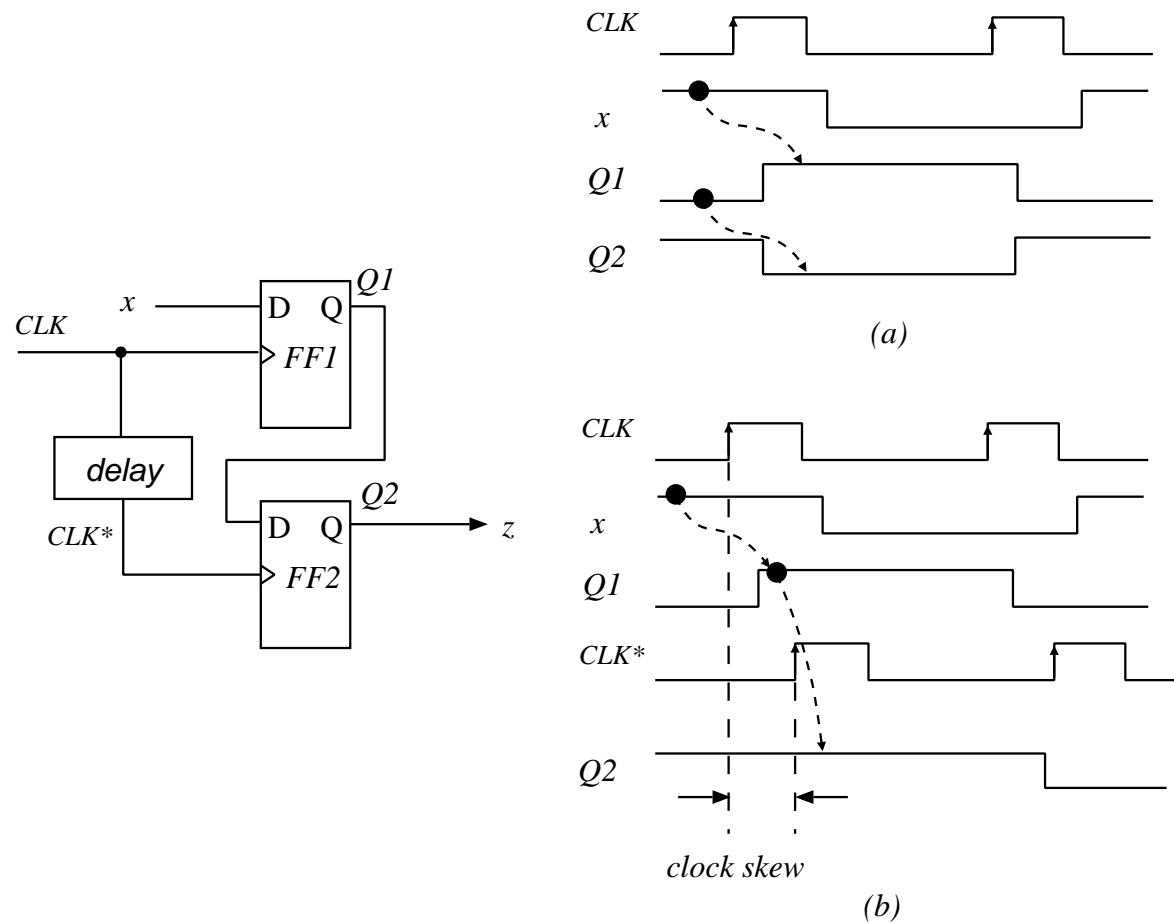


Figure 8.16: a) NETWORK BEHAVIOR WITHOUT CLOCK SKEW. b) NETWORK BEHAVIOR WITH INADMISSIBLE CLOCK SKEW.



1. ANALYZE COMBINATIONAL NETWORK  
DETERMINE THE TRANSITION AND OUTPUT FUNCTIONS
2. DETERMINE HIGH-LEVEL SPECIFICATION OF STATE DESCRIPTION  
OUTPUT FUNCTIONS.
3. IF DESIRED (OR REQUIRED), DETERMINE TIME BEHAVIOR

## EXAMPLE 8.4: ANALYSIS

 


Figure 8.17: SEQUENTIAL NETWORK IN Example 8.4.

State transition	$Y_0 = x'y_1 + xy_0'$
	$Y_1 = xy_0'y_1 + x'y_0'y_1 + xy_0y_1 + x'y_0y_1'$
Output	$z_0 = y_1'$
	$z_1 = y_0$

## EXAMPLE 8.4 (cont.)

- STATE-TRANSITION AND OUTPUT FUNCTIONS:

$PS$	Input		
$y_1y_0$	$x = 0$	$x = 1$	
00	01	11	01
01	11	00	11
10	10	01	00
11	00	10	10
	$Y_1Y_0$		$z_1z_0$
	$NS$		Output

- CODES:

$x$	$x$	$z_1z_0$	$z$	$y_1y_0$	$s$
0	$a$	00	$c$	00	$S_0$
1	$b$	01	$d$	01	$S_1$
		10	$e$	10	$S_2$
		11	$f$	11	$S_3$

## EXAMPLE 8.4 (cont.)

---

- HIGH-LEVEL SPECIFICATION:

Input:  $x(t) \in \{a, b\}$   
 Output:  $z(t) \in \{c, d, e, f\}$   
 State:  $s(t) \in \{S_0, S_1, S_2, S_3\}$   
 Initial state:  $s(0) = S_2$

Functions: The state-transition and output functions

<i>PS</i>	$x(t) = a$	$x(t) = b$	
$S_0$	$S_1$	$S_3$	$d$
$S_1$	$S_3$	$S_0$	$f$
$S_2$	$S_2$	$S_1$	$c$
$S_3$	$S_0$	$S_2$	$e$
	$NS$		$z(t)$

 


Figure 8.18: a) STATE DIAGRAM FOR SEQUENTIAL NETWORK.

$x(t)$	$a$	$a$	$b$	$a$	$b$	$b$	$a$	$b$	$a$	$a$	$b$	$b$	$b$	$a$	
$s(t)$	$S_2$	$S_2$	$S_2$	$S_1$	$S_3$	$S_2$	$S_1$	$S_3$	$S_2$	$S_2$	$S_2$	$S_1$	$S_0$	$S_3$	$S_0$
$z(t)$	$c$	$c$	$c$	$f$	$e$	$c$	$f$	$e$	$c$	$c$	$c$	$f$	$d$	$e$	$d$

Figure 8.18: b) A sequence of input-output pairs.

## PROPAGATION DELAY $x$ to $z_0$ :

INPUT LOAD FACTORS:	$I_x = 4$
SET-UP TIME:	$  \begin{aligned}  t_{su}(net) &= t_{pHL}(\text{NOT}) + t_{pHL}(\text{AND3}) \\  &\quad + t_{pHL}(\text{OR4}) + t_{su} \\  &= (0.05 + 0.017 \times 3) + (0.18 + 0.018) \\  &\quad + (0.45 + 0.025) + 0.3 \\  &= 1.07 \text{ [ns]}  \end{aligned}  $
HOLD TIME:	$t_h(net) = 0.14 \text{ [ns]}$
PROPAGATION DELAY:	$  \begin{aligned}  t_p(z_0) &= t_{pLH}(\text{FF}) + t_{pHL}(\text{NOT}) \\  &= (0.49 + 0.038 \times 3) \\  &\quad + (0.05 + 0.017 \times (L + 3)) \\  &= 0.70 + 0.017L \text{ [ns]} \\  &\quad (\text{load of NOT is } L + 3, \text{ load of FF is } 3)  \end{aligned}  $
SIZE:	$  \begin{aligned}  &= 6 \times 2 + 2 + 3 + 2 \times 6 + 3 \times 1 \\  &= 32 \text{ equivalent gates.}  \end{aligned}  $

1. TRANSFORM THE TRANSITION AND OUTPUT FUNCTIONS
2. SPECIFY A STATE REGISTER TO ENCODE THE REQUIRED NUMBER OF STATES
3. DESIGN THE REQUIRED COMBINATIONAL NETWORK

## EXAMPLE 8.5: DESIGN

---

Input:  $x(t) \in \{a, b, c\}$   
 Output:  $z(t) \in \{0, 1\}$   
 State:  $s(t) \in \{A, B, C, D\}$   
 Initial state:  $s(0) = A$

Functions: The state-transition and output functions

<i>PS</i>	Input		
	<i>x = a</i>	<i>x = b</i>	<i>x = c</i>
<i>A</i>	<i>C,0</i>	<i>B,1</i>	<i>B,0</i>
<i>B</i>	<i>D,0</i>	<i>B,0</i>	<i>A,1</i>
<i>C</i>	<i>A,0</i>	<i>D,1</i>	<i>D,0</i>
<i>D</i>	<i>B,0</i>	<i>A,0</i>	<i>D,1</i>
	<i>NS, z</i>		



## EXAMPLE 8.5 (cont.)

## ● CODING:

Input code			State code		
$x$	$x_1$	$x_0$	$s$	$y_1$	$y_0$
$a$	0	1	$A$	0	0
$b$	1	0	$B$	1	0
$c$	1	1	$C$	0	1
			$D$	1	1

## EXAMPLE 8.5 (cont.)

- STATE-TRANSITION AND OUTPUT FUNCTIONS

$PS$	$x_1x_0$		
	01	10	11
00	01,0	10,1	10,0
10	11,0	10,0	00,1
01	00,0	11,1	11,0
11	10,0	00,0	11,1
$Y_1Y_0, z$ $NS, \text{ Output}$			

$$Y_1: \begin{array}{c|cccc} & \overbrace{x_0} & & & \\ & - & 0 & 1 & 1 \\ y_1 & - & 0 & 1 & 1 \\ & - & 1 & 1 & 0 \\ & - & 1 & 0 & 1 \\ & & \underbrace{x_1} & & \end{array} \Bigg| y_0$$

$$Y_0: \begin{array}{c|cccc} & \overbrace{x_0} & & & \\ & - & 1 & 0 & 0 \\ y_1 & - & 0 & 1 & 1 \\ & - & 0 & 1 & 0 \\ & - & 1 & 0 & 0 \\ & & \underbrace{x_1} & & \end{array} \Bigg| y_0$$

$$z: \begin{array}{c|cccc} & \overbrace{x_0} & & & \\ & - & 0 & 0 & 1 \\ y_1 & - & 0 & 0 & 1 \\ & - & 0 & 1 & 0 \\ & - & 0 & 1 & 0 \\ & & \underbrace{x_1} & & \end{array} \Bigg| y_0$$

$$Y_1 = y_1'x_1 + y_1x_1' + y_0'x_0' + y_0x_1x_0$$

$$Y_0 = y_0'x_1' + y_1'y_0x_1 + y_0x_1x_0$$

$$z = y_1'x_0' + y_1x_1x_0$$

## EXAMPLE 8.5 (cont.)

 


Figure 8.19: SEQUENTIAL NETWORK IN Example 8.5.

# SR FLIP-FLOP

 


Figure 8.20: SR FLIP-FLOP AND ITS STATE DIAGRAM.

$PS = Q(t)$	$S(t)R(t)$			
	00	01	10	11
0	0	0	1	-
1	1	0	1	-
	$NS = Q(t + 1)$			

$$Q(t + 1) = Q(t)R'(t) + S(t) \text{ restriction: } R(t) \cdot S(t) = 0$$

## JK FLIP-FLOP

 


Figure 8.21: JK FLIP-FLOP AND ITS STATE DIAGRAM.

$PS = Q(t)$	$J(t)K(t)$			
	00	01	10	11
0	0	0	1	1
1	1	0	1	0
$NS = Q(t + 1)$				

$$Q(t + 1) = Q(t)K'(t) + Q'(t)J(t)$$

## T (Toggle) FLIP-FLOP

 


Figure 8.22: T FLIP-FLOP AND ITS STATE DIAGRAM.

$PS = Q(t)$	$T(t)$	
	0	1
0	0	1
1	1	0
$NS = Q(t + 1)$		

$$Q(t + 1) = Q(t) \oplus T(t)$$

# IMPLEMENTING ONE FF TYPE WITH ANOTHER

 


Figure 8.23: T FLIP-FLOP IMPLEMENTED WITH JK FLIP-FLOP.

1. OBTAIN THE TRANSITION FUNCTION OF THE NETWORK
  - (a) DETERMINE THE INPUTS TO THE FLIP-FLOPS
  - (b) USE THE TRANSITION FUNCTION OF THE FLIP-FLOPS TO DETERMINE THE NEXT STATE
  
2. OBTAIN THE OUTPUT FUNCTION
  
3. DETERMINE A SUITABLE HIGH-LEVEL SPECIFICATION



# CHARACTERISTICS OF A FAMILY OF CMOS FLIP-FLOPS

FF type	Delays					Input factor [std. loads]	Size [equiv. gates]
	$t_{pLH}$ [ns]	$t_{pHL}$ [ns]	$t_{su}$ [ns]	$t_h$ [ns]	$t_w$ [ns]		
D	$0.49 + 0.038L$	$0.54 + 0.019L$	0.30	0.14	0.20	1	6
JK	$0.45 + 0.038L$	$0.47 + 0.022L$	0.41	0.23	0.20	1	8

$L$ : output load of the flip-flop

These flip-flops have only uncomplemented outputs

## EXAMPLE 8.6: ANALYSIS

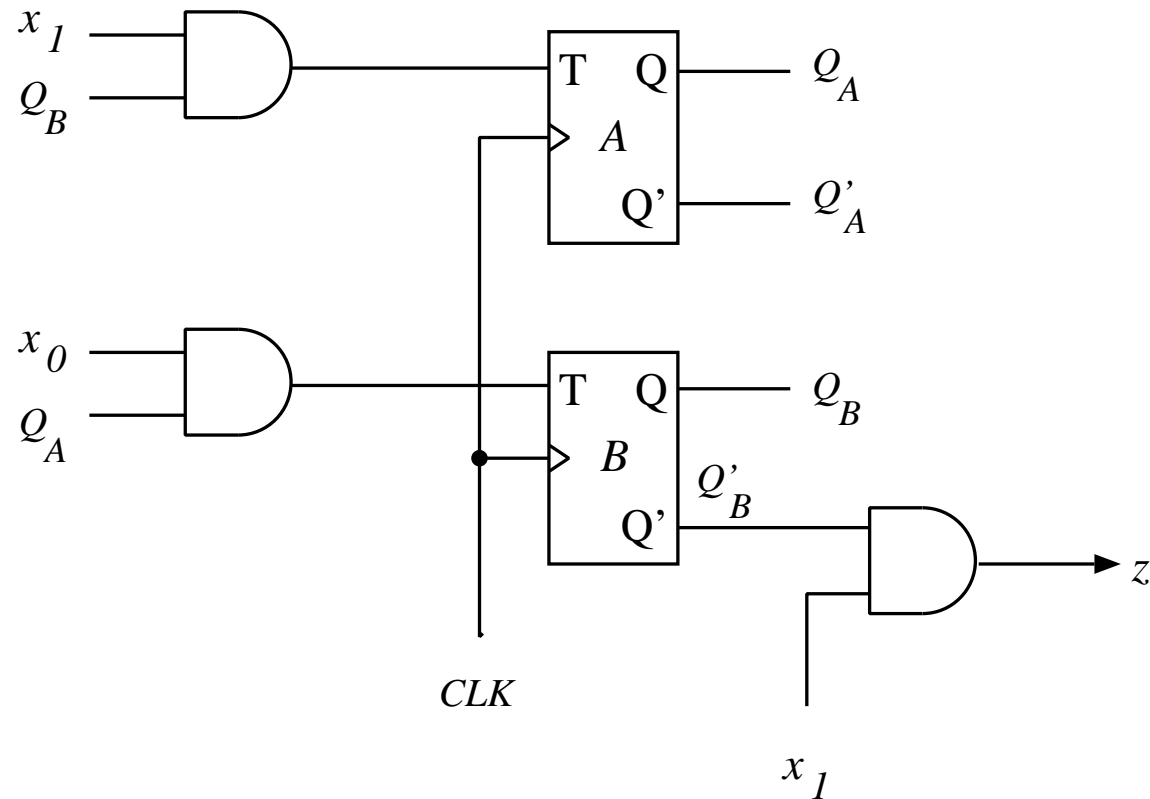


Figure 8.24: SEQUENTIAL NETWORK FOR Example 8.6.

$$\begin{aligned}
 T_A &= x_1 Q_B & Q_A(t+1) &= Q_A(t) \oplus x_1 Q_B(t) \\
 T_B &= x_0 Q_A & Q_B(t+1) &= Q_B(t) \oplus x_0 Q_A(t) \\
 z(t) &= x_1(t) Q'_B(t)
 \end{aligned}$$

## EXAMPLE 8.6 (cont.)

- STATE-TRANSITION AND OUTPUT FUNCTIONS

$PS$	Input								
$Q_A Q_B$	$x_1 x_0$				$x_1 x_0$				
	00	01	10	11	00	01	10	11	
00	00	00	00	00	0	0	1	1	
01	01	01	11	11	0	0	0	0	
10	10	11	10	11	0	0	1	1	
11	11	10	01	00	0	0	0	0	
	$Q_A Q_B$					$z$			
	$NS$					Output			

- CODING:

$Q_A$	$Q_B$	$s$	$x_1$	$x_0$	$x$
0	0	$S_0$	0	0	$a$
0	1	$S_1$	0	1	$b$
1	0	$S_2$	1	0	$c$
1	1	$S_3$	1	1	$d$

## EXAMPLE 8.6 (cont.)

---

- HIGH-LEVEL DESCRIPTION:

Input:  $x(t) \in \{a, b, c, d\}$

Output:  $z(t) \in \{0, 1\}$

State:  $s(t) \in \{S_0, S_1, S_2, S_3\}$

Initial state:  $s(0) = S_0$

Functions: The state-transition and output functions

<i>PS</i>	<i>x</i>				<i>x</i>			
	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>
<i>S</i> <sub>0</sub>	<i>S</i> <sub>0</sub>	<i>S</i> <sub>0</sub>	<i>S</i> <sub>0</sub>	<i>S</i> <sub>0</sub>	0	0	1	1
<i>S</i> <sub>1</sub>	<i>S</i> <sub>1</sub>	<i>S</i> <sub>1</sub>	<i>S</i> <sub>3</sub>	<i>S</i> <sub>3</sub>	0	0	0	0
<i>S</i> <sub>2</sub>	<i>S</i> <sub>2</sub>	<i>S</i> <sub>3</sub>	<i>S</i> <sub>2</sub>	<i>S</i> <sub>3</sub>	0	0	1	1
<i>S</i> <sub>3</sub>	<i>S</i> <sub>3</sub>	<i>S</i> <sub>2</sub>	<i>S</i> <sub>1</sub>	<i>S</i> <sub>0</sub>	0	0	0	0
	<i>NS</i>				<i>z</i>			

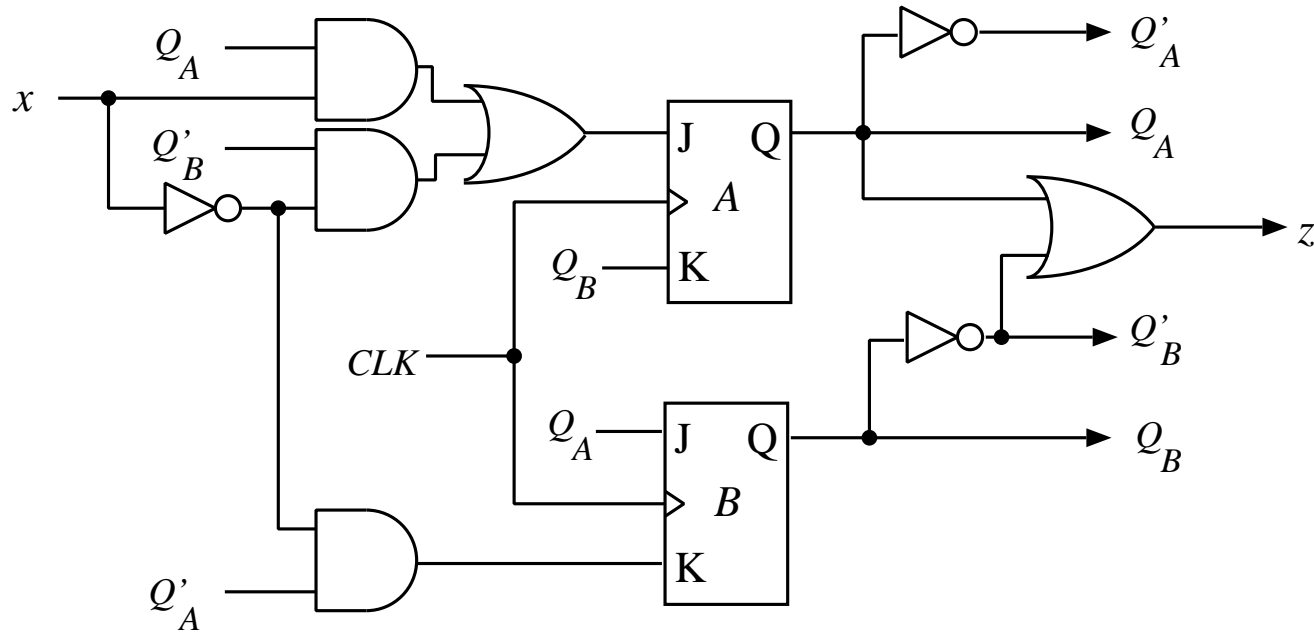


Figure 8.25: SEQUENTIAL NETWORK FOR Example 8.7

$$J_A = x'Q'_B + xQ_A \quad K_A = Q_B$$
$$J_B = Q_A \quad K_B = x'Q'_A$$
$$z = Q_A + Q'_B$$

## EXAMPLE 8.7 (cont.)

---

$$\begin{aligned} J_A &= x'Q'_B + xQ_A & K_A &= Q_B \\ J_B &= Q_A & K_B &= x'Q'_A \end{aligned}$$

$$z = Q_A + Q'_B$$

$$\begin{aligned} Q_A(t+1) &= Q_AK'_A + Q'_AJ_A \\ &= Q_AQ'_B + Q'_A(x'Q'_B + xQ_A) \\ &= Q'_B(Q_A + x') \end{aligned}$$

$$\begin{aligned} Q_B(t+1) &= Q_BK'_B + Q'_BJ_B \\ &= Q_B(x + Q_A) + Q'_BQ_A \\ &= Q_Bx + Q_A \end{aligned}$$

## EXAMPLE 8.7 (cont.)

- STATE-TRANSITION AND OUTPUT FUNCTIONS

$PS$	$NS$		Output
	$x = 0$	$x = 1$	$z$
$Q_A Q_B$	$Q_A Q_B$	$Q_A Q_B$	
00	10	00	1
01	00	01	0
10	11	11	1
11	01	01	1

- STATE CODING

$Q_A$	$Q_B$	$S$
0	0	$S_0$
0	1	$S_1$
1	0	$S_2$
1	1	$S_3$

## EXAMPLE 8.7 (cont.)

---

- HIGH-LEVEL DESCRIPTION

Input:  $x(t) \in \{0, 1\}$

Output:  $z(t) \in \{0, 1\}$

State:  $s(t) \in \{S_0, S_1, S_2, S_3\}$

Initial state:  $s(0) = S_0$

Functions: The state-transition and output functions

$PS$	Input		
	$x = 0$	$x = 1$	
$S_0$	$S_2$	$S_0$	<b>1</b>
$S_1$	$S_0$	$S_1$	<b>0</b>
$S_2$	$S_3$	$S_3$	<b>1</b>
$S_3$	$S_1$	$S_1$	<b>1</b>
	$NS$		$z$



EXAMPLE 8.7 (cont.)

 


Figure 8.26: STATE DIAGRAM IN Example 8.7.

## OTHER CHARACTERISTICS (Example 8.6)

---

INPUT LOAD FACTOR:  $I_x = 2$

---

SET-UP TIME: 
$$\begin{aligned}
 t_{su}(net) &= t_{pLH}(\text{NOT}) + t_{pLH}(\text{AND}) + t_{pLH}(\text{OR}) \\
 &\quad + t_{su}(FF) \\
 &= (0.02 + 0.038 \times 2) + (0.15 + 0.037) \\
 &\quad + (0.12 + 0.037) + 0.41 \\
 &= 0.86 \text{ [ns]}
 \end{aligned}$$

---

HOLD TIME:  $t_h(net) = 0.23 \text{ [ns]}$

---

PROPAGATION DELAY: 
$$\begin{aligned}
 t_p(net) &= t_{pHL}(FF) + t_{pLH}(\text{NOT}) + t_{pLH}(\text{OR}) \\
 &= (0.47 + 0.022 \times 2) + (0.02 + 0.038 \times 2) \\
 &\quad + (0.12 + 0.037L) \\
 &= 0.73 + 0.037L \text{ [ns]}
 \end{aligned}$$

---

SIZE: 
$$\begin{aligned}
 &= 3 + 2 \times 5 + 8 \times 2 \\
 &= 29 \text{ equivalent gates}
 \end{aligned}$$

- EXCITATION FUNCTION  $E(Q(t), Q(t + 1))$

from	to	inputs should be
$Q(t) = 0$	$Q(t + 1) = 0$	$S(t) = 0, R(t) = dc$
$Q(t) = 0$	$Q(t + 1) = 1$	$S(t) = 1, R(t) = 0$
$Q(t) = 1$	$Q(t + 1) = 0$	$S(t) = 0, R(t) = 1$
$Q(t) = 1$	$Q(t + 1) = 1$	$S(t) = dc, R(t) = 0$

## EXCITATION FUNCTIONS

---

### D flip-flop

<i>PS</i>	<i>NS</i>	
	0	1
0	0	1
1	0	1
	<i>D(t)</i>	

$$D(t) = Q(t + 1)$$

### JK flip-flop

<i>PS</i>	<i>NS</i>	
	0	1
0	0-	1-
1	-1	-0
	<i>J(t)K(t)</i>	

### SR flip-flop

<i>PS</i>	<i>NS</i>	
	0	1
0	0-	10
1	01	-0
	<i>S(t)R(t)</i>	

### T flip-flop

<i>PS</i>	<i>NS</i>	
	0	1
0	0	1
1	1	0
	<i>T(t)</i>	

$$T(t) = Q(t) \oplus Q(t + 1)$$

1. OBTAIN A BINARY DESCRIPTION OF THE SYSTEM
2. SELECT THE TYPE OF FLIP-FLOP
3. DETERMINE THE INPUTS TO THE FLIP-FLOPS (use the excitation function)
4. DESIGN A COMBINATIONAL NETWORK

## EXAMPLE 8.8: DESIGN MODULO-5 COUNTER

- USE T FLIP-FLOPS

Input:  $x(t) \in \{0, 1\}$

Output:  $z(t) \in \{0, 1, 2, 3, 4\}$

State:  $s(t) \in \{S_0, S_1, S_2, S_3, S_4\}$

Initial state:  $s(0) = S_0$

Functions: Counts modulo-5, i.e.,  
(0,1,2,3,4,0,1,2,3,4,0...),

 


Figure 8.27: STATE DIAGRAM FOR Example 8.8.

## EXAMPLE 8.8 (cont.)

$z$	$z_2$	$z_1$	$z_0$
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0

$PS$	Input		Input	
$Q_2Q_1Q_0$	$x = 0$	$x = 1$	$x = 0$	$x = 1$
000	000	001	000	001
001	001	010	000	011
010	010	011	000	001
011	011	100	000	111
100	100	000	000	100
	$NS$		$T_2T_1T_0$	

DON'T CARES: 5, 6, AND 7

## EXAMPLE 8.8 (cont.)

sm – STATE MAP

sm:

		$x$				
		0	0	1	1	
$Q_2$		0	0	1	1	$Q_1$
		2	2	3	3	
		6	6	7	7	
		4	4	5	5	
		$Q_0$				

$T_2$ :

		$x$				
		0	0	0	0	
$Q_2$		0	0	0	0	$Q_1$
		0	0	1	0	
		-	-	-	-	
		0	1	-	-	
		$Q_0$				

$T_1$ :

		$x$				
		0	0	1	0	
$Q_2$		0	0	1	0	$Q_1$
		0	0	1	0	
		-	-	-	-	
		0	0	-	-	
		$Q_0$				

$T_0$ :

		$x$				
		0	1	1	0	
$Q_2$		0	1	1	0	$Q_1$
		0	1	1	0	
		-	-	-	-	
		0	0	-	-	
		$Q_0$				

$$T_2 = xQ_2 + xQ_1Q_0$$

$$T_1 = xQ_0$$

$$T_0 = xQ'_2$$



 


Figure 8.28: SEQUENTIAL NETWORK IN Example 8.8.

## EXAMPLE 8.9: DESIGN

---

Input:  $\mathbf{x}(t) = (x_1, x_0), x_i \in \{0, 1\}$

Output:  $z(t) \in \{0, 1\}$

State:  $s(t) \in \{a, b, c, d\}$

Initial state:  $s(0) = a$

Functions: The transition and output functions

<i>PS</i>	$x_1x_0$		
	01	10	11
<i>a</i>	<i>b,0</i>	<i>c,1</i>	<i>c,0</i>
<i>b</i>	<i>a,0</i>	<i>d,1</i>	<i>d,0</i>
<i>c</i>	<i>d,0</i>	<i>c,0</i>	<i>a,1</i>
<i>d</i>	<i>c,0</i>	<i>a,0</i>	<i>d,1</i>
	<i>NS, z</i>		

## EXAMPLE 8.9 (CONT.)

State	$Q_1Q_0$	$PS$		$x_1x_0$			$Q(t)$		$Q(t+1)$		$S$	$R$
		$Q_1Q_0$		01	10	11						
$a$	00	00		01	10	10	0	0	0	-		
$b$	01	01		00	11	11	0	1	1	0		
$c$	10	10		11	10	00	1	0	0	1		
$d$	11	11		10	00	11	1	1	-	0		
				$NS$								

$$S_1: \begin{array}{c} \overline{x_0} \\ \begin{array}{|c|c|c|c|} \hline - & 0 & 1 & 1 \\ \hline - & 0 & 1 & 1 \\ \hline - & - & - & 0 \\ \hline - & - & 0 & - \\ \hline \end{array} \end{array} \begin{array}{l} \\ \\ \\ \\ \end{array} \left. \begin{array}{l} \\ \\ \\ \\ \end{array} \right| Q_0$$

$$S_0: \begin{array}{c} \overline{x_0 x_1} \\ \begin{array}{|c|c|c|c|} \hline - & 1 & 0 & 0 \\ \hline - & 0 & - & - \\ \hline - & 0 & - & 0 \\ \hline - & 1 & 0 & 0 \\ \hline \end{array} \end{array} \begin{array}{l} \\ \\ \\ \\ \end{array} \left. \begin{array}{l} \\ \\ \\ \\ \end{array} \right| Q_0$$

$$\overline{x_1}$$

$$R_1: \begin{array}{c} \overline{x_0} \\ \begin{array}{|c|c|c|c|} \hline - & - & 0 & 0 \\ \hline - & - & 0 & 0 \\ \hline - & 0 & 0 & 1 \\ \hline - & 0 & 1 & 0 \\ \hline \end{array} \end{array} \begin{array}{l} \\ \\ \\ \\ \end{array} \left. \begin{array}{l} \\ \\ \\ \\ \end{array} \right| Q_0$$

$$R_0: \begin{array}{c} \overline{x_0 x_1} \\ \begin{array}{|c|c|c|c|} \hline - & 0 & - & - \\ \hline - & 1 & 0 & 0 \\ \hline - & 1 & 0 & 1 \\ \hline - & 0 & - & - \\ \hline \end{array} \end{array} \begin{array}{l} \\ \\ \\ \\ \end{array} \left. \begin{array}{l} \\ \\ \\ \\ \end{array} \right| Q_0$$

$$\overline{x_1}$$

$$S_1 = x_1 Q'_1$$

$$R_1 = x'_0 Q_1 Q_0 + x_1 x_0 Q_1 Q'_0$$

$$S_0 = x'_1 Q'_0$$

$$R_0 = x'_1 Q_0 + x'_0 Q_1$$

$z:$	$x_0$				
	-	0	0	1	
	-	0	0	1	$Q_0$
$Q_1$	-	0	1	0	
	-	0	1	0	
	$x_1$				

THE OUTPUT EXPRESSION IS

$$z = x'_0 Q'_1 + x_1 x_0 Q_1$$

## EXAMPLE 8.9 (cont.)

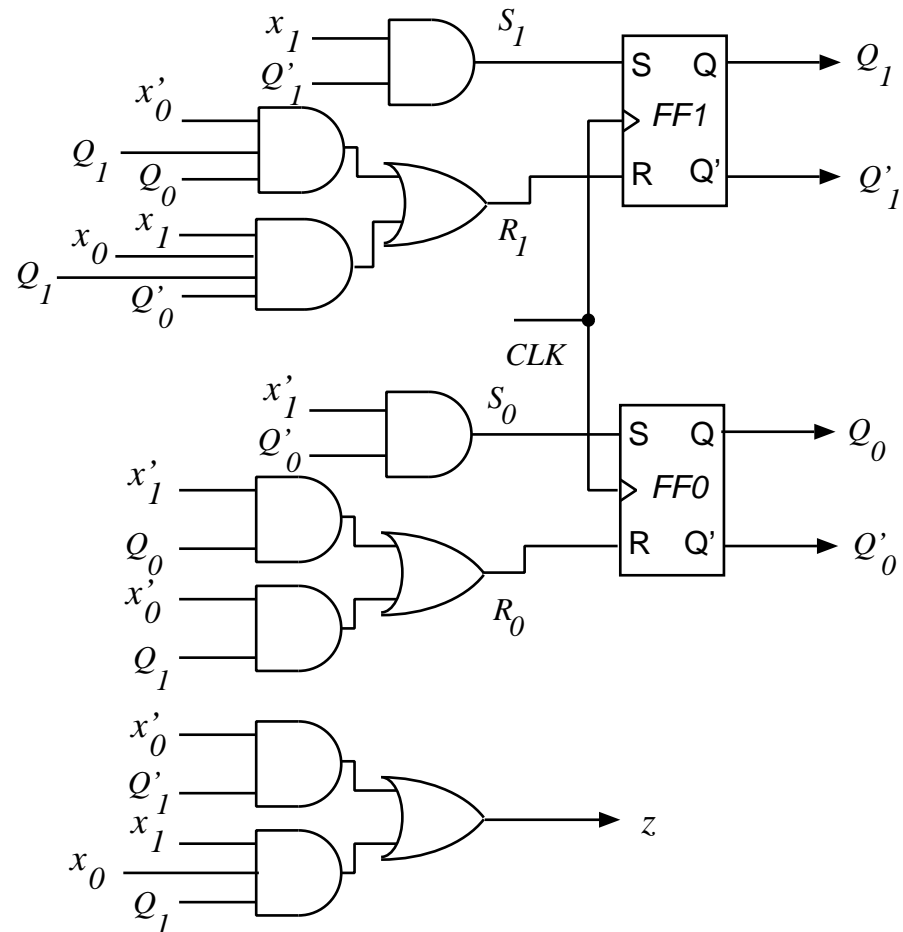


Figure 8.29: SEQUENTIAL NETWORK IN Example 8.9.

- ONE FLIP-FLOP PER STATE

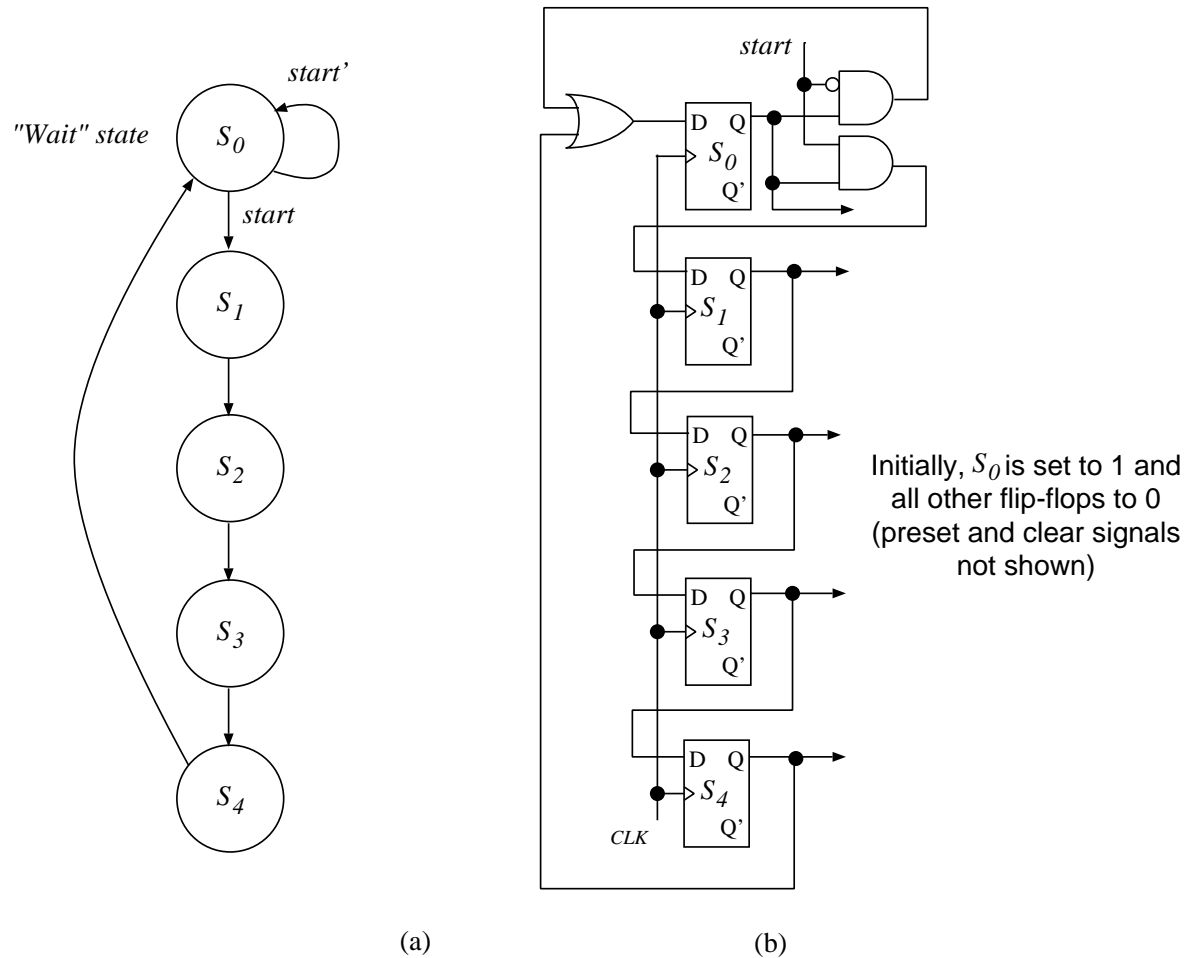


Figure 8.30: ONE FLIP-FLOP PER STATE APPROACH: a) STATE DIAGRAM. b) IMPLEMENTATION (Outputs omitted).

# PRIMITIVES FOR “one-flip-flop-per-state” APPROACH

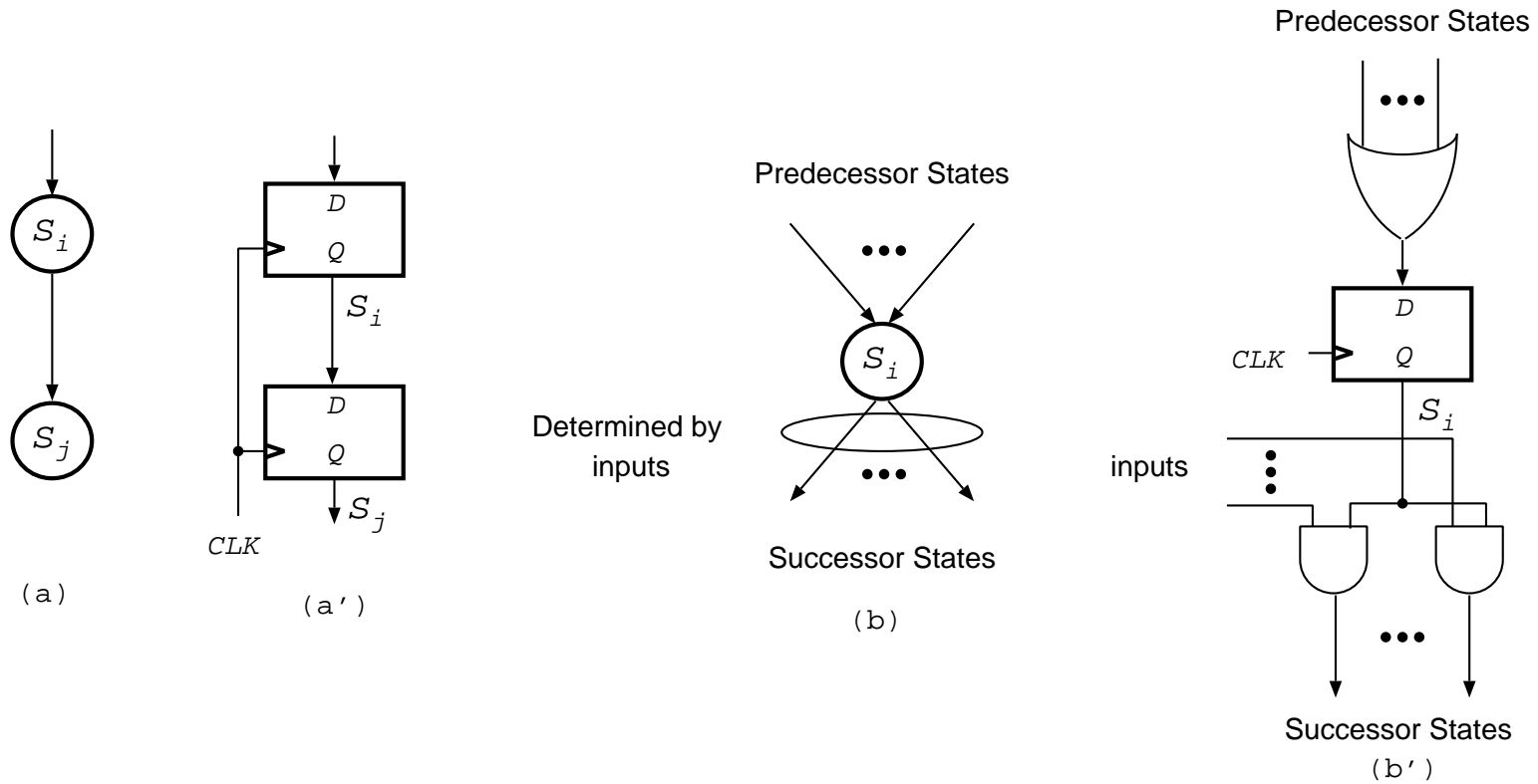


Figure 8.31: PRIMITIVES FOR THE “ONE-FLIP-FLOP-PER-STATE” APPROACH.

# CONTROLLER FOR SIMPLE VENDING MACHINE


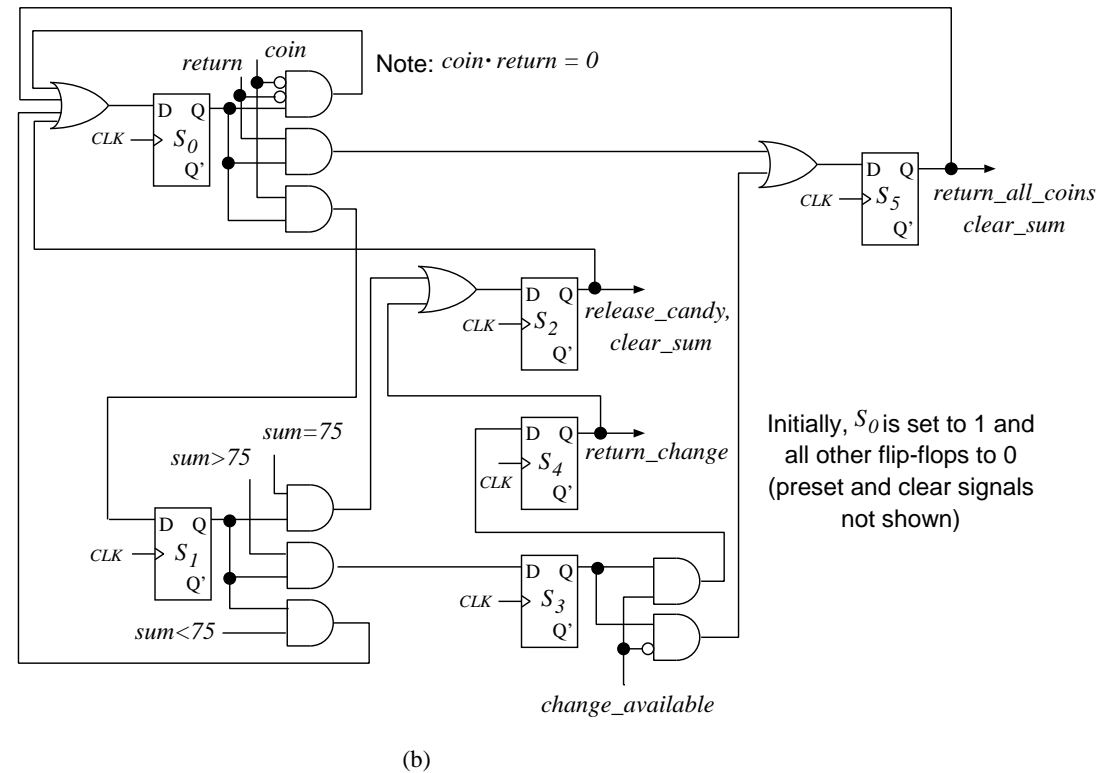


Figure 8.32: A ONE-FLIP-FLOP-PER-STATE IMPLEMENTATION OF A CONTROLLER FOR VENDING MACHINE: a) STATE DIAGRAM. b) IMPLEMENTATION.

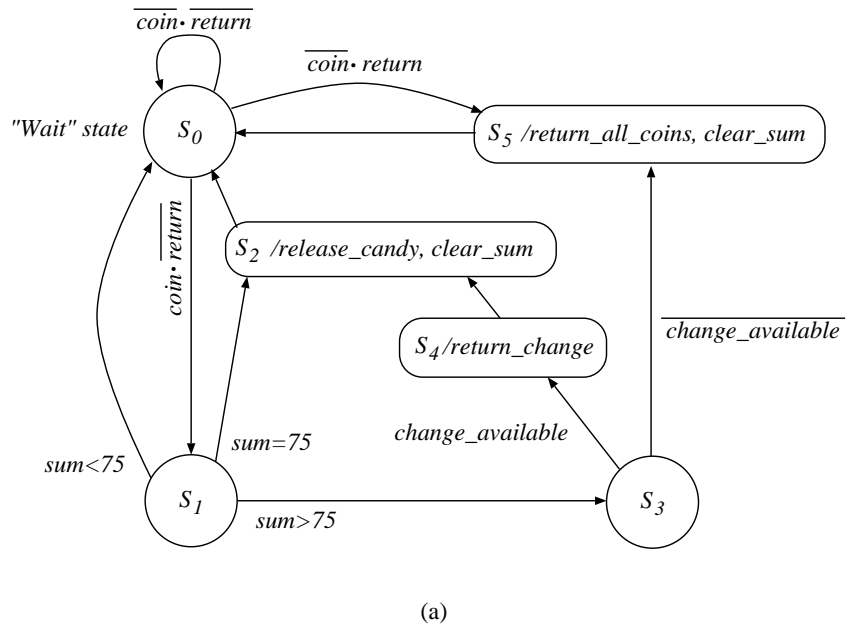

## SHIFTING STATE REGISTER: Example 8.10

---

Input:  $x(t) \in \{0, 1\}$

Output:  $z(t) \in \{0, 1\}$

Function:  $z(t) = \begin{cases} 1 & \text{if } x(t-3, t) = 1101 \\ 0 & \text{otherwise} \end{cases}$

 


Figure 8.33: IMPLEMENTATION OF PATTERN RECOGNIZER IN EXAMPLE 8.10.